

USN

--	--	--	--	--	--	--	--	--	--	--	--

06ES34

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018
Network Analysis

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting atleast TWO questions from each part.

PART - A

- 1 a. Explain the following terms with reference to network topology.
i) tree ii) graph iii) cut-set matrix iv) tie set matrix. (08 Marks)
- b. Write a note on duality in network topology. (02 Marks)
- c. For the network shown in Fig.Q1(c), determine the node voltage. (10 Marks)

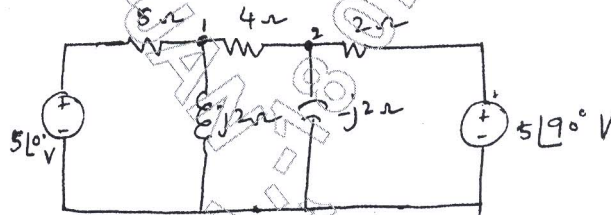


Fig.Q1(c)

- 2 a. State and explain Thevenin's theorem as applied to AC circuit. (08 Marks)
- b. Using Thevenin's theorem, find the current through the coil $(5 + j4)\Omega$ is the bridge circuit shown in Fig.Q2(b). (08 Marks)

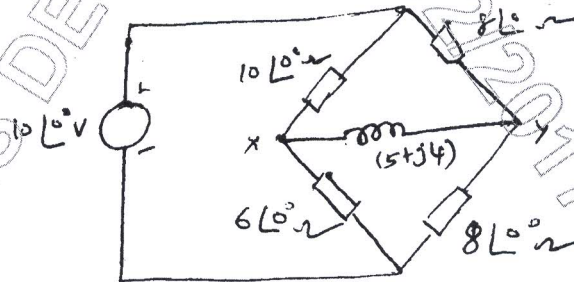


Fig.Q2(b)

- c. Using Norton's theorem find the current through R_L in the circuit shown in Fig.Q2(c). (04 Marks)

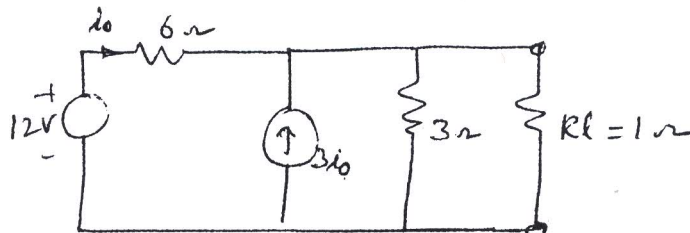


Fig.Q2(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

06ES34

- 3 a. State and explain maximum power transfer theorem. (06 Marks)
 b. Find the value of Z_L to have maximum power transfer from the $10\angle 0^\circ$ voltage source. Also determine the amount of maximum power is eth circuit shown in Fig.Q3(b). (08 Marks)

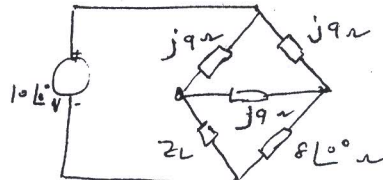


Fig.Q3(b)

- c. Find the current through capacitor $(-j5)\Omega$ reactance in the circuit shown in Fig.Q3(c), using super position theorem. (06 Marks)

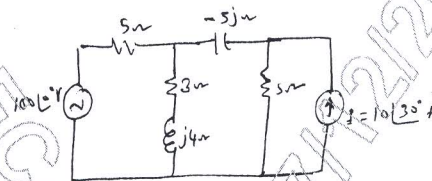


Fig.Q3(c)

- 4 a. Explain the following terms with reference to a resonant circuit :
 i) bandwidth ii) quality factor iii) selectivity curve. (06 Marks)
 b. In the circuit shown in Fig.Q4(b), the current is at maximum value I_m with capacitor value $C = 100 \mu\text{F}$ and $I_m/\sqrt{2}$ with $C = 12.5 \mu\text{F}$. Find the value of Q of the coil at $\omega = 1000$ rad/sec. (07 Marks)

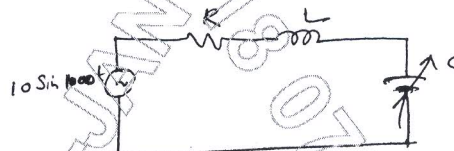


Fig.Q4(b)

- c. In the network shown in Fig.Q4(c), find the value of C for resonance to take place at $\omega = 500$ rad/sec. Also determine the branch currents. (07 Marks)

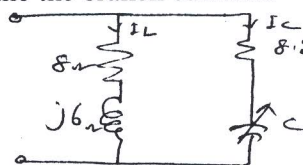


Fig.Q4(c)

PART - B

- 5 a. Why initial conditions are essential? Write a note on initial conditions in basic current elements. (04 Marks)
 b. Define time constant. Explain time constants in case of series RL and series RC circuit. Explain their importance is switching circuits. (06 Marks)
 c. In the network of the Fig.Q5(c), the switch K is closed at $t = 0$ with the capacitor uncharged. Find the values for i , di/dt and d^2i/dt^2 at $t = 0^+$. (10 Marks)

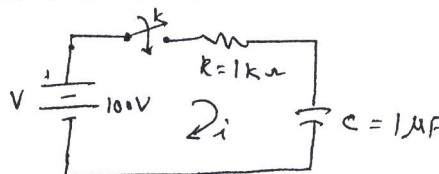


Fig.Q5(c)

- 6 a. In the network shown in the Fig.Q6(a) a steady state is reached with the switch 'k' open. At $t = 0$ the switch is closed. For the element values given, determine the values of $V_a(0^-)$ and $V_a(0^+)$. (10 Marks)

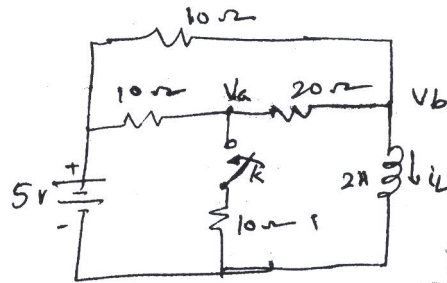


Fig.Q6(a)

- b. Discuss with switch examples the shifting and scaling properties of the Laplace transform. (10 Marks)
- 7 a. Find the Laplace transform of the following function using convolution theorem :
- i) $F_1(s) = \frac{1}{s}$ $F_2 = \frac{1}{(s+1)}$
- ii) $F_1(s) = \frac{1}{s(s+1)}$ $F_2(s) = \frac{1}{(s+2)}$ (10 Marks)
- b. The waveform shown in Fig.Q7(b) is a sweep voltage used to deflect a beam in a CRO. Show that the Laplace transform of this function is $f(s) = \frac{1}{as^2} - \frac{e^{-as}}{s(1 - e^{-as})}$. (10 Marks)

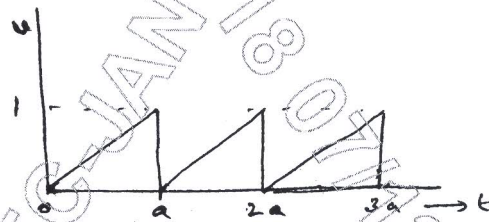


Fig.Q7(b)

- 8 a. Derive equations for the relationship between 'h' and 'y' parameters of a two port network. (10 Marks)
- b. Determine the ABCD parameters for the network shown in Fig.Q8(b). (10 Marks)

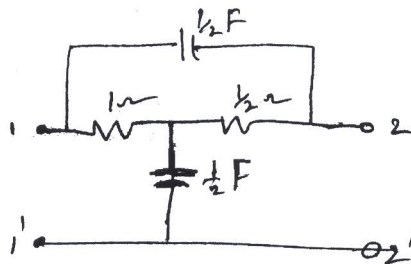


Fig.Q8(b)
