

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018
Analog Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Using Shockley's equation, determine the diode current at 25°C for a silicon diode with $I_S = 20 \text{ pA}$ and $V_D = 0.7 \text{ V}$. Find the same when $V_D = 0.5 \text{ V}$. (04 Marks)
- b. Sketch the output waveform for the following circuit shown in Fig. Q1 (b), and plot the transfer characteristics - (06 Marks)

 


Fig. Q1 (b)

- c. Check the condition for the following circuit shown in Fig. Q1 (c) to work as clamper. Sketch the output waveform. (05 Marks)

 


Fig. Q1 (c)

- d. Find the current in the loop, the output voltage, and the power absorbed by each device. (05 Marks)

 


Fig. Q1 (d)

- 2 a. Derive the expression for I_B and V_{CE} of an emitter bias circuit. (04 Marks)
- b. Check the condition for the approximate analysis of the voltage-divider bias circuit and obtain the Q-point using approximate analysis, given : $V_{CC} = +12 \text{ V}$, $\beta = 120$, $R_C = 1.5 \text{ K}\Omega$, $R_E = 620 \Omega$, $R_1 = 33 \text{ k}\Omega$ and $R_2 = 4.7 \text{ k}\Omega$. Mark the Q-point on the DC load - line. (06 Marks)
- c. Determine the values for the following circuit: V_E , I_E , V_{CE} , V_C , I_B and β . (06 Marks)

 



Fig. Q2 (c)

- d. Design a fixed bias circuit for $V_{CC} = 10 \text{ V}$, $\beta = 120$, $I_{CQ} = 1.4 \text{ mA}$ and $V_{CEQ} = 5 \text{ V}$.

(04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

- 3 a. Using r_e model, derive the expressions for Z_i , Z_o and A_V of a fixed bias circuit. (06 Marks)
 b. Using exact analysis, determine Z_i , Z_o and A_V for the voltage-divider bias network if $R_1 = 220 \text{ k}\Omega$, $R_2 = 56 \text{ k}\Omega$, $R_C = 6.8 \text{ k}\Omega$, $R_E = 2.2 \text{ k}\Omega$, $\beta = 180$, $r_o = 50 \text{ k}\Omega$ and $V_{CC} = 20\text{V}$. (10 Marks)
 c. For the network shown in Fig. Q3 (c), determine Z_i , Z_o and A_V - (04 Marks)

 

$h_{fe} = 150$
 $h_{ie} = 2.75 \text{ k}\Omega$
 $h_{oe} = 25 \mu\text{S}$

Fig. Q3 (c)

- 4 a. Explain the frequency response curves for RC-coupled, transformer-coupled and direct-coupled amplifiers, with reasons for the drop in gain. (09 Marks)
 b. Determine the mid-band gain and the lower cut-off frequencies f_{L_s} and f_{L_c} for the voltage-divider bias BJT amplifier with $C_s = 10 \mu\text{F}$, $C_c = 10 \mu\text{F}$, $R_s = 1 \text{ k}\Omega$, $R_1 = 36 \text{ k}\Omega$, $R_2 = 8.2 \text{ k}\Omega$, $R_E = 1.5 \text{ k}\Omega$, $R_C = 4.7 \text{ k}\Omega$, $R_L = 2.2 \text{ k}\Omega$, $\beta = 100$ and $V_{CC} = 20\text{V}$. (11 Marks)

PART - B

- 5 a. For a Darlington connection, derive the expressions for Z_i , Z_o , A_i and A_V . (12 Marks)
 b. Mention the advantages and disadvantages of the negative feedback. (04 Marks)
 c. Calculate the gain, input impedance and output impedance of a voltage-series-feedback amplifier having $A = -300$, $R_i = 1.5 \text{ k}\Omega$, $R_o = 50 \text{ k}\Omega$ and $\beta = -\frac{1}{15}$. (04 Marks)
 6 a. Enumerate the types of power amplifiers along with their efficiency, conduction angle and Q-point. (05 Marks)
 b. Prove that the maximum efficiency of a class-B power amplifier is 78.5%. (05 Marks)
 c. Calculate the efficiency of the following circuit shown in Fig. Q6 (c), for an input current swing of 10 mA. (05 Marks)

 


Fig. Q6 (c)

- d. Along with the circuit diagram, explain the working of Class-C amplifier. (05 Marks)
 7 a. Along with the circuit diagram, explain the working of a BJT phase-shift oscillator. (06 Marks)
 b. Design a Wien-bridge oscillator for $f_0 = 6 \text{ kHz}$, making suitable assumptions. (06 Marks)
 c. Along with proper diagrams, explain the series resonant and parallel resonant crystal oscillators using BJT. (08 Marks)
 8 a. Explain the operation of JFET amplifier using fixed bias. Draw the JFET small signal model, and derive the expressions for Z_i , Z_o and A_V . (10 Marks)
 b. With necessary circuit diagram, obtain the expressions for Z_i , Z_o and A_V for an E-MOSFET voltage-divider configuration. (10 Marks)