

USN

--	--	--	--	--	--	--	--	--	--

10EE752

Seventh Semester B.E. Degree Examination, Dec.2017/Jan.2018
Programmable Logic Controllers

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Explain the internal Architecture of PLC, with a neat block diagram. (10 Marks)
- b. What are proximity switches? Explain different types of proximity switches. (06 Marks)
- c. Mention any two advantages and disadvantages of PLC. (04 Marks)

- 2 a. Write the Ladder diagram for following gates with 2 inputs A and B, O/P C. (06 Marks)
 i) AND ii) OR iii) NOT iv) NAND v) NOR vi) XOR.
- b. Represent the following boolean equation using function block diagram and ladder diagram. (08 Marks)
 i) $Q = (A \cdot B + C)\bar{D} \cdot E \cdot \bar{F}$ ii) $Y = AB + \bar{A}B$
- c. Write a note on the configuration of multiple outputs. (06 Marks)

- 3 a. Convert the given ladder diagram in Fig. Q3(a) to function block diagram and write the boolean expression (06 Marks)

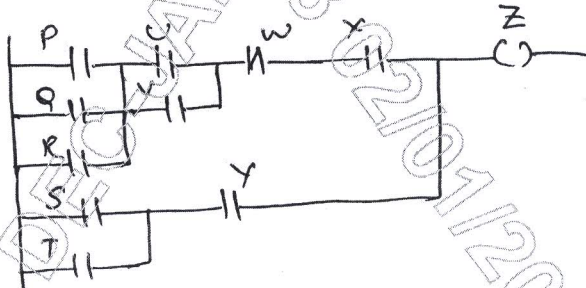


Fig Q3(a)

- b. Write short note on iteration statement used in structured text. (06 Marks)
- c. Explain how branching and convergence is realized in sequential function chart. (08 Marks)

- 4 a. Write ladder diagram and instruction list needed to implement a system in which, for output H to be ON, Input A must be ON both inputs C and D must be off. In addition one or more of inputs E, F and G must be off. (08 Marks)
- b. Explain Jump with jump operation with suitable example ladder. (06 Marks)
- c. For the instruction list below, draw the corresponding ladder diagram. (06 Marks)

```

(i) LD X400 (ii) LD A
    OR X402    AND B
    LD X401    LD C
    OR X403    ORB
    ANB
    OUT Y430   OUT Z
    END        END
    
```

(06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

PART – B

- 5 a. Explain the principle of operation of a master control relay with relevant ladder diagram and programming instructions. (08 Marks)
- b. Explain the working of battery backed relays with relevant ladder diagram. (06 Marks)
- c. Write short note on one-shot operation with relevant ladder diagram. (06 Marks)
- 6 a. Name and explain three different forms of timers with timing diagram. (08 Marks)
- b. Explain with the ladder diagram usage of Timers for flashing of light on and off as long as there is an output occurring. (06 Marks)
- c. Write a ladder diagram with programming instructions to switch on a light 8secs after receiving an input and keep it on for the duration of that input. (06 Marks)
- 7 a. Explain the operation of pulse timer with relevant ladder diagram. (06 Marks)
- b. Explain the use of counter to extend the range of timer. (06 Marks)
- c. Write an instruction list program and ladder diagram for a counter to control a machine which is required to direct 6 tins along one path for packaging in a box and then 12 tins for packaging in another box. A deflector plate might be controlled by a photocell sensors that gives an output every time a tin passes and also draw the ladder diagram. (08 Marks)
- 8 a. Write a ladder program that switches on a pump when the water level in a tank rises above 1.2m and switches it off when it falls below 1.0m. Explain the data comparison unit used. (08 Marks)
- b. Explain the implementation of closed loop control system using PLC's. (06 Marks)
- c. Explain with ladder diagram and the sequence signals of a 4-bit shift register. (06 Marks)
