

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

CMRIT LIBRARY  
BANGALORE - 560 037

15EE35

## Third Semester B.E. Degree Examination, June/July 2018 Digital System Design

Time: 3 hrs.

Max. Marks: 80

*Note: Answer any FIVE full questions, choosing one full question from each module.*

### Module-1

- Define combinational logic, canonical SOP and canonical POS, with examples. (06 Marks)
  - Place the following equations into proper canonical form:
    - $R = f(a, b, c) = (\bar{a} + b)(b + c)$  into minterm canonical form. (04 Marks)
    - $Z = f(a, b, c) = a + \bar{a}b$  into maxterm canonical form. (04 Marks)
  - Solve the following Boolean equation using four variable Karnaugh map and implement the simplified equation using minimum number of logic gates.  
 $f(a, b, c, d) = \sum (0, 5, 7, 8, 10, 13) + d (2, 4, 14, 15)$ . (06 Marks)

OR

- Solve four variable expression using Quine McCluskey minimization technique.  
 $K = f(a, b, c, d) = \pi M(0, 3, 4, 7, 8, 10, 12, 14) + d(2, 6)$  (08 Marks)
  - Simplify the Boolean expression using a 3-variable VEM, with 'Z' as MEV  
 $f(w, x, y, z) = \sum m(3, 4, 5, 7, 8, 11, 12, 13, 15)$ . (08 Marks)

### Module-2

- Implement 3-bit binary to gray code conversion circuit using IC 74139. Draw neat diagram, truth table with switching equations in SOP form. (06 Marks)
  - Implement the following multiple output functions for active low outputs using IC74138.  
 $F_1 = f(x, y, z) = \bar{x}y + xy\bar{z} + xz$ ,  $F_2 = f(x, y, z) = \pi(0, 1, 4, 5, 7)$ . (04 Marks)
  - What are multiplexers? Implement the function using 8:1 MUX,  
 $f(a, b, c, d) = \sum m(0, 1, 3, 4, 7, 10, 11, 14, 15)$ . (06 Marks)

OR

- Implement 4-bit parallel adder/subtractor using 4-full adder blocks. If  $C_{in} = 0$  the circuit should act as adder and if  $C_{in} = 1$  the circuit should act as subtractor. Explain its operation by considering examples. (06 Marks)
  - What is the problem associated with the parallel adder? Explain the method of correcting it, with suitable circuit and equations. (06 Marks)
  - Design 1-bit comparator circuit, represent truth table, K-maps and logic diagram. (04 Marks)

### Module-3


- Explain the operation of Master-Slave JK flip-flop with logic diagram, truth table, symbol and timing diagram. (08 Marks)
  - Distinguish between sequential circuits and combinational circuits. (04 Marks)
  - Explain the operation of basic bistable element, using two-inverter configuration. (04 Marks)

OR

- Derive characteristics equations for SR flip-flop and JK flip-flop, represent truth table and K-maps. (04 Marks)
  - Explain the operation of 4-bit ring counter and twisted ring counter. (06 Marks)
  - Design synchronous MOD6 counter using clocked 'D' flip flops for the sequence  $0 \rightarrow 2 \rightarrow 3 \rightarrow 6 \rightarrow 5 \rightarrow 1$ , again, 0.... represent application table, excitation table and logic diagram. (06 Marks)


**CMRIT LIBRARY**  
**BANGALORE - 560 037**  
**Module-4**

 - 7 a. Define state variables and excitation variables and write a note on Moore and Mealy sequential models. (08 Marks)
- b. For the logic diagram shown in Fig.Q.7(b), find excitation table, state table and state diagram. (08 Marks)




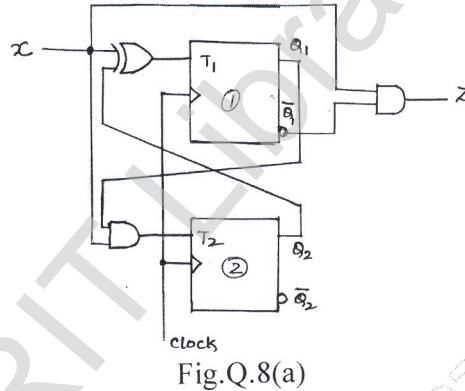**OR**

- 8 a. Analyze the circuit shown in Fig.Q.8(a), obtain excitation table, state table and state diagram. (10 Marks)



 - b. Design the sequential logic circuit for single input single output system shown in Fig.Q.8(b) state diagram using clocked 'D' flip-flop. (06 Marks)



**Module-5**

- 9 a. Explain the structure of VHDL and verilog module with example code for each and compare them. (08 Marks)
- b. List the various styles/types of descriptions in VHDL and verilog. Explain VHDL structural description with example code. (08 Marks)

**OR**

- 10 a. Explain the structure of data flow description in VHDL and verilog, using suitable example code. (08 Marks)
- b. Write VHDL and verilog code for  $2 \times 2$  magnitude comparator for all input combinations. (08 Marks)

\*\*\*\*\*