

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EE36

CMRIT LIBRARY
BANGALORE - 560 037

Third Semester B.E. Degree Examination, June/July 2018 Electrical and Electronic Measurements

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Discuss limitations of Wheatstone Bridge and explain how low resistance is measured by KDB. (08 Marks)
- b. For an ac bridge evaluate unknown impedance in the arm DC when bridge is balanced at 2kHz with following components in each arm.
Arm AB: $10k\Omega$
Arm BC: $100\mu F$ series with $100k\Omega$
Arm AD: $50k\Omega$
Detector is connected between B and D. (08 Marks)

OR

- 2 a. Obtain the dimensional equations in SI units for
i) Absolute permeability ii) Absolute permittivity. (06 Marks)
- b. Discuss how capacitance of the capacitor is measured by Schering bridge. (10 Marks)

Module-2

- 3 a. Reproduce the errors in 1- ϕ kWh meter and explain how energy meter calibrated. (08 Marks)
- b. A 1- ϕ energy meter operating at normal 1- ϕ voltage has a constant load of 4A passing through it for 6 hrs at 0.8 power factor. If the meter disc makes 2209 revolutions during this period, what is the meter constant in revolutions/kWh? Calculate the power factor of the load if the number of revolutions made by meter are 1472 when operated at normal 1- ϕ AC supply at 5A for 4 hrs. (08 Marks)

OR

- 4 a. Explain the construction and operating principle of Weston frequency meter and 1- ϕ pf meter. (08 Marks)
- b. Discuss phase sequence indicator. (03 Marks)
- c. A Wattmeter has current coil and pressure coil resistance of 0.2Ω and 5000Ω respectively. Evaluate the percentage of error in the Wattmeter reading when load takes 20A, at 250V with 0.8 pf lag for two methods of connection of Wattmeter. (05 Marks)

Module-3

- 5 a. Discuss Silsbee's method of testing CT. (08 Marks)
- b. What do you mean by shunts and multipliers and derive the expression for shunt and multipliers. (08 Marks)

OR

- 6 a. Discuss how the iron losses are measured by using Wattmeter. (07 Marks)
- b. List advantages of instrument transformers. (02 Marks)
- c. Discuss how leakage flux is measured. (07 Marks)

1 of 2

CMRIT LIBRARY
BANGALORE - 560 037

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

CMRIT LIBRARY
BANGALORE - 560 037

Module-4

- 7 a. List advantages of electronic meters over the conventional meters. (03 Marks)
b. Discuss construction and operation of TRUE RMS reading voltmeter. (05 Marks)
c. List characteristics of DVM and explain successive approximation type DVM. (08 Marks)

OR

- 8 a. Explain the principle of operation Q meter and discuss different application of Q-meter. (08 Marks)
b. List different types of DVM. Explain with sketch the Ramp type DVM. (08 Marks)

Module-5

- 9 a. Explain why recorders are essential? With sketch explain x-y recorder. (08 Marks)
b. Discuss with necessary figure i) ECG ii) EEG. (08 Marks)

OR

- 10 a. Write a short notes on i) LED ii) Nixie tube iii) LCD. (08 Marks)
b. With neat sketch explain LVDT recorder. (05 Marks)
c. Write a short note on dot matrix display. (03 Marks)

* * * * *

CMRIT LIBRARY
BANGALORE - 560 037