

USN

--	--	--	--	--	--	--	--	--	--

**CMRIT LIBRARY**  
BANGALORE - 560 037

10EE56

**Fifth Semester B.E. Degree Examination, June/July 2018**

**Linear ICs and Applications**

Time: 3 hrs.

Max. Marks:100

**Note: 1. Answer any FIVE full questions, selecting at least TWO questions from each part.**

**2. Use of 741 data sheet is permitted.**

**3. Use standard resistor and capacitor chart is permitted.**

**PART – A**

1. a. Explain the operation of high input impedance capacitor coupled voltage follower. Develop the expression for input impedance  $Z_{in}$ . (08 Marks)
- b. Discuss the need to set upper cut off frequency of an OPAMP. Show how upper cut off frequency can be set for an inverting amplifier. (06 Marks)
- c. Design a capacitor coupled voltage follower using 741 OPAMP. The lower cut off frequency of circuit is to be 50 Hz. Take  $R_L = 3.9 K\Omega$ . (06 Marks)
2. a. Discuss briefly phase-lag compensation for frequency compensation. (08 Marks)
- b. Discuss the compensation for stray capacitance effect with necessary circuit. (06 Marks)
- c. What are the precautions to be observed for OPAMP circuit stability? (06 Marks)
3. a. Mention advantage of precision rectifier over ordinary diode rectifier. Sketch circuit of precision full wave rectifier using half wave rectifier and summer. Explain the working of the circuit. (08 Marks)
- b. Explain the operation of voltage follower peak detector with necessary circuit diagram. (06 Marks)
- c. With a neat circuit explain operation of a 2-bit flash ADC. (06 Marks)
4. a. A capacitor coupled zero crossing detector is to handle 1 kHz square wave input with peak-to-peak amplitude of 6V. Design a suitable circuit using OPAMP 741 with  $\pm 12V$  supply. Also estimate minimum slew rate of circuit. (08 Marks)
- b. Sketch the circuit of OPAMP astable multivibrator. Explain its operation with relevant waveforms. (06 Marks)
- c. Discuss how trigger points can be adjusted to realize a different UTP and LTP for a inverting Schmitt trigger circuit. (06 Marks)

**PART – B**

5. a. Explain with necessary circuit operation of triangular/rectangular waveform generator. Draw waveforms at various output points. (08 Marks)
- b. Explain with necessary circuit how diodes may be used for output amplitude stabilization with Wein bridge oscillator. (06 Marks)
- c. Design phase shift oscillator to have a frequency of 3.5 kHz. Use OPAMP 741 with  $\pm 12V$  supply. (06 Marks)

**CMRIT LIBRARY**  
BANGALORE - 560 037

- 6 a. Sketch circuit of a single stage band pass filter. Explain the lowpass and highpass operation of circuit. (08 Marks)
- b. Design a 2<sup>nd</sup> order lowpass filter for a cutoff frequency of 2 kHz using OPAMP 741. (06 Marks)
- c. Explain how band stop filter can be realized using lowpass filter, highpass filter and summer. (06 Marks)
- 7 a. Explain the theory of operation of switched capacitor filters. (06 Marks)
- b. Explain with block diagram the operation of PLL. (08 Marks)
- c. Draw circuit representation of LM380 power amplifier and discuss its features. (06 Marks)
- 8 a. Discuss about the various parameters used to measure regulator performance. (06 Marks)
- b. Explain the operation of adjustable output regulator with necessary circuit. (08 Marks)
- c. Sketch regulator using LM340IC voltage regulator. Briefly discuss LM340 and its performance. (06 Marks)