

USN									
-----	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, June/July 2019 Digital System Design

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Prove the following using Boolean theorems : (04 Marks)
 i) $(x + \bar{x}\bar{y})(\bar{x} + \bar{y}) + yz = \bar{y} + z$ ii) $\bar{w}\bar{y}\bar{z} + wz + \bar{y}z + xyz = \bar{w}\bar{y} + wz + xz$.
 b. Using K - maps determine all the minimal sums and products of the following Boolean function.
 i) $f(w, x, y, z) = \pi m(1, 3, 4, 5, 10, 11, 12, 14)$
 ii) $g(a, b, c, d) = \Sigma m(0, 1, 4, 8, 9, 10) + dc(2, 11)$. (07 Marks)
 c. Using MEV method determine minimal sum for the following function where x, y, z are map variables. Realize the expression using double rail logic. (05 Marks)
 $f(A, B, x, y, z) = A\bar{x}\bar{y}\bar{z} + A\bar{x}\bar{y}z + Ax\bar{y}z + B\bar{x}\bar{y}z + B\bar{x}yz + \bar{x}yz + x\bar{y}\bar{z}$.

OR

- 2 a. For the following Boolean function use Quine Mc Cluskey algorithm method and Petrick's method to obtain all the irredundant disjunctive normal expressions. Which of these from minimal sums? $f(a, b, c, d) = \Sigma m(0, 4, 7, 8, 11, 12, 14, 15)$. (08 Marks)
 b. For the following function use decimal Quine Mc Cluskey method and prime implicant table reduction technique to obtain minimal sum.
 $f(a, b, c, d) = \Sigma m(0, 1, 2, 4, 6, 7, 9, 11, 12, 13, 15)$. (08 Marks)

Module-2

- 3 a. Implement the following functions using IC 74139, a - 2 to 4 decoder.
 i) $f_1(abc) = \Sigma(3, 5, 6, 7)$ ii) $f_2(a, b, c) = \Sigma(1, 2, 4)$ (04 Marks)
 b. Design a 4 to 2 line priority encoder with 'valid' output where highest priority is given to input with highest index and obtain the minimal sum expressions for outputs. Realize the expressions with basic gates. (06 Marks)
 c. Design and implement half adder and half subtractor circuits, with a and b as inputs. (06 Marks)

OR

- 4 a. Implement $f(a, b, c) = \Sigma m(1, 4, 5, 6, 7)$ using
 i) 4 - 1 MUX with 'b' and 'c' to select line ii) 2 - 1 MUX with 'a' to select line
 Show with K - maps and logic circuits. (08 Marks)
 b. The 1-bit comparator had 3 outputs corresponding to $a > b$, $a = b$ and $a < b$. It is possible to code these three outputs using two bits pq such that $pq = 10$ for $a > b$, $pq = 00$ for $a = b$ and $pq = 01$ for $a < b$. This reduces the number of output lines of each 1-bit comparator to 2. The 1-bit comparator at the most significant position, however, should have a converter to convert back to three outputs. Design such a 1-bit comparator as well as the output converter network. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Design a switch debouncer using SR latch. Show relevant logic diagram and timing diagrams. (06 Marks)
- b. What are characteristic equations? Derive them for SR, JK and T flip-flops. (06 Marks)
- c. Clearly distinguish between:
- i) Synchronous and asynchronous circuits
 - ii) Combinational and sequential circuits. (04 Marks)

OR

- 6 a. Explain with suitable logic and timing diagram:
- i) Serial-in-serial out shift register
 - ii) Parallel-in-parallel out unidirectional shift register. (08 Marks)
- b. Consider the synchronous counter shown in Fig.Q.6(b). Assuming it is initialized to "000" prior to the first count pulse, determine the counting sequence. Is this counter self correcting. (08 Marks)

 


Fig.Q6(b)

Module-4

- 7 a. Briefly explain structure of clocked synchronous sequential network. (05 Marks)
- b. Compare Mealy and Moore models. (05 Marks)
- c. Construct the state table for the following state diagram in Fig.Q7(c). (06 Marks)

 


Fig.Q7(c)

CMBIT LIBRARY
BANGALORE - 560 037

OR

- 8 a. Design a clocked sequential circuit that operates according to state diagram shown in Fig.Q8(a). Implement the circuit using D-flip-flops. (08 Marks)

 


Fig.Q8(a)

- b. For the clocked synchronous sequential network shown in Fig.Q8(b). Construct excitation table, transition table, state table and state diagram. (08 Marks)

 


Fig.Q8(b)

Module-5

- 9 a. With schematic explain VHDL logical and relational operators. (08 Marks)
 b. Briefly explain all VHDL data types. (08 Marks)

OR

- 10 a. Compare VHDL and verilog in detail. (08 Marks)
 b. Write data flow description of a half adder (in both VHDL and verilog). Draw the truth table and derive the Boolean expressions, simulate and verify the circuit. (08 Marks)
