

Sixth Semester B.E. Degree Examination, June/July 2019 Power System Analysis - I

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Show that per unit impedance of two winding transformer will remain same referred to primary as well as secondary. (06 Marks)
- b. A 300 MVA, 20 KV, 3-phase generator has subtransient reactance of 20%. The generator supplies two synchronous motors through a 64 KVA transmission line having transformers at both ends as shown in Fig.Q1(b). T_1 is a 3-phase transformer and T_2 is composed of 3-single phase transformers of rating 100 MVA each, 127/13.2 KV, 10% reactance, series reactance of transmission line is 0.5 ohm/km. Draw the reactance diagram with all reactances marked in per unit. Select generator rating on base values.

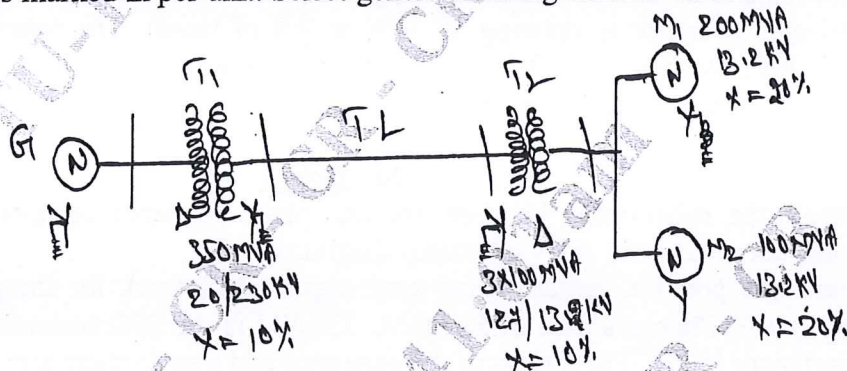


Fig.Q1(b)

(10 Marks)

OR

- 2 a. Define per unit quantity. Mention the advantages of per unit system. (04 Marks)
- b. The one line diagram of an unloaded generator is shown in Fig.Q2(b). Draw the PU reactance diagram. Choose a base of 50 MVA, 13.8 KV in the circuit of generator G_1 . The ratings are as follows:

G_1 : 20 MVA, 13.8 KV, $X'' = 20\%$	T_1 : 25 MVA, 13.8/220 KV, $X = 10\%$
G_2 : 30 MVA, 18 KV, $X'' = 20\%$	T_2 : 30 MVA, 220/18 KV, $X = 10\%$
G_3 : 30 MVA, 20 KV, $X'' = 20\%$	T_3 : 35 MVA, 220/22 KV, $X = 10\%$

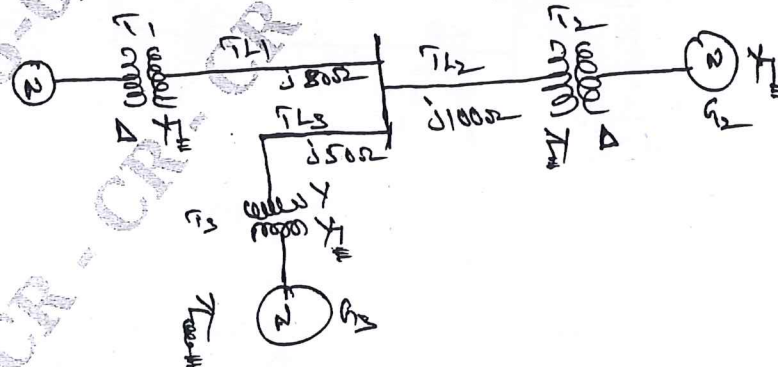


Fig.Q2(b)

(12 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-2

- 3 a. With the help of waveform at the time of three phase symmetrical fault, on synchronous generator define steady state, transient and subtransient reactances. (08 Marks)
- b. A generator is connected to a synchronous motor through transformer. Reduced to a common base, the per unit subtransient reactances of generator and motor are 0.15 and 0.35 PU respectively. The leakage reactance of the transformer is 0.1 PU. A 3-phase star circuit fault occurs at terminals of the motor when terminal voltage of generator is 0.9 P.U and output current of generator is 1 P.U at 0.8 pf leading. Find the subtransient current in the fault, generator and motor.

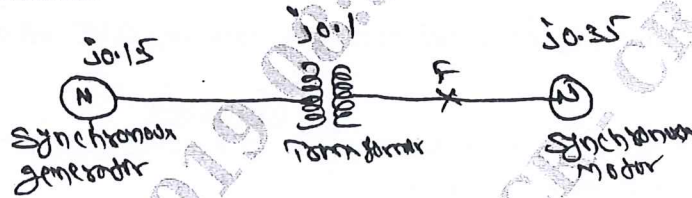


Fig.Q3(b)

(08 Marks)

OR

- 4 a. Explain clearly, how circuit breaker are rated? (06 Marks)
- b. A synchronous generator and motor are rated 30 MVA, 13.2 KV, both have subtransient reactance of 20%. The line connecting them has a reactance of 20%, on the base of machine rating. The motor is drawing 20 MW at 0.8 pf (lead). The terminal voltage of motor is 12.8 KV, when a symmetrical fault occurs at motor terminals, find subtransient current in generator, motor and at the point of fault? (10 Marks)

Module-3

- 5 a. Obtain the relationship between line and phase sequence components of voltages in star connection. Give the relevant phasor diagrams. (08 Marks)
- b. Draw the positive, negative and zero sequence network for the power system shown in Fig.Q5(b). Choose a base of 50 MVA, 220 KV in the 50Ω transmission lines and marks all reactances in PU. The ratings of the generator and transformers are:
 G_1 : 25 MVA, 11 KV, $X'' = 20\%$; G_2 : 25 MVA, 11 KV, $X'' = 20\%$
 3φ transformers (each) : 20 MVA, 11/220 KV, $X = 15\%$
 The negative sequence reactance of each synchronous machine is equal to the sub-transient reactance. The zero sequence reactance of a each machine is 8%. Assume that the zero sequence reactances of lines are 250% of their positive sequence reactances.


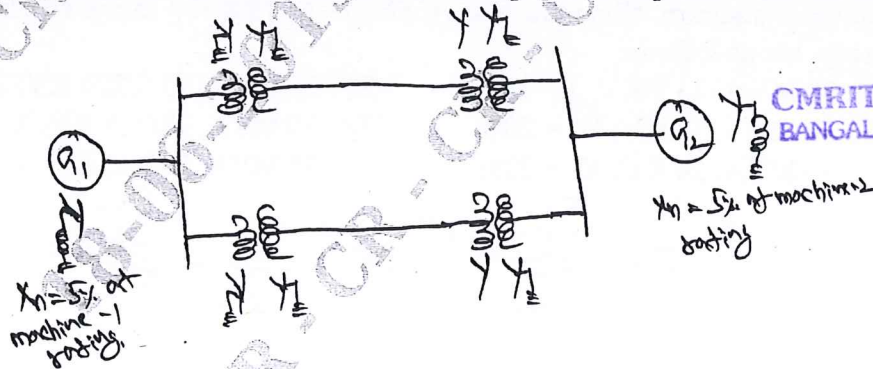


Fig.Q5(b)

(08 Marks)

OR

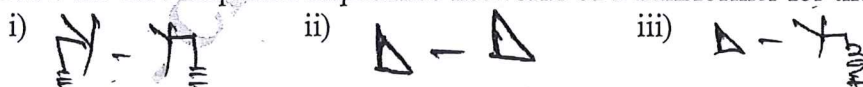- 6 a. Draw the zero sequence impedance networks of a transformer for the following connections:



(06 Marks)

- b. The positive, negative and zero sequence components of line currents are $20\angle 10^\circ$, $6\angle 60^\circ$ and $3\angle 30^\circ$ A respectively. Determine the line currents. (04 Marks)
- c. In a 3ϕ , 4 wire system, the sequence voltages and currents are:
 $V_{a1} = 0.9\angle 10^\circ$ PU; $V_{a2} = 0.25\angle 110^\circ$ PU; $V_{a0} = 0.12\angle 300^\circ$ PU;
 $I_{a1} = 0.75\angle 25^\circ$ PU; $I_{a2} = 0.15\angle 170^\circ$ PU; $I_{a0} = 0.1\angle 330^\circ$ PU
 Find the complex power in PU. If the neutral gets disconnected, find the new power. (06 Marks)

Module-4

- 7 a. An unloaded fully excited three phase alternator is subjected to an L-G fault at its terminals. Find the fault current. Using symmetrical components by showing the interconnection of all sequence networks. (08 Marks)
- b. Draw the sequence networks for the system shown in Fig. Q7(b). Determine the fault current if a line to line occurs at F. The PU reactances all referred to the same base are as follows. Both the generators are generating 1.0 PU.

Component	X_0	X_1	X_2
G_1	0.05	0.30	0.20
G_2	0.03	0.25	0.15
Line-1	0.70	0.30	0.30
Line-2	0.70	0.30	0.30
T_1	0.12	0.12	0.12
T_2	0.10	0.10	0.10

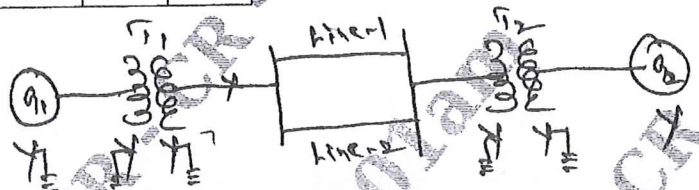


Fig. Q7(b)

(08 Marks)

OR

- 8 a. Derive expression for fault current if Line-Line-Ground (LLG) fault occurs through fault impedance Z_f in power system. Show the connection of sequence networks to represent the fault. (08 Marks)
- b. A three phase generator with an open circuit voltage of 400 V is subjected to an LG fault through a fault impedance of $j2\Omega$. Determine the fault current if $Z_1 = j4\Omega$, $Z_2 = j2\Omega$ and $Z_0 = j1\Omega$. Repeat the problem for LL fault. (08 Marks)

Module-5

- 9 a. Explain 'equal area criteria' concept when a power system is subjected, to sudden loss of one of the 'parallel lines'. (08 Marks)
- b. Define stability pertaining to a power system and classify the different types of stability. (04 Marks)
- c. A 2 pole, 50 Hz, 11 KV turbo alternator has a rating of 100 MW, 0.85 p.f. lagging. The rotor has moment of inertia of 10000 kg-m^2 . Calculate H and M. (04 Marks)

OR

- 10 a. Derive the power angle equation of a salient pole synchronous machine connected to an infinite bus. Draw the power angle curve. (08 Marks)
- b. Derive an expression for the swing equation. (08 Marks)
