

Seventh Semester B.E. Degree Examination, June/July 2019

Industrial Drives and Applications

AdvGALORE. 3 hrs.

Max. Marks:100

Note: 1. Answer any FIVE full questions, selecting at least TWO questions from each part.

2. Any data missing can be assumed.

PART - A

1 a. Explain the different parts of electrical drives system.

(10 Marks)

- b. What is quadrantal diagram? Explain the multi quadrant operation of a motor driving a hoist load. (10 Marks)
- 2 a. What is load equalization? Explain the components of load torque.

(10 Marks)

b. What are the classes of motor duty? Explain them in brief.

- (10 Marks)
- a. Explain the operation of 1φ fully controlled rectifier control of D.C. motor separately excited.

 (10 Marks)
 - b. A 200 V, 875 rpm separately executed d.c. motor has an armature resistance of 0.06 Ω . It is fed from a 1 ϕ fully controlled rectifier with an ac voltage of 220 V, 50 Hz. Assuming continuous conduction, calculate:
 - i) Firing angle for rated motor torque and 750 rpm
 - ii) Firing angle for rated torque with (-500 rpm)
 - iii) Motor speed for $\alpha = 160^{\circ}$ and rated torque.

(10 Marks)

- a. With a relevant circuit diagram and waveforms, explain the operation of chopper control of separately excited d.e. motor. (08 Marks)
 - b. A 230 V, 960 rpm and 200 A, separately excited d.c. motor has an armature resistance of 0.02 Ω. The motor is fed from a chopper which provide both motoring and braking operations. The source has a voltage of 230 V. Assuming continuous conduction.
 - i) Calculate duty ratio of chopper for motoring operation at rated torque and 350 rpm
 - ii) Calculate duty ratio of chopper for braking operation at rated torque and 350 rpm
 - iii) If max. duty ratio of chopper is limited to 0.95 and Max. permissibility motor current is twice the rated. Calculate max permissible field weakening and power feed to the source
 - iv) If motor field is also controlled. Calculate field current as a fraction of its rated filed current as a function of its rated value for a speed of 1200 rpm. (08 Marks)
 - c. Explain regeneration braking of a separately excited D.C. generator using chopper circuit.

 (04 Marks)

PART - B

- 5 a. What are the methods employed for braking of an Induction motor? Explain in brief Regenerative braking. (10 Marks)
 - b. A 400 V, Y connected, 3 phase, 6 pole, 50 Hz induction motor has following parameters referred to the stator $R_s = R_r' = 1\Omega$, $X_s = X_r' = 2\Omega$ for regenerative braking operation of this motor determine:
 - i) Maximum overhauling torque it can hold and range of speed for safe operation.
 - ii) Speed at which it will hold an overhauling load with a torque of 10 N-m. (10 Marks)

- Explain the operation of synchronous machine from a fixed frequency supply. (05 Marks)
 - Explain the operation of braking in synchronous machines. (05 Marks) b.

Explain the steady-state stability limit, and dynamic stability in synchronous motors.

(10 Marks)

- Explain the operation of rotor resistance control of induction motor. (08 Marks)
 - A 3 phase 400 V, 6-pole, 50 Hz, Δ-connected, slip-ring induction motor has rotor resistance of 0.2 Ω and leakage reactance of 1 Ω /phase referred to stator when driving a fan load it runs at full load at 4% slip. What resistance must be inserted in the rotor circuit to obtain a speed of 850 rpm? Neglect stator impedance and magnetizing branch. Stator to rotor ratio is 2.2.

(12 Marks)

- Explain the different drives used in textile mills. (05 Marks)
 - Explain the different drives used in rolling mill drives. BANGALORE - 560 037 (05 Marks) b.
 - Explain the operation of self controlled synchronous motor drive employing load commutated thyristor inverter. (10 Marks)

2 of 2