

CBCS Scheme

USN

ISEC32

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018 Analog Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

1. a. Derive the expression for input impedance, output impedance and voltage given for common emitter fixed bias configuration using re model. (08 Marks)
- b. Draw the graphical symbol and hybrid equivalent model for CE and CB configuration. (04 Marks)
- c. Calculate DC bias voltage and currents for the Darlington configuration shown in Fig.Q1(c). (04 Marks)

 


Fig.Q1(c)

OR

2. a. Derive the expression for Z_i , Z_o and A_v for emitter-follower configuration using re-model. (08 Marks)
- b. For the network shown in Fig.Q2(b), determine Z_i , Z_o , A_v and A_{i_v} . (08 Marks)

 


Fig.Q2(b)

Module-2

3. a. Explain the construction and working principle of n-channel JFET and draw the characteristics. (06 Marks)
- b. Derive an expression for Z_i , Z_o and A_v of FET self bias configuration with bypassed R_S . (06 Marks)
- c. Distinguish between depletion type and enhancement type MOSFET. (04 Marks)

OR

- 4 a. Explain the construction and working principle of n-channel depletion type MOSFET and draw the characteristics curve. (08 Marks)
- b. The source follower circuit shown in Fig.Q4(b) results in $V_{GSQ} = -2.86V$ and $I_{DQ} = 4.56mA$:
- Determine g_m
 - Determine Z_i and Z_o
 - Determine A_v with r_d and without r_d
- $I_{DSS} = 16mA$, $V_P = -4V$; $r_d = 40k\Omega$; $g_{os} = 25\mu S$. (08 Marks)

 


Fig.Q4(b)

CMRIT LIBRARY
BANGALORE - 560 037Module-3

- 5 a. Derive the expression for low frequency response of BJT amplifier due to capacitors C_S and C_C . (08 Marks)
- b. Calculate f_{Hi} and f_{Ho} for amplifier circuit shown in Fig.Q5(b), for the base current $I_B = 14.79\mu A$ and $A_{vmid} = 102.58$; $\beta = 100$; $C_{be} = 20pF$; $C_{bc} = 4pF$; $h_{ie} = 1100$; $C_{wi} = 6pF$; $C_{wo} = 8pF$; $C_{CE} = 1pF$. (08 Marks)

 


Fig.Q5(b)

OR

- 6 a. Derive the expression for Miller's input and output capacitance. (08 Marks)
- b. Obtain the expression for over all lower and higher cut-off frequency for a multistage amplifier. (08 Marks)

Module-4

- 7 a. What are the advantages of negative feedback in amplifier? (04 Marks)
 b. Derive the expression for Z_{if} and Z_{of} for voltage series feedback connection type. (06 Marks)
 c. In a transistor Hartley oscillator, the two inductances are 2mH and $20\mu\text{H}$ while the frequency is to be changed from 950KHz to 2050KHz . Calculate the range over which the capacitor is to be varied. (06 Marks)

OR

- 8 a. Draw the circuit diagram of uni-junction oscillator and explain the principle of operation and draw the characteristics curve. (06 Marks)
 b. With a neat circuit diagram, explain the working of colpitts oscillator using transistor. (06 Marks)
 c. A crystal $L = 0.4\text{H}$, $C = 0.085\text{PF}$ and $C_m = 1\text{PF}$ with $R = 5\text{K}\Omega$ find :
 i) Series resonate frequency
 ii) Parallel resonate frequency. (04 Marks)

CRIT LIBRARY
BANGALORE - 560 037Module-5

- 9 a. With circuit diagram, explain the operation of transformer coupled class -A power amplifier and show that maximum efficiency is 50%. (06 Marks)
 b. Calculate the harmonic distortion components for an output signal having a fundamental amplitude of 2.5V , second harmonic amplitude of 0.25V , third harmonic amplitude of 0.1V and fourth harmonic amplitude of 0.05V . Also calculate the total harmonic distortion. (04 Marks)
 c. Define voltage regulator. Explain series voltage regulator using transistor. (06 Marks)

OR

- 10 a. Explain the operation of a class-B push-pull amplifier and show that maximum conversion efficiency is 78.5%. (08 Marks)
 b. Explain shunt voltage regulator using transistor, and also find the regulated voltage and circuit currents for the shunt regulator shown in Fig.Q10(b). (08 Marks)

 


Fig.Q10(b)
