

Fifth Semester B.E. Degree Examination, Dec.2017/Jan.2018

Fundamentals of CMOS VLSI

Time: 3 hrs.

Max. Marks: 100

Note: 1. Answer any FIVE full questions, selecting at least TWO questions from each part.
 2. Draw Neat diagram.

PART - A

- 1 a. Describe with neat diagrams, the P-well fabrication process. (08 Marks)
- b. Explain the DC transfer characteristics of CMOS inverter and mark all the regions of operation with necessary expressions for V_{out} in each region. (08 Marks)
- c. Compare CMOS and Bipolar Technology. (04 Marks)

- 2 a. Explain Transmission gate and Tristate inverter operations with neat diagram. (06 Marks)
- b. Give the λ -based design rules for different layers, p and n MOSFETs and contact cuts. (08 Marks)
- c. Obtain the stick diagram and layout of two way selector with enable. (06 Marks)

- 3 a. What are the features of CMOS Domino logic? Explain with neat diagram. (06 Marks)
- b. In the following circuit find V_1 , V_2 , V_3 and V_4 . (06 Marks)

 


Fig Q3(b) 1

 


Fig Q3(b) 2

- c. Explain following logic structure with their salient features with neat diagram
 - i) Pseudo nMOS logic
 - ii) C²MOS logic(08 Marks)

- 4 a. Define sheet Resistance and standard unit of capacitance $\square C_g$. (06 Marks)
- b. Explain cascaded inverter to drive large capacitance loads? Obtain an equation to find the number of stages. (08 Marks)
- c. Calculate the total capacitance in terms of $\square C_g$ for the following Fig.Q4(c) (06 Marks)

 


Fig Q4(c)

1 of 2

PART - B

- 5 a. What are the properties of nMOS and PMOS switches? How TG is useful. (06 Marks)
b. Explain the structure design of a parity generation with necessary diagrams and also write stick diagrams. (08 Marks)
c. Obtain the logic implementation of 4-way multiplexer (Selector) using nMOS switches with necessary diagrams. (06 Marks)
- 6 a. Explain nMOS and CMOS non-inverting dynamic storage cell and draw the 4-bit shift register using nMOS. (07 Marks)
b. How to implement arithmetic and logic operation with a standard adder? Explain with the help of logic expression. (06 Marks)
c. Explain 4×4 Barrel shifter with neat diagram. (07 Marks)
- 7 a. What are system timing consideration? (05 Marks)
b. Explain Read/write operation of one T dynamic memory cell (one transistor). (05 Marks)
c. Discuss Baugh Worley method used for Two's complement multiplication with neat diagrams. (10 Marks)
- 8 a. Write a note on Testability and Testing. (06 Marks)
b. What are different types of I/O pads? (06 Marks)
c. Write short notes on:
i) Built in self Test (BIST)
ii) Scan design Technic. (08 Marks)

CMRIT LIBRARY
BANGALORE - 560 037

* * * * *