

USN

--	--	--	--	--	--	--	--	--	--

10TE54

Fifth Semester B.E. Degree Examination, Dec.2017/Jan.2018

Transmission Lines and Waveguides

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Deduce the expression for attenuation constant and phase constant for the following conditions:
 - i) If a transmission line is to have neither frequency distortion nor delay distortion. (06 Marks)
 - ii) The ordinary telephone cable. (06 Marks)
- b. A transmission line has a characteristic impedance of $710 \angle -16^\circ$ at 1 kHz. At this frequency, attenuation and phase shift is found to be 0.01 Np and 0.035 radians per km respectively. Calculate the primary constants of the line. (08 Marks)
- c. With necessary equations, draw the equivalent T-section for transmission line. (06 Marks)
- 2 a. Define insertion loss. Derive an expression for insertion loss of a transmission line. (10 Marks)
- b. A prototype low pass constant K π -section filter network consists of a series arm inductance of 20 mH and two shunt arm capacitor of 0.16 μ F each. Calculate the cut-off frequency, attenuation and phase shift at 15 kHz. What is the value of the nominal impedance in the pass band?

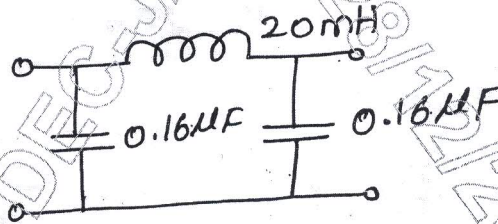


Fig.Q2(b)

- c. Show that the maximum and minimum impedance on the line for a lossless line is given by $R_o S$ and R_o / S respectively. (05 Marks)
- 3 a. Derive expressions for input impedances of open and short circuited lines at radio frequencies. Sketch and comment on the variations of normalized reactance's with various lengths of the line. (10 Marks)
- b. Explain the applications of quarter wave line. (06 Marks)
- c. Calculate the standing wave ratio and reflection coefficient on a line having $Z_o = 300 \Omega$ and terminated by $Z_R = 300 + j400 \Omega$. (04 Marks)
- 4 a. Consider quarter wave small dissipation line. Derive expressions for short circuited and open circuited input impedances. (08 Marks)
- b. A load impedance of $Z_R = 200 - j100 \Omega$ is required to be matched to a 400Ω line by using a short circuited stub of length ' l ' located at a distance ' d ' from the load. The wavelength of operation is 3 meter. Solve the problem numerically and then by Smith chart. (12 Marks)

PART – B

- 5 a. Explain the theory of scattering matrix for a multiport network. (06 Marks)
b. State and prove the properties of S-parameters. (10 Marks)
c. Two transmission lines of characteristic impedance z_1 and z_2 are joined at plane pp' . Express s-parameters in terms of impedances. (04 Marks)
- 6 a. Derive expressions for guide wavelength, phase and group velocities for TM_{mn} waves in rectangular waveguides. (06 Marks)
b. Draw a neat diagram of a H-plane Tee junction and explain its operation. Write its [s] matrix. (07 Marks)
c. Dominant mode is propagated through a waveguide of breadth 10 cm at frequency of 2.5 GHz. Find:
i) Cut-off wavelength ii) Phase velocity iii) Group velocity
iv) Guide wavelength v) Wave impedance vi) Phase constant (07 Marks)
- 7 a. With a neat diagram, explain the working of 2-hole directional coupler. (06 Marks)
b. Explain the operation of parametric amplifier with equivalent circuit. Also explain Manley-Rowe relations. (07 Marks)
c. With a neat diagram, explain the operation of a Faraday rotation isolator. (07 Marks)
- 8 a. Explain the working principle of GUNN diode. (06 Marks)
b. Explain the construction and working of varactor diode. (06 Marks)
c. Explain operating principle and mechanism of oscillations in IMPATT diode with neat and relevant diagram. (08 Marks)

* * * * *