

CBCGS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

CMRIT LIBRARY
BANGALORE - 560 037

15EC655

Sixth Semester B.E. Degree Examination, June/July 2018 Microelectronics

Time: 3 hrs.

Max. Marks: 80

**Note: Answer any FIVE full questions, choosing
ONE full question from each module.**

Module-1

- 1 a. Derive the expression for drain to source current for triode and saturation regions of n-MOSFET. (10 Marks)
- b. Design the circuit shown in Fig.Q1(b) to obtain a drain voltage of 0.1V. Find the value of R_D . At the operating point, let $V_t = 0.5V$ and $K'_n \left(\frac{W}{L} \right) = 2mA / V^2$. (06 Marks)

 


Fig.Q1(b)

OR

- 2 a. Derive the expression for drain current under channel length modulation. (08 Marks)
- b. What is body effect? Write the expressions for V_t related to body effect and draw its small signal model. (04 Marks)
- c. Design the circuit in Fig.Q2(c) to obtain $I_D = 80 \mu A$, find the value required for R and find the DC voltage V_D . Let the NMOS transistor have $V_t = 0.6V$, $\mu_n C_{ox} = 200 \mu A/V^2$, $L = 0.8 \mu m$ and $W = 4 \mu m$. Neglect channel length modulation. (04 Marks)

 


Fig.Q2(c)

Module-2

- 3 a. Briefly explain any two types of biasing methods in MOS amplifier circuits. (06 Marks)
- b. Derive the expression for transconductance g_m and voltage gain A_v for a CS amplifier with small input signal. (10 Marks)

OR

- 4 a. Develop a T equivalent model for the MOSFET from a hybrid π model. (08 Marks)
- b. For a n-channel MOSFET with $t_{ox} = 10nm$, $L = 1.0 \mu m$, $W = 10 \mu m$, $L_{OV} = 0.05 \mu m$, $C_{sbo} = C_{dbo} = 10fF$, $V_0 = 0.6V$, $V_{SB} = 1 V$ and $V_{DD} = 2V$. Calculate the following capacitances when the transistor is operating in saturation C_{OX} , C_{OV} , C_{gs} , C_{gd} , C_{db} , C_{sb} . Given $E_{OX} = 3.45 \times 10^{-11} F/m^2$. (08 Marks)

1 of 2

CMRIT LIBRARY
BANGALORE - 560 037

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-3

- 5 a. Make a comparison between BJT and MOSFET (Any 4 characteristics). (08 Marks)
b. Determine the G_V , A_y , R_{out} , R_{in} , A_{VO} for a common source MOS amplifier without source degeneration. (08 Marks)

OR

- 6 a. Explain the operation of a MOS current steering circuit and mention its advantage. (08 Marks)
b. Consider CG amplifier designed using a circuit. Given $g_m = 1\text{mA/V}$ and $R_D = 15\text{k}\Omega$. Find R_{in} , R_{out} , A_V , A_{VO} , and G_V for $R_L = 15\text{k}\Omega$ and $R_{sig} = 50\Omega$. (08 Marks)

Module-4

- 7 a. A CMOS CS amplifier fabricated in $0.18\mu\text{m}$ technology has $W/L = 7.2\mu\text{m}/0.36\mu\text{m}$ for all transistor $K'_n = 387\mu\text{A/V}^2$, $K'_p = 86\mu\text{A/V}^2$, $I_{ref} = 100\mu\text{A}$, $V'_{An} = 5\text{V}/\mu\text{m}$ and $|V_{AP}| = 6\text{V}/\mu\text{m}$. Find g_{m1} , r_{o1} , r_{o2} and voltage gain. (08 Marks)
b. For a CG amplifier with active load determine the expression for R_i , A_{VO} , A_V , G_{VO} , G_V , R_O . (08 Marks)

OR

- 8 a. Write a notes on : i) Double cascode ii) Folded cascode. (08 Marks)
b. Explain CMOS implementation of common source amplifier. (08 Marks)

Module-5

- 9 a. For a MOS differential pair with a common mode voltage V_{CM} is shown in Fig. Q9 (a). Let $V_{DD} = V_{SS} = 1.5\text{V}$, $K'_n \left(\frac{W}{L}\right) = 4\text{mA/V}^2$, $V_t = 0.5\text{V}$, $I = 0.4\text{mA}$ and $R_D = 2.5\text{k}\Omega$. Neglect channel length modulation.
i) Find V_{OV} and V_{GS} for each transistor
ii) For $V_{CM} = 0$, find V_S , i_d , i_{d2} , V_{d1} and V_{d2}
iii) Repeat (b) for $V_{CM} = +1\text{V}$
iv) What is the highest value for which Q_1 and Q_2 are in saturation? If current I requires a minimum voltage of 0.4V to operate properly. What is the lowest allowed V_S and hence V_{CM} ? (10 Marks)

 


Fig.Q9(a)

- b. What is the effect of mismatch of R_D on CMRR of a MOS differential amplifier? (06 Marks)

OR

- 10 a. Explain the operation of MOS differential pair with a differential input signal. (08 Marks)
b. Explain 2-stage CMOS OPAMP configuration. (08 Marks)

* * * * *