 


CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EC32



Third Semester B.E. Degree Examination, Dec.2018/Jan.2019

Analog Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Define h parameters using two port systems. (05 Marks)
- b. Derive expressions for input impedance, output impedance and voltage gain for common emitter fixed bias configuration using re model. (07 Marks)
- c. Find Z_i , Z_o , A_v and A_i for the network shown in Fig.Q.1(c). Given data $h_{fb} = -0.99$, $h_{ib} = 14.3\Omega$, $h_{ob} = 0.5 \mu A/v$. (04 Marks)

 


Fig.Q.1(c)

OR

- 2 a. Explain hybrid π model. (04 Marks)
- b. Find r_e , Z_i , Z_o and A_v for the circuit shown in Fig.Q.2(b). Given data $B = 90$, $r_o = 50k\Omega$. (05 Marks)

 


Fig.Q.2(b)

- c. Derive the expressions for Z_i , Z_o , A_v and A_i for fixed bias configuration using approximate $C\epsilon$ hybrid equivalent model. (07 Marks)

Module-2

- 3 a. List the differences between JFET and MOSFET. (04 Marks)
- b. Explain with neat sketches, operation and characteristics of n-channel E-MOSFET. (08 Marks)
- c. Find: i) input impedance ii) output impedance iii) voltage gain for the circuit shown in Fig.Q.3(c). Given data $g_m = 2ms$, $r_d = 50K\Omega$. (04 Marks)

 


Fig.Q.3(c)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 4 a. Find transconductance and drain current for the JFET if $I_{DSS} = 20\text{mA}$, $V_P = -5\text{V}$, $V_{GS} = -4\text{V}$ and $g_{m0} = 4\text{ms}$. (04 Marks)
- b. Derive an expressions for Z_i , Z_o and A_v using small signal JFET amplifier under fixed bias configuration. (07 Marks)
- c. Sketch the following circuit diagrams:
- JFET ac equivalent model of source follower
 - Cascaded FET amplifier. (05 Marks)

Module-3

- 5 a. An amplifier rated at a 40W output is connected to a 10Ω speaker, Find:
- Input power required for full output if power gain is 25dB
 - Input voltage for rated output if the amplifier voltage gain is 40dB. (04 Marks)
- b. Explain high frequency response of FET amplifier. (07 Marks)
- c. Explain multistage frequency effects. (05 Marks)

OR

- 6 a. Derive an expressions for Miller input and output capacitor. (06 Marks)
- b. Determine A_v , Z_i and A_{vs} for the low frequency response of the BJT amplifier circuit shown in Fig.Q.6(b). Assume $r_0 = \infty$. (06 Marks)

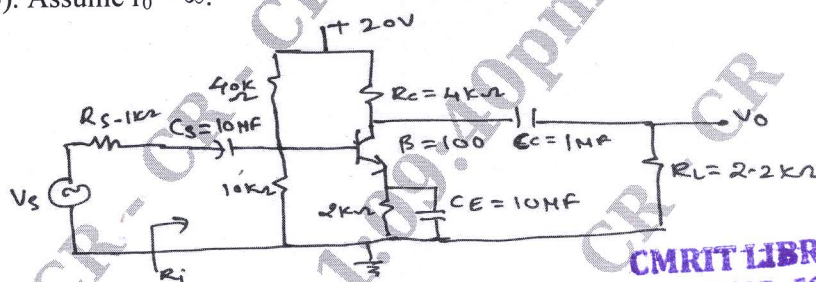


Fig.Q.6(b)

CMRIT LIBRARY
BANGALORE - 560 037

- c. Draw the circuit diagram of high frequency response of BJT amplifier under CE mode with capacitances. (04 Marks)

Module-4

- 7 a. List the conditions for sustained oscillations. (04 Marks)
- b. Determine the voltage gain, input impedance and output impedance with feedback for series voltage feedback having $A = -100$, $R_i = 10\text{k}\Omega$ and $R_o = 20\text{k}\Omega$ for feedback factor $\beta = -0.1$. (05 Marks)
- c. Explain with neat circuit diagram the operation of colpitt oscillator. (07 Marks)

OR

- 8 a. Show that gain with feedback in voltage series feedback system reduced by a factor $(1 + AB)$. (05 Marks)
- b. Explain the operation of FET RC phase oscillator with neat circuit diagram. (06 Marks)
- c. Design the RC elements of a Wein bridge oscillator for the operation at $f = 10\text{kHz}$ and draw the oscillator circuit diagram. (05 Marks)

Module-5

- 9 a. Define class A, class B, class C and class D power amplifiers. (04 Marks)
 b. Calculate the output voltage and the zener current for the regulator shown in Fig.Q9(b) for $R_L = 1K\Omega$. (04 Marks)

 


Fig.Q.9(b)

- c. Explain with neat diagram and waveforms class B push pull power amplifier. (08 Marks)

OR

- 10 a. Compare the series and shunt voltage regulators. (04 Marks)
 b. Define the following:
 i) Cross over distortion
 ii) Harmonic distortion
 iii) Percentage load regulation
 iv) Amplifiers efficiency (04 Marks)
 c. Calculate input power, output power and efficiency of the series fed class A power amplifier circuit shown in Fig.Q10(c). (08 Marks)

CMRIT LIBRARY
 BANGALORE - 560 037

 


Fig.Q.10(c)
