 


CBCS SCHEME



USN

--	--	--	--	--	--	--	--	--	--

15EC32

Third Semester B.E. Degree Examination, June/July 2019 Analog Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- Derive the expression for Z_{in} , Z_0 , A_v and A_I for voltage divider bias CE amplifier with R_E unbypassed using re-model. (10 Marks)
 - Write a note on hybrid π model. (06 Marks)

OR

- For a emitter bias circuit with $R_B = 470k\Omega$, $R_C = 3.3k\Omega$, $R_E = 1.2k\Omega$, $C_{C1} = C_{C2} = 0.1\mu F$, $h_{fe} = 120$, $h_{ie} = 1k\Omega$, $h_{oe} = 50\mu\Omega$. Find A_I , A_v , Z_{in} and Z_0 if R_E is unbypassed. Also write the hybrid model. (08 Marks)
 - Derive the expression for Z_{in} , Z_0 , A_v and A_I for common collector configuration amplifier using approximate hybrid model. (08 Marks)

Module-2

- Derive the expression for transconductance also relate I_D and g_m . (06 Marks)
 - Obtain the expression for Z_{in} and A_v for a JFET common gate amplifier. Write the small signal model. (10 Marks)

OR

- For a common drain configuration amplifier if $R_G = 2\mu\Omega$, $R_S = 2.2k\Omega$, $V_{DD} = 20V$, $C_{C1} = C_{C2} = 0.1\mu F$. Find Z_{in} , Z_0 and A_v given. $I_{DSS} = 10mA$, $V_p = -5V$, $r_d = 40k\Omega$, $V_{GSQ} = -2.85V$. (06 Marks)
 - With a neat diagram, explain the construction and operation of D-MOSFET and E-MOSFET. Also write the drain and transfer characteristics. (10 Marks)

Module-3

- State Miller's theorem and also obtain the expression for input and output capacitances. (08 Marks)
 - Derive the expressions for low frequency response of BJT amplifier due to input and output coupling capacitors and also due to bypass capacitor. (08 Marks)

OR

- 6 a. Determine the higher frequency response of the amplifier circuit shown in Fig.Q6(a) below, also plot the graph.

 


Fig.Q6(a)

- b. Given $V_{GS} = -8V$, $I_{GSS} = 80mA$, $g_m = 6ms$, $C_{gs} = 4pF$, $C_{gd} = 2pF$. (08 Marks)
 Obtain the expression for overall lower and upper cutoff frequency of multistage amplifier. (08 Marks)

Module-4

- 7 a. Prove that input and output impedances in voltage shunt feedback amplifier decreases. (06 marks)
 b. With the help of neat block diagram, deduce the conditions for sustained oscillations. (04 marks)
 c. Explain the important advantages of negative feedback. (06 marks)

OR

- 8 a. For a Wein bridge oscillator, if $R_1 = 1k\Omega$ and $R_F = 2.5k\Omega$. Find frequency of oscillation for $R = 2k\Omega$ and $C = 10mF$. Is oscillations sustained? (04 Marks)
 b. Derive the expression for frequency of oscillation in Hartley oscillator with the help of neat circuit diagram. (06 Marks)
 c. Explain the construction and operation of UJT. (06 Marks)

Module-5

- 9 a. Explain push pull amplifier with a neat circuit diagram. Show that its maximum conversion efficiency is 78.5%. (12 Marks)
 b. Write a note on class C amplifiers. (04 Marks)

OR

- 10 a. Explain services and shunt voltage regulator. (10 marks)
 b. For the circuit shown in Fig.Q10(b) below, if peak base current is 1mA. Calculate : (06 Marks)
 i) $P_{0(ac)}$ ii) $P_{in(dc)}$ iii) $\eta(\%)$.

 


Fig.Q10(b)
