

--	--	--	--	--	--	--	--	--	--

First/Second Semester B.E. Degree Examination, Dec.2017/Jan.2018
Basic Electronics

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting ONE full question from each module.

Module - 1

- 1 a. Explain the operation of a full wave rectifier using centre tap transformer with the help of a circuit diagram and relevant waveforms. Show that its maximum efficiency is 81.2%. (10 Marks)
- b. Draw the common emitter circuit of a transistor and sketch the input and output characteristics. Explain the different regions of operation by indicating them on the characteristic curve. (07 Marks)
- c. Calculate I_C , I_E and β in a common emitter transistor circuit that has $\alpha = 0.98$ and $I_B = 100 \mu A$. (03 Marks)
- 2 a. With appropriate circuit diagram, explain the DC load line analysis of a semiconductor diode. (05 Marks)
- b. Explain the working of a negative clamper circuit. (05 Marks)
- c. A transformer with 10 : 1 turns ratio is connected to a halfwave rectifier with supply voltage of $220\sin 210t$. If load and forward resistances are 500Ω and 10Ω respectively, calculate the average output voltage, dc output power, ac input power, rectification efficiency and peak inverse voltage. (05 Marks)
- d. With neat circuit diagrams, explain zener voltage regulator with load and no load. (05 Marks)

Module - 2

- 3 a. In a voltage divider bias circuit, $V_{CC} = 24V$, $R_1 = 180 K\Omega$, $R_2 = 56 K\Omega$, $R_E = 4.7 K\Omega$ and $R_C = 8.2 K\Omega$. Calculate the approximate levels of I_C , V_E , V_C and V_{CE} . (05 Marks)
- b. Explain how an opamp can be used as a, (i) Voltage follower, (ii) Integrator (iii) Differentiator and (iv) Summing amplifier. (10 Marks)
- c. Design an inverting and non inverting operational amplifier to have a gain of 15. (05 Marks)
- 4 a. What is an operational amplifier? List the ideal characteristics of an opamp. (06 Marks)
- b. The base bias circuit has $R_B = 470 K\Omega$, $R_C = 2.2 K\Omega$, $V_{CC} = 18 V$ and if the transistor has $\beta = 100$. Determine I_B , I_C and V_{CE} . (06 Marks)
- c. Design an adder circuit using an opamp to obtain an output voltage of, $V_o = -[2V_1 + 3V_2 + 5V_3]$ (05 Marks)
- d. Explain slew rate and CMRR of an opamp. (03 Marks)

Module - 3

- 5 a. Realize a two input exclusive NOR gate using only NAND gates, indicating the output at each of the gate. (04 Marks)
- b. Realize a Full adder using two half adders and an OR gate. Write the truth table and expressions for sum and carry outputs. (08 Marks)
- c. State and prove DeMorgan's theorem. (04 Marks)
- d. Simplify the Boolean expression, $\overline{xy + xyz} + x(y + xy)$. (04 Marks)

- 6 a. Subtract $(1111.101)_2$ from $(1001.101)_2$ using 1's and 2's complement method. (04 Marks)
- b. Convert (i) $(2AD.E3)_{16}$ to its octal and decimal equivalents. (04 Marks)
- (ii) $(1456.72)_8$ to its decimal and Hexadecimal equivalents. (06 Marks)
- c. Explain the 'OR' and 'AND' operation using diodes. (06 Marks)
- d. Simplify and realize the expression using Basic gates.
 $Y = \overline{AB} + \overline{AC} + \overline{ABC} + (AB + C)$ (06 Marks)

Module - 4

- 7 a. What is a flip flop? With the help of a logic diagram and truth table, explain the working of a clocked SR flip flop. (06 Marks)
- b. What is a transducer? Explain the working of LVDT. (05 Marks)
- c. What is a microprocessor? With a neat block diagram, explain the architecture of 8085 microprocessor. (09 Marks)
- 8 a. What is a Latch? With the help of a logic diagram and truth table, explain the working of a NAND gate latch. (06 Marks)
- b. List the differences between microprocessors and microcontrollers. (04 Marks)
- c. Write a short note on:
 (i) Resistance thermometer and
 (ii) Thermistor. (10 Marks)

CMRIT LIBRARY
BANGALORE - 560 037

Module - 5

- 9 a. What are the commonly used frequency ranges in communication systems? Mention the applications of each range. (04 Marks)
- b. Define amplitude modulation. Draw the AM signal and its spectrum. For an amplitude modulated wave, prove that total power is given by, $P_t = P_c \left[1 + \frac{\mu^2}{2} \right]$, where μ is the modulation index. (06 Marks)
- c. What is ISDN? Explain the services of ISDN. (05 Marks)
- d. With a neat block diagram, explain the optical fibre communication system. (05 Marks)
- 10 a. With a block diagram, explain typical cellular mobile radio unit. (05 Marks)
- b. What are the advantages of optical fibre communication? (05 Marks)
- c. Compare AM and FM modulation schemes. (04 Marks)
- d. An audio signal frequency signal $5 \sin 2\pi(1000)t$ is used to amplitude modulate a carrier of $100 \sin 2\pi(1.0^6)t$. Assume modulation index of 0.4. Find (06 Marks)
- (i) Sideband frequencies.
 (ii) Band width required.
 (iii) Amplitude of each side band
 (iv) Total power delivered to a load of 100Ω

* * * * *