

First/Second Semester B.E. Degree Examination, Dec.2016/Jan.2017
Basic electrical Engineering

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

1 a. Choose the correct answers for the following : (04 Marks)

- i) Which of the following does not represent the power
 A) VI B) V/I C) I^2R D) J/sec
- ii) The potential difference between A and B in Fig. Q1(a)(ii) is

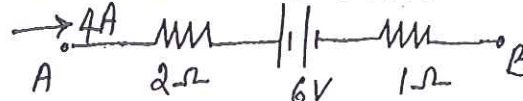


Fig. Q1(a)(ii)

- A) 18V B) -18V C) 4V D) -4V
- iii) When two identical inductors are connected in series aiding, the effective inductance is
 A) $L_1 + L_2 + 2m$ B) $L_1 + L_2 - 2M$ C) $2L_1 + 2L_2 + M$ D) $2L_1 + 2L_2 - 2M$
- iv) The coupling between two magnetically coupled coils is said to be ideal if the coefficient of coupling is

- A) 0 B) 0.25 C) 0.5 D) 1.

b. Obtain the potential difference V_{xy} in the circuit of Fig. Q1(b). (05 Marks)

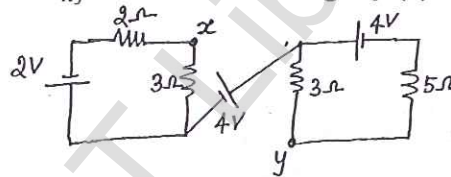


Fig. Q1(b)

c. Define coefficient of coupling and find its relation with L_1 , L_2 and M . (06 Marks)

d. A coil consists of 600 turns and current of 10 A in the coil gives rise to a magnetic flux of 1 milli weber. Calculate : i) the self inductance ii) the energy stored iii) the self induced emf when current is reversed in 0.01 second. (05 Marks)

2 a. Choose the correct answers for the following : (04 Marks)

- i) The time period of a sinusoidal waveform with frequency 200 Hz is
 A) 0.05 sec B) 0.005 sec C) 0.00055 sec D) 0.5 sec
- ii) The rms value of an AC sinusoidal current is 10A it's peak value is
 A) 7.07 A B) 14.14A C) 10A D) 28.28A
- iii) The power factor of a series RL circuit is given by
 A) $\frac{X_L}{R}$ B) $\frac{R}{X_L}$ C) $\frac{R}{Z}$ D) $\frac{Z}{R}$

iv) In a series RLC circuit, the inductive reactance is 10Ω and capacitive reactance is 15Ω . Then the total reactance is

- A) 25Ω B) 18.03Ω C) 5Ω D) 1.5Ω .

b. Derive average value of sinusoidal voltage interms of its maximum value. (04 Marks)

c. Prove that current in a purely inductive circuit lags behind the applied voltage by 90° . (06 Marks)

d. A circuit consists of resistance 10Ω an inductance 16 mH and a capacitance of $150 \mu\text{F}$ connected in series. A supply of 100V , 50 Hz is given to the circuit. Find the current and power consumed by the circuit. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 3 a. Choose the correct answers for the following : (04 Marks)
- The frequencies of 3 phase voltage in a three phase balanced system are
A) different B) same C) zero D) infinity
 - Electrical displacement between different phases in a six phase system is
A) 60° B) 120° C) 240° D) none of these
 - A balanced star connected load of $(8 + j6)\Omega$ per phase is connected to a 3 phase 440V supply. The line current is
A) 254.03A B) 25.403A C) 103.3A D) 33.33A
 - Two wattmeters connected in a balanced system indicates 4.5 KW, -0.5 KW. The power factor of the circuit is
A) 0.4193 B) 0.707 C) unity D) 0.963.
- b. Obtain the relationship between the phase and line values of voltages and currents in a balanced star connected system. (08 Marks)
- c. Three similar coils each having resistance 10Ω and reactance 10Ω are connected in star across 440V, 3-phase supply. Find line current and reading of each two wattmeters connected to measure power. (08 Marks)
- 4 a. Choose the correct answers for the following : (04 Marks)
- The electric energy meter installed near the mains switch in a house is
A) an indicating instrument B) an integrating instrument
C) a recording instrument D) an absolute instrument
 - The damping force in an instrument to
A) oppose the deflecting force B) oppose the controlling force
C) bring the pointer to steady position quickly D) none of these
 - A good earthing should provide _____ resistance in earth path
A) low B) high C) medium D) none of these
 - The ratio fusing current to rated current is known as
A) fuse current ratio B) fuse rated capacity C) fusing factor D) none of these.
- b. Explain two-way control of a lamp. (04 Marks)
- c. Explain the principle of operation of dynamometer type wattmeter. (06 Marks)
- d. Explain with a neat diagram pipe earthing. (06 Marks)

PART – B

- 5 a. Choose the correct answers for the following : (04 Marks)
- The back emf in a DC motor is given as
A) $V + I_a R_a$ B) $V - I_a R_a$ C) V D) $I_a R_a$
 - The emf generated by a DC generator depends upon
A) the flux only ;B) the speed only;C) both the flux and speed ;D) the terminal voltage
 - At the moment of starting a DC motor, its back emf is
A) zero B) maximum C) minimum D) optimum
 - The function of a starter in a DC motor is to
A) control its speed B) increase its starting torque
C) limit the starting current to safer value D) reduce armature reaction.
- b. Mention the classification of DC generator. (04 Marks)
- c. A shunt wound DC generator delivers 496A at 440V to a load. The resistance of the shunt field coil is 110Ω and that of the armature winding is 0.02Ω . Calculate the emf induced in the armature. (04 Marks)
- d. An 8-pole DC generator has 500 conductors on its armature and produces 0.02Wb of flux per pole.
- What voltage will it generate at a speed of 1800 rpm if armature is a) lap wound and b) if armature is wave wound?
 - If the allowable current is 5A per path, what KW power generated by the machine when a) lap wound b) wave wound. (08 Marks)

- 6 a. Choose the correct answers for the following :
- The eddy current loss in a transformer is minimized by using
A) solid core B) laminated core C) plastic core D) none of these
 - If an ammeter in the secondary of a 100V/10V transformer reads 10A, the current in the primary would be
A) 1A B) 2A C) 10A D) 100A
 - Efficiency of a transformer is maximum when
A) copper loss = $\sqrt{\text{core loss}}$ B) core loss = $\sqrt{\text{copper loss}}$
C) copper loss = core loss D) none of these
 - Losses which do not occur in a transformer is
A) copper losses B) magnetic losses C) friction losses D) none of these.
- b. Explain briefly the principle of operation of a transformer and show that the voltage ratio of primary and secondary windings is the same as their turns ratio. (04 Marks)
- c. Derive the condition for maximum efficiency in a single-phase transformer. (04 Marks)
- d. In a 25 KVA, 2000/200V transformer, the iron and copper losses are 350 watts and 400 watts respectively, calculate the efficiency at UPF at half full load. (08 Marks)
- 7 a. Choose the correct answers for the following : (04 Marks)
- A 6 pole 1000 rpm alternator generates emf at a frequency of
A) 60 Hz B) 40 Hz C) 25 Hz D) 50 Hz
 - A smooth cylindrical type rotor is used for alternator having
A) low speed B) low and medium speed C) high speed D) none of these
 - Frequency of supply in India is
A) 60 Hz B) 25 Hz C) 50 HZ D) 75 Hz
 - The frequency of emf generated by an alternator depends upon the alternator speed N and number of poles P is given by
A) $\frac{PN}{60}$ B) $\frac{60N}{P}$ C) $\frac{PN}{120}$ D) $\frac{120N}{P}$
- b. Obtain expression for emf of an alternator. (06 Marks)
- c. What are the advantages of stationary armature? (04 Marks)
- d. A 3 phase 50 Hz 16 pole alternator with star connected windings has 144 slots with 10 conductors/slot. The flux per pole is 24.8 mwb. The coils are full pitched and assume $k_d = 0.96$; find : i) speed ii) the line emf. (06 Marks)
- 8 a. Choose the correct answers for the following : (04 Marks)
- An induction motor works with
A) DC only B) AC only C) both AC and DC D) none of these
 - A 3-phase 50Hz 6-pole induction motor has a full load slip of 3%, the synchronous speed is
A) 2000 rpm B) 1000 rpm C) 100 rpm D) 10 rpm
 - Speed of an induction motor is _____ that of N_s
A) greater than B) less than C) same as D) double
 - The frequency of rotor induced current is given by
A) $f' = f/s$ B) $f' = sf$ C) $f' = \sqrt{sf}$ D) $f' = 1 - s$.
- b. What is slip in an induction motor? Why slip is never zero in an induction motor. (04 Marks)
- c. Derive an expression for frequency of rotor induced emf interms of slip of induction motor. (06 Marks)
- d. If a 6-pole induction motor supplied from a 3-phase 50 Hz supply has a rotor frequency of 2.3 Hz. Calculate: i) the percentage slip ii) speed of the rotor. (06 Marks)