

**Fifth Semester B.E. Degree Examination, Dec.2016/Jan.2017**  
**Linear IC's & Applications**

Time: 3 hrs.

Max. Marks:100

- Note: 1. Answer FIVE full questions, selecting at least TWO questions from each part.**  
**2. Data sheets of typical standard Resistor, Capacitor values permitted.**

**PART – A**

- 1 a. Sketch the circuit of high zin capacitor coupled voltage follower and derive an expression for input impedance. (08 Marks)
- b. Design a capacitor coupled voltage follower using 741 op-amp, the lower cut-off frequency for the circuit is to be 50 Hz with  $R_L = 3.9 \text{ k}\Omega$  (06 Marks)
- c. Sketch the circuit of capacitor coupled non-inverting amplifier using single polarity supply and explain briefly. (06 Marks)
- 2 a. What is frequency compensation? With the help of circuit and its response, explain phase lag and phase lead compensation. (12 Marks)
- b. List the circuit stability precautions. (08 Marks)
- 3 a. Sketch the circuit of precision full wave rectifier with half wave rectifier and summing circuit with waveform and explain its operation with waveforms. (08 Marks)
- b. Design a precision full wave rectifier circuit to produce 2 V peak output from a sine wave input with a peak value of 0.5 V and with a frequency of 1 MHz. Use bipolar op-amp with a supply of  $\pm 15 \text{ V}$ . (06 Marks)
- c. With the help of neat sketch and waveform, explain diode clamping circuit. (06 Marks)
- 4 a. Sketch the circuit of capacitor coupled crossing detectors, draw its waveforms and explain its operation. (08 Marks)
- b. Sketch the circuit of inverting Schmitt Trigger circuit and explain its operation with necessary waveforms. (06 Marks)
- c. Using BIFET op-amp, design astable multivibrator to have  $\pm 9 \text{ V}$  output with a frequency of 1 kHz. (06 Marks)

**PART – B**

- 5 a. Sketch the circuit of triangular / rectangular wave generator. Explain its operation with necessary waveform. (10 Marks)
- b. Sketch the circuit of Weinbridge oscillator and explain its operation with necessary waveforms. (05 Marks)
- c. Using BIFET op-amp with a supply of  $\pm 12 \text{ V}$ , design a wein bridge oscillator to have output frequency of 15 kHz. (05 Marks)
- 6 a. Sketch the circuit of I<sup>st</sup> order low pass filter and explain its operation with necessary waveform. (08 Marks)
- b. Using a 741, design a I<sup>st</sup> order active low pass filter to have cut-off frequency of 1 kHz. (06 Marks)
- c. Design a II<sup>nd</sup> order LPF circuit to have cut-off frequency of 1 kHz. (06 Marks)
- 7 a. With the help of block diagram, explain phase locked loops. (08 Marks)
- b. Briefly explain the operation of switched capacitor filter. (08 Marks)
- c. Write a note on power amplifier. (04 Marks)
- 8 a. With the help of circuit, explain the operation of the adjustable output regulator. (10 Marks)
- b. With the help of circuit diagram, explain the previous voltage regulator. (10 Marks)

\* \* \* \* \*

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.