

**Sixth Semester B.E. Degree Examination, Dec.2016/Jan.2017**  
**Power System Analysis & Stability**

Time: 3 hrs.

Max. Marks:100

**Note: 1. Answer any FIVE full questions, selecting atleast TWO questions from each part.**  
**2. Assume missing data, if any suitably.**

**PART - A**

- 1 a. What is per unit quantity? Mention the advantages of per unit quantities. (06 Marks)  
 b. What is single line diagram? Explain how to obtain impedance and reactance diagrams from single line diagram of a power system. (06 Marks)  
 c. Draw a per unit reactance diagram for the power system shown in Fig.Q1(c).

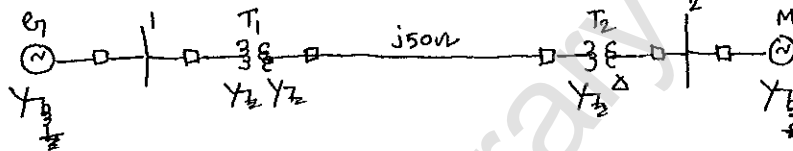


Fig.Q1(c)

Use a base of 100 MVA, 220 kV in 50Ω line.

The ratings of the generator, motor and transformers are

Generator : 40 MVA, 25 kV,  $X'' = 20\%$

Motor : 50 MVA, 11 kV,  $X'' = 30\%$

Y - Y Transformer : 40 MVA, 33Y / 220Y kV,  $X = 15\%$

Y - Δ Transformer : 30 MVA, 11Δ / 220Y kV,  $X = 15\%$

(08 Marks)

- 2 a. Discuss the different types of faults in Power system. (04 Marks)  
 b. Explain clearly, how circuit breakers are rated? (08 Marks)  
 c. A generator is connected to a synchronous motor through transformer. Reduced to a common base, the per unit subtransient reactances of generator and motor are 0.15 and 0.35 pu respectively. The leakage reactance of the transformer is 0.1 pu. A 3φ short circuit fault occurs at terminals of the motor when terminal voltage of generator is 0.9 pu and output current of generator is 1 pu at 0.8 p.f. leading. Find the subtransient current in the fault, generator and motor. (08 Marks)
- 3 a. What are symmetrical components? How they are useful in solution of power system? (04 Marks)  
 b. Derive an expression for the 3φ complex power in terms of symmetrical components. (08 Marks)  
 c. A delta connected balanced resistive load is connected across a balanced 3φ supply as shown in Fig.Q3(c). With currents in lines A & B specified. Find the symmetrical components of the currents. (08 Marks)

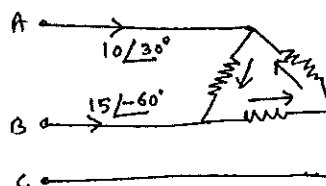


Fig.Q3(c)

- 4 a. With the help of relevant vector diagrams for voltages and currents establish the phase-shift of symmetrical components in Y- $\Delta$  transformer. (12 Marks)
- b. What are sequence impedances and sequence network? Draw the zero sequence networks for different combinations of 3 $\phi$  transformer bank. (08 Marks)

**PART – B**

- 5 a. Mention the different types of faults occurring in electrical power system and their probability of occurrence. (04 Marks)
- b. A double line to ground fault occurs at the terminals of an unloaded generator. Derive an expression for the fault currents. Also draw connection of sequence networks. (10 Marks)
- c. Discuss briefly about the open-conductor faults in power system. (06 Marks)
- 6 A single line to ground fault occurs at mid point F of transmission line in power system shown in Fig.Q6(a). Determine the fault current in pu and in amperes from generator if the system were on no load and at a voltage of 100 kV at the fault point.



Fig.Q6(a)

The ratings are

Generator : 11.5 kV, 500 MVA,  $X_1 = 0.3$  pu,  $X_2 = 0.2$  pu,  $X_0 = 0.1$  pu

Transformer –  $T_1$  : 11/110 kV, 45 MVA,  $X = 0.1$  pu

Transformer –  $T_2$  : Consists of 3 single phase units each rated  
20 MVA, 66/6.6 kV,  $X = 10\%$

Motor : 6 kV, 55 MVA,  $X_1 = 0.4$  pu,  $X_2 = 0.3$  pu,  $X_0 = 0.2$  pu

Line :  $X_1 = X_2 = 48.5 \Omega$ ,  $X_0 = 90 \Omega$

Choose a base of 60 MVA, 110 kV in transmission line. (20 Marks)

- 7 a. Differentiate between steady state and transient state stability of a power system. Can these stability limits have multiple values? (06 Marks)
- b. Derive swing equation with usual notation. (08 Marks)
- c. Explain the equal area criterion for investigating the stability of power system. (06 Marks)
- 8 a. An ac generator is delivering 50% of maximum power to an infinite bus. Due to a sudden short circuit, the reactance between generator and infinite bus increases to 500% of the value before fault. The maximum power that can be delivered after clearance of the fault is 75% of the original value. Calculate the critical clearing angle to maintain the stability of the system. (08 Marks)
- b. Explain the analysis of 3 $\phi$  induction motor with one line open. (06 Marks)
- c. Explain the analysis of 3 $\phi$  induction motor with unbalanced voltage. (06 Marks)

\* \* \* \* \*