

Fourth Semester B.E. Degree Examination, Dec.2016/Jan.2017
Fundamentals of HDL

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1
 - a. Explain composite VHDL and verilog data types. (08 Marks)
 - b. If A, B and C are the unsigned variables with A = "110011", B = "010100", C = "101". Find the values of
 - (i) $Y = \&A$ (ii) $Y = A \&\& B$ (iii) $Y = A \text{ sra } 2$
 - (iv) $Y = B \text{ rol } 2$ (v) $Y = A \ll 2$ (vi) $Y = A \text{ and not } B \text{ xor } 2 \text{ nand } C$ (07 Marks)
 - c. Write the major differences between VHDL and verilog. (05 Marks)
- 2
 - a. Write a VHDL program in data flow style using signal assignment statements to implement a 2 to 1 multiplexer with active low enable signal (Ebar). If the propagation delay of each gate is 9 ns, calculate at what time the output is available when the input signals (A, B, select, Ebar) are changed at T_0 , T_1 and T_2 as shown in Fig.Q2(a). (07 Marks)

 


Fig.Q2(a)

- b. Write a VHDL program to realize a D-latch in Data flow style, Consider enable signal as active low. (06 Marks)
 - c. Write a verilog program to implement a 3-bit carry-look ahead adder in data flow style. (07 Marks)
- 3
 - a. Compare signal and variable assignment statement. (05 Marks)
 - b. Write a verilog code to implement a positive edge triggered JK flip flop shown in Fig.Q3(b) in behavioural style using (i) else if and (ii) case statement. (08 Marks)

 


Fig.Q3(b)

- c. Write the flow chart of Booth multiplication algorithm. Show the steps to find the product of two signed 5-bit numbers -5 and 9. (07 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 4 a. Write a VHDL program to realize the block diagram shown in Fig.Q4(a) in structural style (No need to show the implementation of components). (07 Marks)

 


Fig.Q4(a)

- b. Write a verilog program to implement a 4-bit magnitude comparator using 4-bit adders in structural style. (07 Marks)
- c. Explain the following keywords (i) Generate (ii) Generic and (iii) Parameter. (06 Marks)

PART - B

- 5 a. Explain procedure with syntax and example in VHDL. (06 Marks)
- b. Write a verilog program to convert an unsigned binary to an integer using task. (08 Marks)
- c. Write a VHDL function to find the greater of two signed numbers. (06 Marks)
- 6 a. When mixed type description is preferred? Give example. (06 Marks)
- b. Explain different VHDL user defined types. (06 Marks)
- c. Write a verilog description of a 32x8 SRAM to implement the function table shown in Table 6(c).

CS	R/ \overline{WR}	Memory Function
0	X	Deselected
1	1	Read cycle
1	0	Write cycle

Table 6(c)

- 7 a. Explain how to invoke a VHDL entity from a verilog module. (08 Marks)
- b. Write the block diagram of a 9-bit adder and implement it by mixed language description. (12 Marks)
- 8 a. What is synthesis? With a neat flow chart explain the steps involved in a synthesis process. (10 Marks)
- b. Find the gate-level mapping for the verilog code given below:

```

module if_st(a, y)
input[2:0] a;
output y;
reg y;
always (a)
begin
    if (a < 3' b 1 0 1)
        y = 1' b 1;
    else
        y = 1' b 0;
    end
end module

```

(10 Marks)