

Fifth Semester B.E. Degree Examination, June/July 2016

Fundamentals of CMOS VLSI



Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1
 - a. Discuss latch-up in a p-well CMOS structure and its remedies. With neat figure explain twin tub CMOS process steps. (10 Marks)
 - b. For an NMOSFET, the following details are available $\mu_n = 500\text{cm}^2/\text{V}\cdot\text{se}$, $(V_a - V_{tn}) = 2.6\text{V}$, $t_{\text{ox}} = 100 \text{ \AA}$. Calculate R_n of the device if $w = 100\mu\text{m}$, $L = 0.5\mu\text{m}$. (05 Marks)
 - c. Deduce an equation for figure of merit of MOS transistor. Find the operating frequency f_o in the following condition $\mu_n = 125\text{cm}^2/\text{v}\cdot\text{sec}$, $L = 2\mu\text{m}$, $V_{\text{gs}} = 2\text{V}$ and $\mu_{\text{tn}} = 1\text{V}$. (05 Marks)
- 2
 - a. What are the uses of stick diagram? Give the table of color and monochrome stick encoding for simple single metal NMOS process. (07 Marks)
 - b. Draw the CMOS circuit diagram, stick diagram and symbolic diagram of Boolean function $F = wx + yz$. (06 Marks)
 - c. What do you mean by λ based design rule? Explain λ based design rules applicable to MOS layers and transistors. (07 Marks)
- 3
 - a. With neat circuit diagram explain the following : (i) A simple BiCMOS inverter and (ii) An improved BiCMOS inverter with no static current flow and better output logic levels. (10 Marks)
 - b. Draw and explain the basic structure of dynamic CMOS logic and discuss the charging sharing problem in this structure. (10 Marks)
- 4
 - a. What are the most commonly used scaling models? Provide scaling factors for (i) power dissipation per gate (ii) Gate delay (iii) current density and (iv) speed power product. (10 Marks)
 - b. For the given multilayer structure shown in Fig. Q4(b) calculate the total capacitance. (10 Marks)

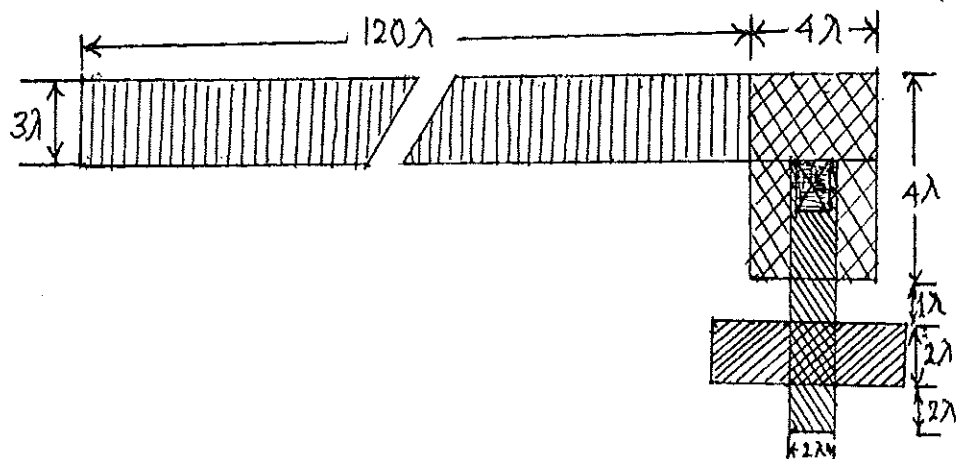


Fig. Q4(b)

PART – B

- 5 a. Obtain switch logic arrangements for (i) $V_{out} = V_1A + V_2B + V_3C$ using 3 way selector switch and (ii) 3 input nMOS OR gate. (10 Marks)
- b. Draw and explain 4 : 1 MUX using transmission gate. (05 Marks)
- c. Explain with neat figure, non – inverting dynamic storage cells using CMOS transmission gate switch. (05 Marks)
- 6 a. With the help of logic expressions explain how to implement arithmetic logic operations with a standard adder. (10 Marks)
- b. Explain with neat diagram the 4×4 cross bar switch. (10 Marks)
- 7 a. With neat figure explain transistor dynamic RAM cell. (06 Marks)
- b. Describe the CMOS pseudo static memory cell with neat figure. (06 Marks)
- c. Explain read and write operations in dynamic memory cell. (08 Marks)
- 8 Write short notes on :
- a. Input/output pads (05 Marks)
- b. Test and Testability. (05 Marks)
- c. Level sensitive scan design and (05 Marks)
- d. Built in self test (BIST). (05 Marks)

* * * * *