

--	--	--	--	--	--	--	--	--	--

## Fifth Semester B.E. Degree Examination, June/July 2016

### Linear ICs and Applications



Max. Marks:100

- Note:** 1. Answer FIVE full questions, selecting at least TWO questions from each part.  
 2. Missing data may be suitably assumed.  
 3. Use of resistor, capacitor standard values list, op-amp data sheets is permitted.

#### PART – A

- 1
  - a. Explain the working of a high input impedance capacitor coupled voltage follower circuit, with a neat circuit diagram. (08 Marks)
  - b. Design and explain the operation of a single polarity non-inverting amplifier, with a neat sketch. (08 Marks)
  - c. A capacitor coupled inverting amplifier has the following components:  $R_1 = 2.7K\Omega$ ,  $R_2 = 100k\Omega$ ,  $R_L = 1.5 k\Omega$ ,  $c_1 = 3.9 \mu F$ ,  $c_2 = 0.68 \mu F$ . Determine the circuit voltage gain input impedance, lower cut off frequency and the impedance of  $c_1$  at  $f_1$ . (04 Marks)
  
- 2
  - a. Explain in detail about the phases lag and phase lead frequency compensation method, analog with the circuit and frequency response curves. (10 Marks)
  - b. Discuss the effect of slew rate on bandwidth and output impedance. (08 Marks)
  - c. Calculate the slew rate limited cutoff frequency for a voltage follower circuit using a 741 op-amp if the peak of sine wave output is to be 5V? (02 Marks)
  
- 3
  - a. With a neat circuit diagram, show how a half wave precision rectifier can be combined with a summing circuit to produce a full wave precision rectifier. Draw the voltage wave forms at relevant stages of the circuit and write equations to show that full wave rectification is performed. (08 Marks)
  - b. Explain the operations of an adjustable peak clipper circuit with back – to – back connected zener diodes. (06 Marks)
  - c. Sketch and explain the working of op – amp sample – and hold circuit. (06 Marks)
  
- 4
  - a. With a neat circuit diagram and wave forms, explain the operation of inverting Schmitt trigger circuit with different LTP and UTP. (06 Marks)
  - b. Sketch the circuit of an op – amp astable multi – vibrator, show the voltage waveforms at various points in the circuit and explain its operation. (08 Marks)
  - c. Sketch the circuit of capacitor coupled crossing detector. Show the waveforms at various points in the circuit and explain its operation. (06 Marks)

#### PART – B

- 5
  - a. Draw the circuit of a triangular/rectangular waveform generator, which has frequency and duty cycle controls. Explain the circuit operation with relevant waveforms for a smaller duty cycle. (10 Marks)
  - b. Using a BIEET op-amp with a supply of  $\pm 12 V$ , design a Wein bridge oscillator to have an output frequency of 15kHz. (04 Marks)
  - c. Draw the circuit of an output stage for controlling the output amplitude and d.c. voltage level of a signal generator. Briefly explain its operation. (06 Marks)

- 6 a. Explain the following terms with a suitable diagram as applied to active filters :
- Figure of merit
  - Bandwidth
  - Centre frequency and
  - Narrow band and wide band. (06 Marks)
- b. Design a second-order high-pass active filter to have a cut-off frequency of 12kHz. Use a 715 op-amp and estimate the highest signal frequency that will be passed. (for 715 op-amp,  $I_{B(max)} = 1.5\mu A$  and  $f_a = 11MHz$ ). (08 Marks)
- c. Explain with a block diagram and response curve, how band stop filter can be obtained using low pass, high pass a summing circuit. (06 Marks)
- 7 a. What is an universal active filter? List the salient features of FLT – U2 specialized IC filter. (06 Marks)
- b. Explain the theory of operation of a switched capacitor filter. List out the advantages of switched capacitor filter. (08 Marks)
- c. With a block diagram, explain the operation of a phase locked loop. (06 Marks)
- 8 Write explanatory notes with relevant circuit diagrams and wave forms whenever applicable:
- Block diagram of a PLL. (06 Marks)
  - Power amplifier using general purpose – op – amp. (06 Marks)
  - Theory of operation of switched capacitor filter. (08 Marks)

\*\*\*\*\*