


(64)

CMR INSTITUTE OF TECHNOLOGY		USN <input type="text"/>					
Internal Assessment Test I – Sep 2018							
Sub:	POWER ELECTRONICS					Code:	15EE53
Date:	10/09/2018	Duration:	90 mins	Max Marks:	50	Sem:	<input checked="" type="checkbox"/> A & B
Note: Answer any <b>five FULL</b> Questions Sketch neat figures wherever necessary. Answer to the point. <b>Good luck!</b>							

		Marks	OBE	
			CO	RBT
1 (a)	With neat circuit diagram ,input and output waveforms, explain the different types of power electronic circuits	[8]	CO1	L2
(b)	Discuss the major industrial applications of power electronic converter circuits	[2]	CO1	L1
2 (a)	With the help of neat waveform, explain the reverse recovery characteristics of a power diode. And also obtain an expression for peak reverse current	[10]	CO1	L2
3 (a)	With neat circuit diagram and switching times explain steady state and switching characteristics of power MOSFET	[10]	CO2	L1
4 (a)	The reverse recovery time of a diode is $5\mu\text{s}$ and rate fall of diode current is $80\text{A}/\mu\text{s}$ Calculate i)the storage charge ii) peak reverse current	[4]	CO1	L2
(b)	The $\beta$ of BJT varies from 12 to 75. The load resistance is $1.5\Omega$ . the supply voltage $V_{cc} = 40\text{V}$ and base input voltage is $6\text{V}$ .If $V_{CEsat} = 1.2\text{V}$ , $V_{BEsat} = 1.6\text{V}$ and $R_B = 0.7\Omega$ . Calculate i) ODF ii) Forced $\beta$ iii) total power loss in transistor	[6]	CO2	L2

5 (a)	List and explain the switching limits of BJT	[5]	CO2	L1
(b)	Briefly explain different types of power diodes	[5]	CO1	L1
6 (a)	Discuss the transfer and output characteristics of BJT	[5]	CO1	L1
(b)	Compare power BJT with power MOSFET	[5]	CO2	L1
7	Derive the average and rms output voltage of a single phase full bridge rectifier with R load. Also draw the related output voltage and current waveforms	[10]	CO1	L2
8	Write short notes on the following , i) Ideal characteristics of a switch ii) Practical characteristics of a switch iii) Switch specifications	[10]	CO1	L2

## TYPES OF POWER ELECTRONIC DEVICES .

The power electronic circuits are classified in


six types

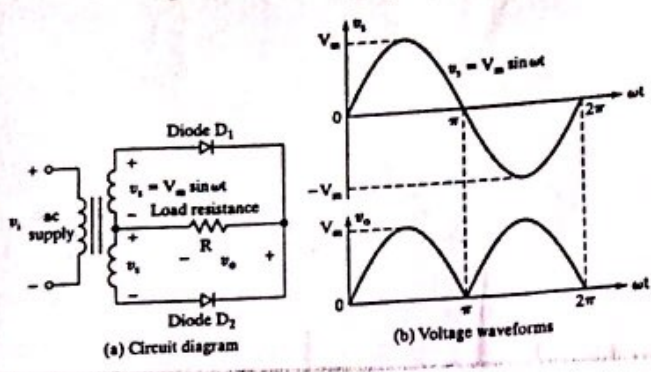1. Diode rectifiers
2. AC-DC converter / controlled rectifiers
3. AC-AC converters / ac voltage controllers
4. DC-DC converters / dc choppers
5. DC-AC converters / inverters
6. Static switches .


Diode Rectifier:

- converts ac voltage into fixed dc
- input could be either  $1\phi$  or  $3\phi$ .






 AC-DC Converter:- (controlled rectifiers)  
 The output voltage can be controlled by varying firing or triggering angle  $\alpha$ . A single phase converter with natural commutated thyristor is shown below.




 AC-AC Converters (ac voltage controllers)  
 Variable ac output voltage from fixed ac source.  
 A 1 $\phi$  converter with TRIAC is shown below.


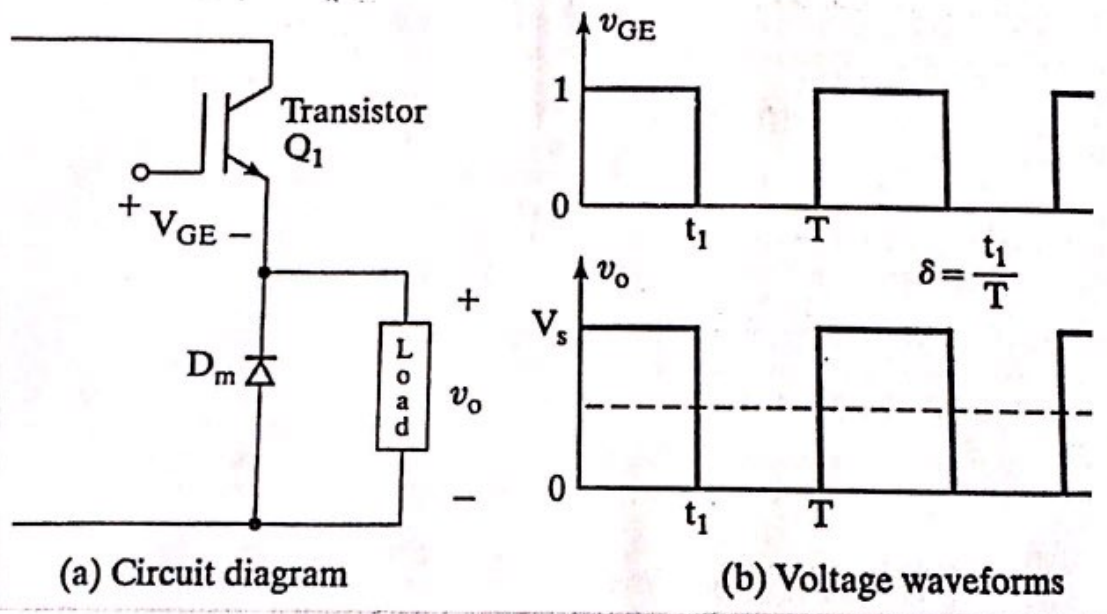
# DC-DC Converters (Chopper) (Switching Regulator)


To obtain variable dc voltage from fixed dc voltage. The average output voltage is controlled by varying the conduction time.



If  $T$  is chopping period,  $t_1 = \delta T$  where  $\delta$  is called duty cycle.
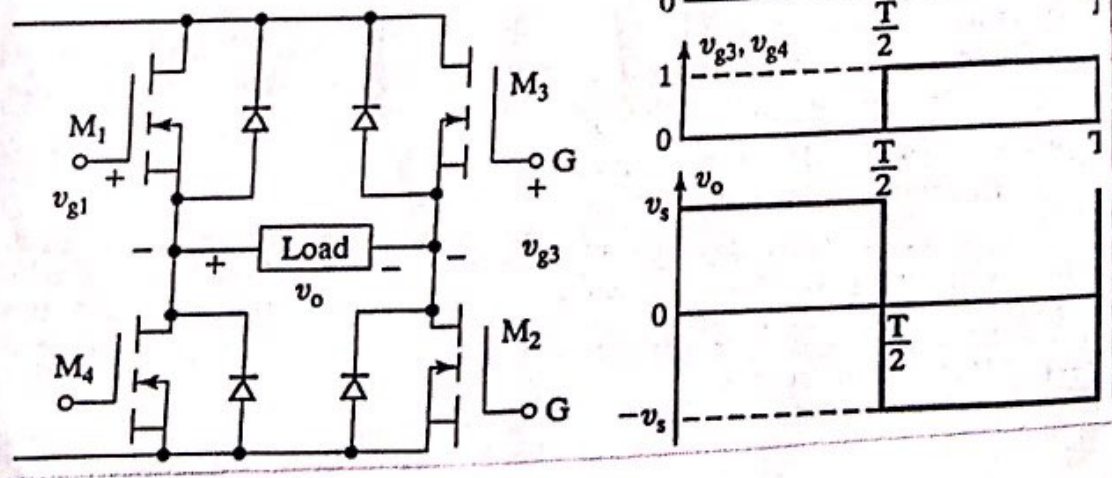
# DC-AC Converters (Inverter)

To obtain variable ac voltage from fixed dc voltage






Transistors  $M_1$  and  $M_2$  conduct for one half of a period and  $M_3$  &  $M_4$  conduct for other half. The c/p is varied by controlled the conduction time of thy transistors. (ii)

Static Switches:- (ac or dc static switches)

Power electronic devices used as static switches in an UPS is shown below.

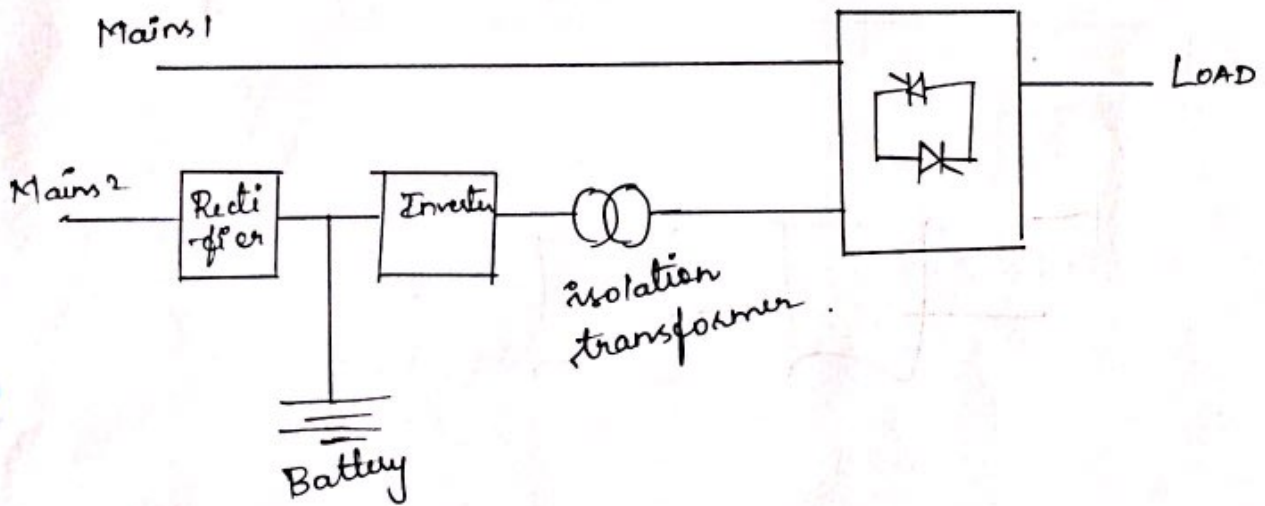Mains1 and mains2 are connected to same supply.




Power electronics - now used in a great variety of high - power products,

- \* heat controls
- \* light controls
- \* motor controls
- \* power supplies
- \* vehicle propulsion systems
- \* HVDC systems
- \* FACTS .
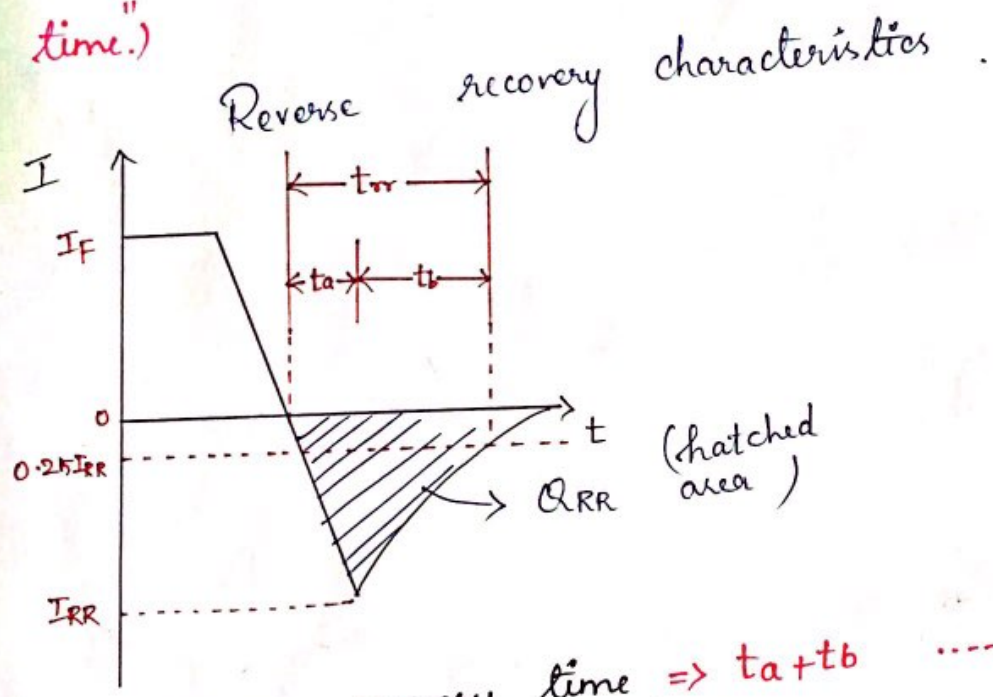
# REVERSE RECOVERY CHARACTERISTICS:

→ The current in diode is due to net effect of majority and minority carriers. Once the diode current is reduced to zero (application of reverse voltage), the diode continues to conduct due to minority carriers in junction and semiconductor material. This carriers require certain time to recombine and neutralize called "reverse recovery time."



- $t_{rr}$  - reverse recovery time  $\Rightarrow t_a + t_b$  ..... (1)
- measured from initial zero crossing of diode current to 25% of max reverse current  $I_{RR}$
- $t_a$  - due to charge stored in the depletion region of jxn.
- time b/w zero crossing and  $I_{RR}$
- $t_b$  - due to charge stored in the material
- $\frac{t_b}{t_a} \Rightarrow$  softness factor (S)
- if  $S \geq 1 \rightarrow$  soft recovery
- $S < 1 \rightarrow$  fast recovery



The peak reverse current is given by, (5)

$$I_{RR} = I_a \frac{di}{dt} \dots \dots (2)$$

Reverse recovery charge  $Q_{RR}$  - the amt of charge carriers that flows across the diode in reverse dir due to changeover from forward conduction to reverse blocking condition.

$$Q_{RR} \cong \frac{1}{2} I_{RR} t_a + \frac{1}{2} I_{RR} t_b$$

$$= \frac{1}{2} I_{RR} t_{rr}$$

(area - considering triangle =  $\frac{1}{2} \times l \times b$ )

$$I_{RR} \cong \frac{2Q_{RR}}{t_{rr}} \dots \dots (3)$$

using (2) and (3),

$$I_a \frac{di}{dt} = \frac{2Q_{RR}}{t_{rr}}$$

assume  $t_b \ll t_a$ , i.e.  $t_{rr} \cong t_a$

$$t_{rr} t_a = \frac{2Q_{RR}}{di/dt}$$

$$t_{rr}^2 = \frac{2Q_{RR}}{di/dt}$$

$$t_{rr} = \sqrt{\frac{2Q_{RR}}{di/dt}} \dots \dots (4)$$

using (3) and (4),

$$I_{RR} = \frac{2Q_{RR}}{t_{rr}} = \frac{2Q_{RR}}{\sqrt{\frac{2Q_{RR}}{di/dt}}}$$

## Steady state characteristics:-


↳ Mosfets are voltage controlled devices with very high input impedance and gate draws a very small leakage current in the order of nano-amperes.

↳ very high current gain  $\frac{I_D (o/p)}{I_{G1} (i/p)} \cong 10^9$



↳ However in case of MOSFETS, rather than current gain, there is an another important parameter called transconductance

$$\text{transconductance} = \frac{I_D}{V_{GS}} \left[ \frac{\text{drain current}}{\text{gate voltage}} \right]$$

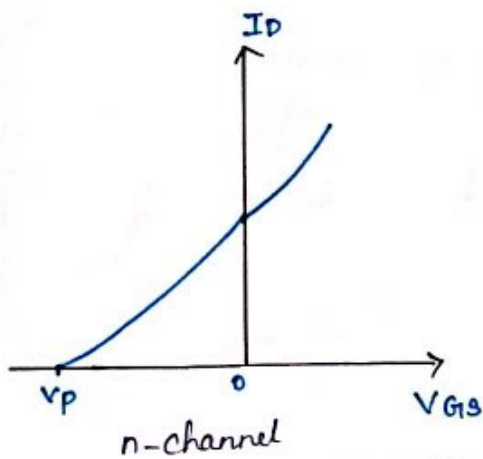
The transfer characteristics of n-channel and p-channel MOSFETS are shown below.




(i) depletion type MOSFET

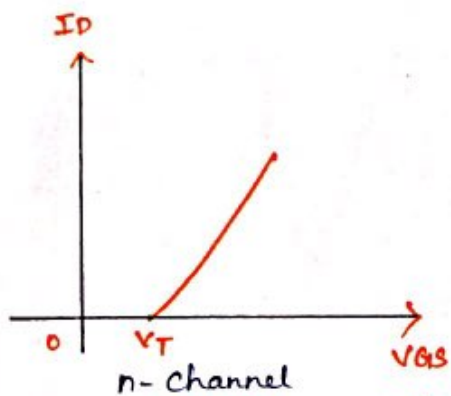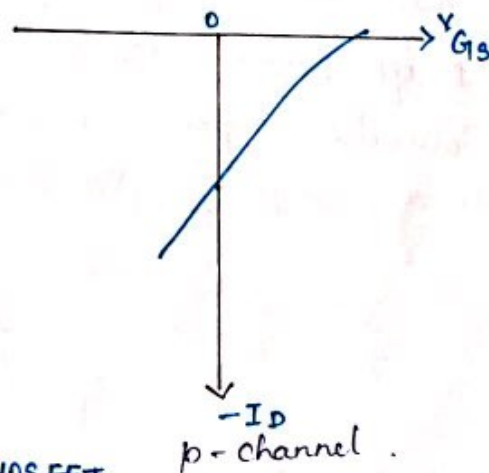

(ii) Enhancement type MOSFET

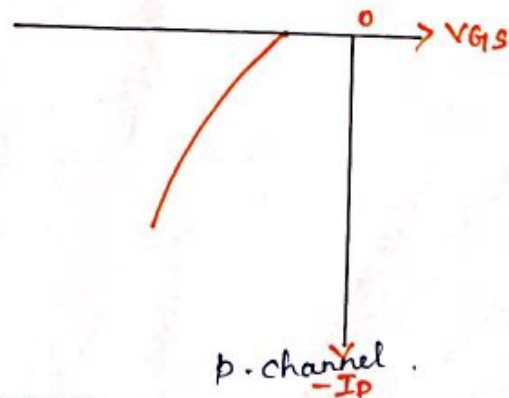

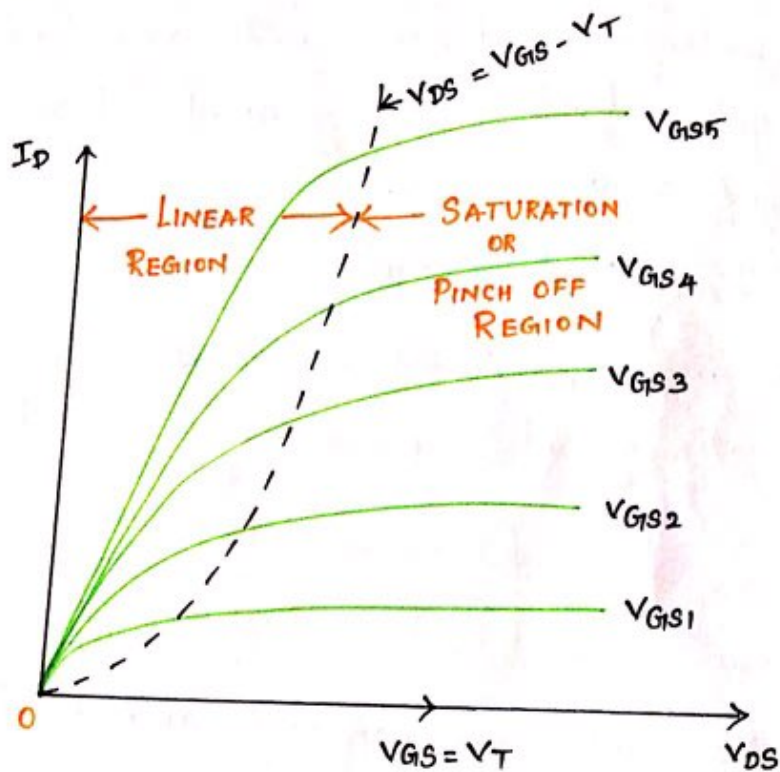Output characteristics:- (n-channel enhancement MOSFET)



$$V_{GS5} > V_{GS4} > V_{GS3} > V_{GS2} > V_{GS1} > V_T$$

the o/p characteristics  $I_D - V_{DS}$  is shown above.


There are three region of operation

1. cut off region  $V_{GS} \leq V_T$
2. Saturation region  $V_{DS} \geq V_{GS} - V_T$
3. Linear region  $V_{DS} \leq V_{GS} - V_T$ .



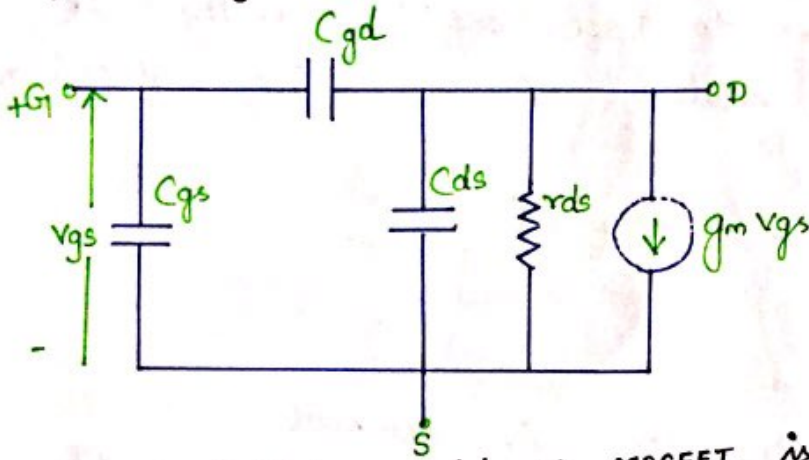
## SWITCHING CHARACTERISTICS:-

- \* The switching characteristics of MOSFET are influenced by internal capacitance of the device and internal impedance of the gate driver circuit.



 - \* The switching model of MOSFET is shown in figure



↳ When +ve gate voltage is applied, the device doesn't turn on instantly, it requires some time delay for the input capacitance to charge to gate threshold voltage  $V_{GS(T)}$ .

↳ This time delay is called as turn-on time delay ( $t_{dn}$ )

↳ There is a further delay called rise time  $t_r$  during which gate voltage rises to  $V_{GS(P)}$  (sufficient voltage to drive MOSFET into on state) and  $I_D$  rises from zero to full-on current.

$$\text{turn-on time} = \text{delay time} + \text{rise time}$$

$$t_{on} = t_{dn} + t_r$$

↳ At time  $t_1$ , when gate-voltage is removed, the turn OFF process is initiated (since MOSFET is majority carrier device) and here also there is a delay time during which input capacitance discharges from  $V_i$  to  $V_{GS(P)}$

↳ Fall time  $t_f$  - the time during which i/p capacitance discharges from  $V_{GS(P)}$  to  $V_{GS(T)}$  and drain current falls from  $I_D$  to zero.

↳ When  $V_{GS} \leq V_{GS(T)}$  - the device is turned OFF completely.



② If the reverse recovery time of a diode is  $5 \mu\text{s}$  and the rate of decay of the diode current is  $50 \text{ A}/\mu\text{s}$  calculate i)  $Q_{RR}$  ii)  $I_{RR}$ .

$$\text{Given } t_{rr} = 5 \mu\text{s}, \quad \frac{di}{dt} = 50 \text{ A}/\mu\text{s}$$

$$= 5 \times 10^{-6} \text{ s} \quad = 50 \times 10^6 \text{ A/s}$$

$$Q_{RR} = \frac{1}{2} \frac{di}{dt} t_{rr}^2$$

$$= \frac{1}{2} \frac{di}{dt} \times t_{rr}^2 \Rightarrow \frac{1}{2} \times 50 \times 10^6 \times (5 \times 10^{-6})^2$$

$$Q_{RR} = 625 \mu\text{C}$$

$$I_{RR} = \sqrt{2 Q_{RR} \frac{di}{dt}}$$

$$= \sqrt{2 \times 625 \times 10^{-6} \times 50 \times 10^6}$$

$$I_{RR} = 250 \text{ A}$$



②  $\beta \rightarrow 12 \text{ to } 75$ ,  $R_C = 1.5 \Omega$ ,  $V_{CC} = 40V$ ,  $V_B = 6V$ ,  
 $V_{CE}(\text{sat}) = 1.2V$ ,  $V_{BE}(\text{sat}) = 1.6V$  and  $R_B = 0.7 \Omega$ . (find)

i) ODF (ii)  $\beta_{\text{forced}}$  (iii)  $P_T$ .

$$ODF = \frac{I_B}{I_{BS}} ; I_B = \frac{V_B - V_{BE}(\text{sat})}{R_B} \Rightarrow \frac{6 - 1.6}{0.7} \Rightarrow 6.29 A.$$

$$I_{BS} = \frac{I_{CS}}{\beta} ; I_{CS} = \frac{V_{CC} - V_{CE}(\text{sat})}{R_C} \Rightarrow \frac{40 - 1.2}{1.5} \Rightarrow 25.87 A.$$

$$I_{BS} = \frac{25.87}{\beta_{\text{min}}} \Rightarrow \frac{25.87}{12} \Rightarrow 2.15 A.$$

$$ODF = \frac{6.29}{2.15} \Rightarrow 2.91 \approx 3$$

$$\boxed{ODF = 3}$$

$$\text{ii) } \beta_{\text{forced}} = \frac{I_{CS}}{I_B} \Rightarrow \frac{25.87}{6.29} \Rightarrow 4.1128$$

$$\text{iii) } P_T = V_{BE} I_B + V_{CE} I_C$$

$$= (1.6 \times 6.29) + (1.2 \times 25.87)$$

$$P_T = 11.108$$

# SWITCHING LIMITS

- ↳ Secondary breakdown
- ↳ Safe operating area SOA
- ↳ Power derating
- ↳ Break down voltages.

## Secondary breakdown:

\* failure mode in BJTs. In a power transistor with large junction area, under certain cond of current and voltage, the current concentrates in small spots of BEJ.

\* This causes localised heating, progressing into a short b/w collector and emitter which can destroy the transistor.

## Safe Operating Area:-

- ↳ forward - biased SOA
- ↳ reverse - biased SOA

→ the safe operating limits of collecting current  $I_c$  versus collector - emitter voltage  $V_{CE}$  - for reliable operation must always lie within this area.

**Forward biased SOA:- (FBSOA)**  
 during on-state conds, the avg jcn temp and second-ary of transistor. The power handling capability - curve which indicates the  $I_c - V_{CE}$  limits under forward biased conditions. The manufacture always provide FBSOA



### Reverse biased SOA:- RBSOA

during turn-off, a high current and high voltage must be sustained by the transistor with BEJ reverse biased. The manufacture provides the  $I_C-V_{CE}$  limits during reverse-biased turn-off as RBSOA.

### Power derating:-


The power derating factor of a transistor is the amount by which the power dissipating rating of a transistor falls when the transistor junction temperature increases.

The power dissipation rating of a transistor is usually given at  $25^\circ C$ . Manufacturers usually supply the derating factors for determining power dissipation at any temperature above  $25^\circ C$ . The derating factor is specified in  $W/^\circ C$ .

Eg:-  $2mW/^\circ C$  - for each rise in temperature the power rating of the transistor is reduced by  $2mW$ .




# Cross sectional view of BJT

 

NPN

 - ↳ E side n-layer - wider
- ↳ E side p-layer - narrow
- ↳ C side n-layer - narrow and heavily doped.




PNP

- ↳ E side p-layer - wider
- ↳ E side n-layer - narrow
- ↳ C side p-layer → narrow and heavily doped.

Steady-state characteristics:-

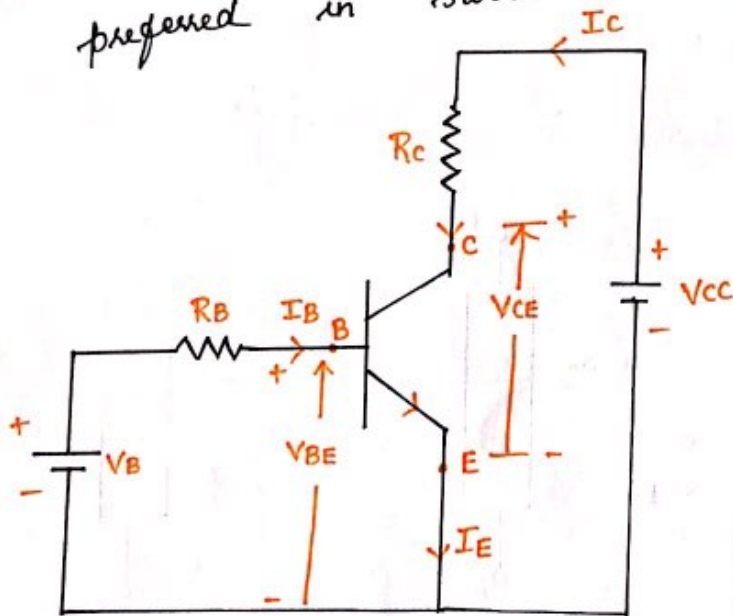Common-emitter configuration is taken which is generally preferred in switched application.



Input Characteristics: ( $I_B$  Vs  $V_{BE}$  keeping const  $V_{CE}$ )

(2)

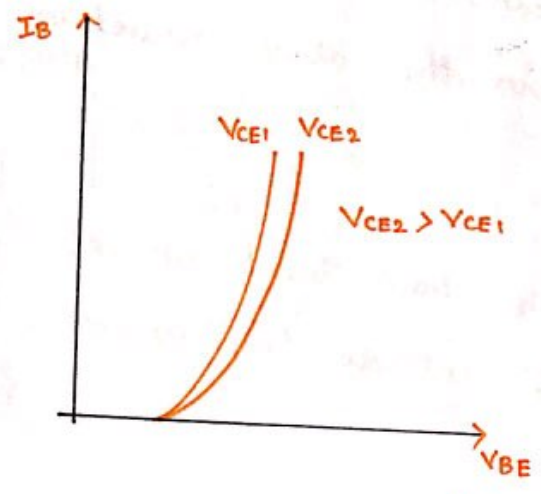


FIG 1

Output Characteristics: ( $I_C$  Vs  $V_{CE}$ )

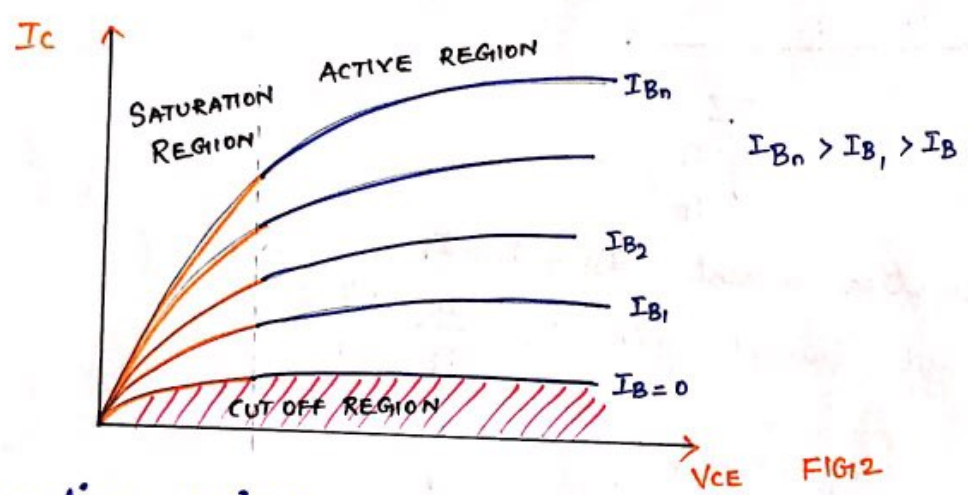


FIG 2

Three - operating regions:

1. cut-off
2. Active
3. Saturation

\* CUT-OFF REGION:-

- Transistor is OFF -  $I_B$  is not sufficient to turn on it
- Both the jxn CBJ and BEJ are reverse biased

\* ACTIVE REGION:-

- Transistor acts as an amplifier
- $V_{CE}$  vs with  $\uparrow$  in  $I_B$
- CBJ is RB and BEJ is FB

 


FIG 3

COMPARISON OF BJT - MOSFET


BJT MOSFET

1. Unipolar device
2. High input impedance (mega ohm)
3. Low switching losses but high conduction losses
4. High frequency applications
5. Voltage controlled device
6. +ve temp - coeff for resistance - easy parallel operations
7. Secondary breakdown does not occur.
8. Limited voltage rating bcoz of more conduction loss - 500V, 140A rating

BJT

 1. Bipolar device
2. Comparitively low input impedance. (k $\Omega$ )
3. High switching losses and low conduction loss.
4. Low frequency applications
5. current controlled device.
6. -ve temp co-eff - current sharing resistors necessary for parallel operations
7. Secondary breakdown occurs.
8. BJTs with rating 1200V, 800A are available.






### FULL WAVE RECTIFIERS

There are two types of single phase full-wave rectifiers,

- \* Center-tapped transformer
- \* Bridge type

The waveform for current

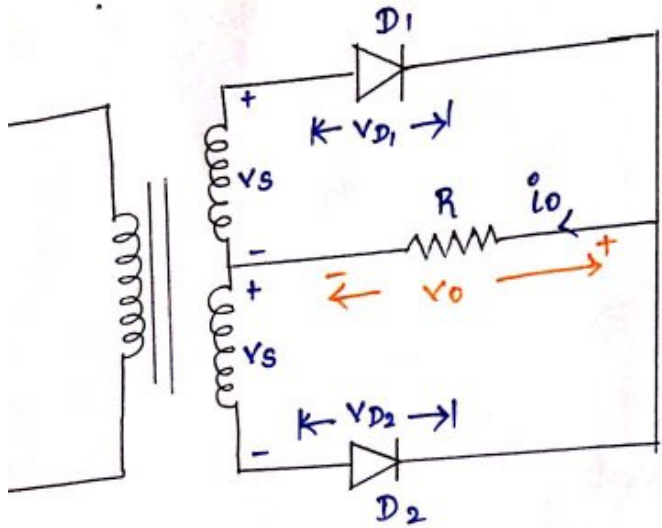

**CENTER TAPPED TRANSFORMER**




During first half cycle  $D_1$  gets forward biased and source voltage appears across the load

During -ve half cycle of i/p,  $D_2$  gets forward biased and load gets connected to the source.

The source, output, and the voltage across diode is shown in the above waveforms.

The average o/p. voltage is,

$$\begin{aligned}
 V_{dc} &= \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t \\
 &= \frac{V_m}{\pi} \int_0^{\pi} \sin \omega t \, d\omega t \\
 &= \frac{V_m}{\pi} (-\cos \omega t) \Big|_0^{\pi}
 \end{aligned}$$

  
 


$$= \frac{V_m}{\pi} [-\cos \pi + \cos 0]$$


$$= \frac{V_m}{\pi} [-(-1) + 1]$$

$$V_{dc} = \frac{2V_m}{\pi} \quad (0.6366 V_m)$$

  Instead of using center-tapped transformer, full-wave rectifier can be obtained using four diodes called **full-wave bridge rectifier** using four diodes



 \* During +ve half cycle,  $D_1, D_2$  gets forward biased, load gets connected to the source and the current flows from (a)  $V_s - D_1 - R - D_2 - V_s$  (b)



\* During -ve half cycle,  $D_3, D_4$  gets forward biased and current flows from (b)  $V_s - D_3 - R - D_4 - V_s$  (a).

The corresponding voltage and current waveform are shown in the figure.



The waveform

$D_1$

$V_s$

$\Rightarrow$  It should be noticed that in case of center-tapped transformer, the peak inverse voltage (PIV) is  $2V_m$ , whereas in case of bridge rectifier PIV is only  $V_m$ .

$\Rightarrow$  center-tapped transformer configuration requires only two diodes whereas bridge rectifier requires four diodes.

Performance parameters:-

\* Average output voltage,  $V_{dc} = \frac{2V_m}{\pi}$

\* Average load/output current,  $I_{dc} = \frac{V_{dc}}{R} \Rightarrow \frac{2V_m}{\pi R}$

\* RMS value of the output voltage,

$$V_{rms} = \left[ \frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t \, d\omega t \right]^{1/2}$$

$$V_{rms}^2 = \frac{1}{\pi} V_m^2 \left[ \int_0^{\pi} \left( \frac{1 - \cos 2\omega t}{2} \right) d\omega t \right]$$

$$= \frac{V_m^2}{2\pi} \left[ \omega t - \frac{\sin 2\omega t}{2} \right]_0^{\pi}$$

$$= \frac{V_m^2}{2\pi} \left[ (\pi - 0) - \frac{\sin 2\pi}{2} + \frac{\sin 0}{2} \right]$$

$$= \frac{V_m^2}{2}$$

Si

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

-- WITH RL LOAD:-

$$V_{rms} = 0.707 V_m$$

$$I_{rms} = \frac{V_{rms}}{R}$$

$$I_{rms} = \frac{0.707 V_m}{R}$$

O/p ac power =  $V_{rms} I_{rms}$

$$= \frac{0.707 V_m \times 0.707 V_m}{R}$$

$$= \frac{0.4998 V_m^2}{R}$$

O/p dc power =  $V_{dc} I_{dc}$

$$= \frac{2 V_m}{\pi} \times \frac{2 V_m}{\pi \times R}$$

$$= \frac{0.4053 V_m^2}{R}$$

Rectification ratio or efficiency  $\eta = \frac{P_{dc}}{P_{ac}}$

$$= \frac{0.4053 V_m^2}{R} \times \frac{R}{0.4998 V_m^2}$$

$$\eta = 81.09\%$$

increases during turn ON and OFF time.

## Characteristics and specification of switches

- \* Ideal characteristics
- \* Practical characteristics
- \* Switch specifications
- \* Device choices.


### Ideal Characteristics:

1. Switch - ON state → i) ability to carry high forward current  $I_F (\infty)$ , ii)  $V_{ON} (0)$  - low on state forward voltage drop iii)  $R_{ON} (0)$  - low on-state resistance -  $\therefore$  power loss  $P_{ON}$  is also zero.
2. Switch OFF state → i)  $V_{BR}$  - ability to withstand high reverse voltage  $\infty$  - reverse voltage ii)  $I_{OFF}$  - low off-state leakage current (zero) iii) high off-state resistance  $R_{OFF} (\infty)$  -  $P_{OFF}$  (zero).
3. The TURN ON - TURN OFF process should be instantaneous → i.e. LOW delay time  $t_d$ , rise time  $t_r$ , storage time  $t_s$ , fall time  $t_f$  (all tending to zero). and also it must require low gate-driver power  $P_G$ , gate-drive voltage  $V_G$ , gate drive current  $I_G$  → all tending to zero.  
→ the ON-OFF process should be controllable (gate signal).
4. The switch should be capable of handling rapid changes in voltage and current i.e. high  $\frac{dv}{dt}$  and  $\frac{di}{dt}$  rating and it should also have high  $i^2t$ .
5. Negative temp co-efficient - to result in equal current rating - when operated in parallel.



losses increases during turn ON and OFF time.

### PRACTICAL CHARACTERISTICS:

 

→ A practical switch will have **FINITE**  $t_d$ ,  $t_r$ ,  $t_s$ , and  $t_f$ .

$$\text{Turn on time} = t_d + t_r \Rightarrow t_{ON}$$

$$\text{Turn off time} = t_s + t_f \Rightarrow t_{OFF}$$

→ The waveforms for device voltage and current are shown in figure.

→ The practical switch dissipates some energy during conduction and switching.

$P_{ON}$  - the average conduction power loss

$$= \frac{1}{T_S} \int_0^{t_{ON}} p \, dt$$

where  $T_S$  - conduction period

$p$  - instantaneous power  $\Rightarrow V_{SW} \times i_{SW}$

$V_{SW}$  - voltage drop across switch

$i_{SW}$  - conducted current.

\* power losses increases during turn ON and OFF time.  
 $\therefore$  power dissipation of a switching device

$$P_D = P_{ON} + P_{SW} + P_G$$

$P_{ON}$  - average conduction power loss

$P_{SW}$  - switching power loss

$$= f_s \left[ \int_0^{t_r} p \, dt + \int_0^{t_s} p \, dt + \int_0^{t_f} p \, dt \right]$$

$\downarrow$  switching freq ( $1/T_s$ )

$P_G$  - gate drive power.

### SWITCH SPECIFICATIONS:- (DATA SHEET)

- \* Voltage ratings
- \* Current ratings
- \* Frequency or switching speed
- \*  $di/dt$  rating
- \*  $dv/dt$  rating
- \* Switching losses
- \* Gate drive requirements
- \* SOA - safe operating area
- \*  $I^2t$  for fusing
- \* Temperature
- \* Thermal resistance.

### DEVICE CHOICES:-

- \* High power applications  $\rightarrow$  Thyristors
- \* Low " "  $\rightarrow$  initially MOSFETs, BJTs - now-a-days slowly replaced by COOLMOS<sub>3</sub> & IGBTs
- \* High power applications with forced commutation - GTOs and IGBTs.