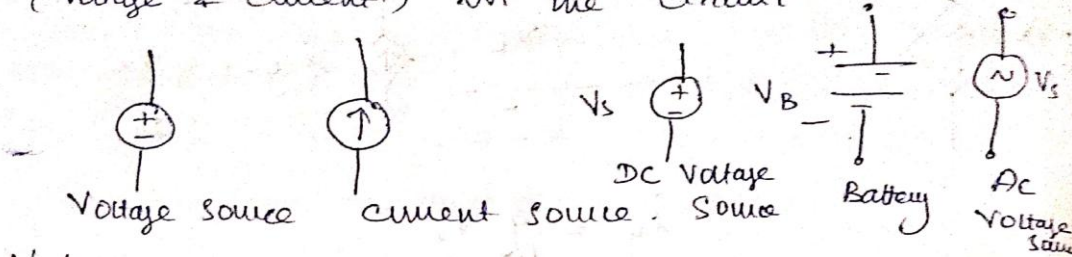


Sub:	Electric Circuit Analysis					Code:	18EE32			
Date:	06/09/2019	Duration:	90 mins	Max Marks:	50	Sem:	3 - B	Branch:	EEE	
								M	OBE C R O B T	
1a	Distinguish between (i) ideal and practical sources, (ii) active and passive elements.							[2]	CO 1	L2
<p><u>Ideal Sources.</u></p> <ul style="list-style-type: none"> → Imaginary electrical sources. → Which provide constant voltage or current to the circuit regardless of load. → They don't have <u>zero internal resistance</u> any internal resistance (R_s) → It is impossible to build a source with zero internal resistance. → Ideal sources are not the practical sources. → Not available in the market. <p><u>Practical Sources.</u></p> <ul style="list-style-type: none"> → Practically possible available. → Have some internal resistance (R_i) → Provides variable current / voltage. → Available in market. 										

Independent Source

* The source does not depend on any other quantity (voltage & current) in the circuit.




Dependent and Independent Sources

Dependent Sources / controlled source.

→ Source quantity is determined by the voltage (or) current existing at some other location in the system.

1b Determine three unknown currents using Mesh Analysis.

[8] CO L4
1

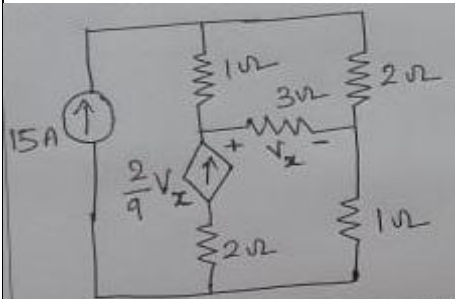

from figure,

$$\boxed{i_1 = 15A}$$

$$i_3 - i_1 = \frac{2V_x}{9} \rightarrow \textcircled{1}$$

KVL for loop 2

$$-i_1 + 6i_2 - 3i_3 = 0 \quad (\because i_1 = 15A)$$

$$6i_2 - 3i_3 = 15 \rightarrow \textcircled{2}$$

$$V_x = 3(i_3 - i_2) \rightarrow \textcircled{3}$$

Sub. $\textcircled{3}$ in $\textcircled{1}$

$$i_3 - i_1 = \frac{6}{9}(i_3 - i_2) = \frac{2}{3}(i_3 - i_2)$$

$$2i_2 + i_3 = 45 \rightarrow \textcircled{4}$$

Solving $\textcircled{2}$ & $\textcircled{4}$


$$\boxed{i_2 = 12.5A}$$

$$\boxed{i_3 = 20A}$$

$$\boxed{i_1 = 15A}$$

2 Find the node voltages for the circuit shown in Figure using nodal analysis.

[10] CO L3
1

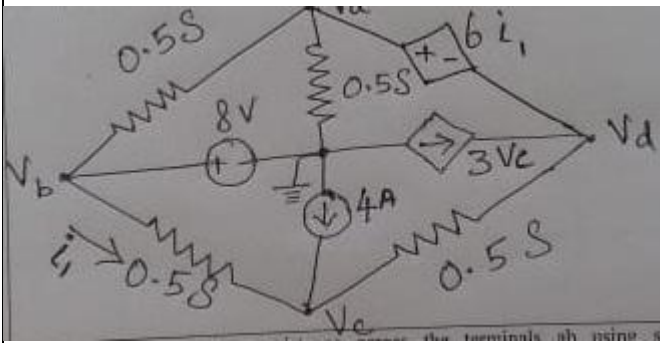

KCL at node c,
 $4 - \frac{V_c - V_d}{0.5} - 0.5 \times \frac{V_c - V_a}{1} = 0$
 $4 - 0.5(V_c - V_d) - 0.5(V_c - V_a) - 3V_c = 0$
 $-4V_c + 0.5V_b + 0.5V_d = 0$
 $-V_b + \frac{4}{0.5}V_c - \frac{0.5}{0.5}V_d = 0$
 $-V_b + 8V_c - V_d = 20 \rightarrow \textcircled{1}$

$V_b = 8V$ \rightarrow constant eqn.
 $V_a - V_d = 6i_1 = 6 \times 0.5(V_b - V_c)$
 $i_1 = 0.5(V_b - V_c)$
 $V_a - V_d = 3V_b - 3V_c$
 $V_a + 3V_c - 3V_b - V_d = 0 \rightarrow \textcircled{3}$

From $\textcircled{1}$
 $8 + 8V_c - V_d = 20$
 $8V_c - V_d = 12 \rightarrow \textcircled{4}$


From $\textcircled{3}$, $V_a + 3V_c - 3 \times 8 - V_d = 0$
 $V_a + 3V_c - V_d = 24 \rightarrow \textcircled{5}$



KCL at Supernode,
 $-(V_a - V_b)0.5 - V_a \times 0.5 + 3V_c - 0.5(V_d - V_c) = 0$
 $-V_a + V_b - V_a - \frac{3}{0.5}V_c - V_d + V_c = 0$
 $-2V_a + V_b - 5V_c - V_d = 0$
 $2V_a - V_b + 5V_c + V_d = 0 \rightarrow \textcircled{6}$
 $2V_a - 8 + 5V_c + V_d = 0$
 $2V_a + 5V_c + V_d = 8 \rightarrow \textcircled{7}$

Solving eqn. $\textcircled{4}$, $\textcircled{5}$ & $\textcircled{6}$.
 $V_a = 63.281V$
 $V_b = 8V$
 $V_c = -0.173V$
 $V_d = -39.8V$


3a Determine the equivalent resistance across the terminals ab using star-delta transformation. Consider all resistance are 10Ω .

[6] CO L4
2

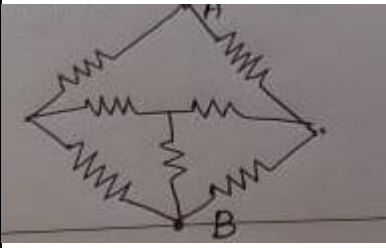

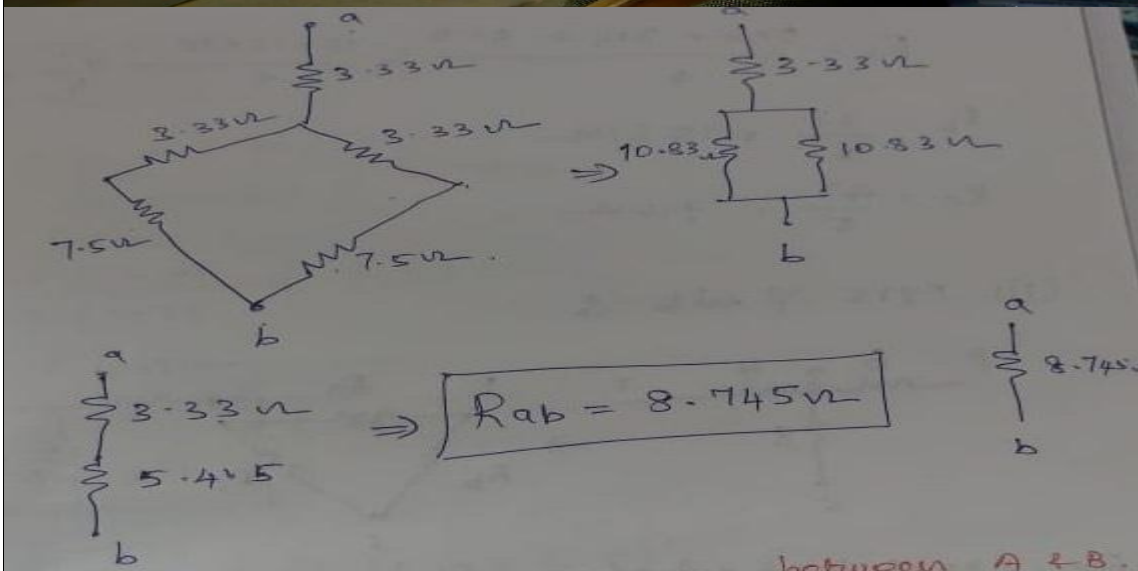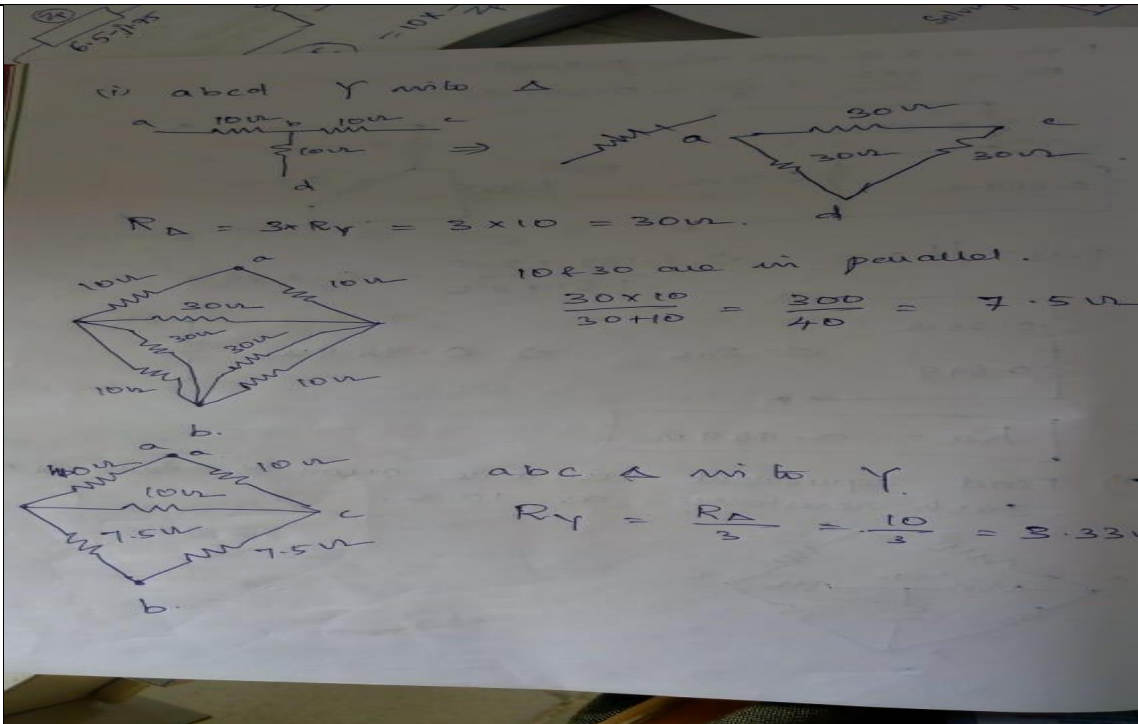


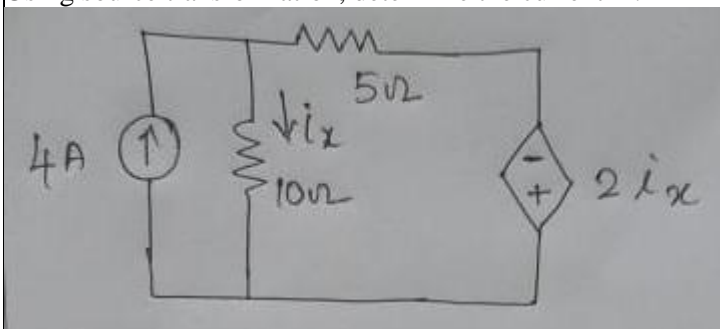3b Using source transformation, determine the current i_x .



[4] CO L4
2

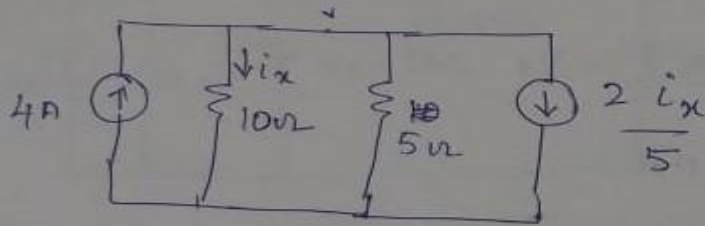i) Convert $\frac{2i_x}{5}$ A, 10Ω into current source



$$i' = \frac{V}{R}$$

$$= \frac{2i_x}{5}$$

$$4 - \frac{2i_x}{5} = \frac{V}{10} + \frac{V}{5} + 5i_x + 5i_x + 30$$

$$\Rightarrow 0.1V + 0.2V$$

$$4 - 0.4i_x = 0.3V$$

$$i_x = \frac{V}{10}$$

$$4 - 0.4 \frac{V}{10} = 0.3V$$

$$4 - 0.04V = 0.3V$$


$$4 = 0.34V$$

$$V = 11.7V$$




$$i_x = \frac{V}{10} = \frac{11.7}{10}$$

$$i_x = 1.17A$$

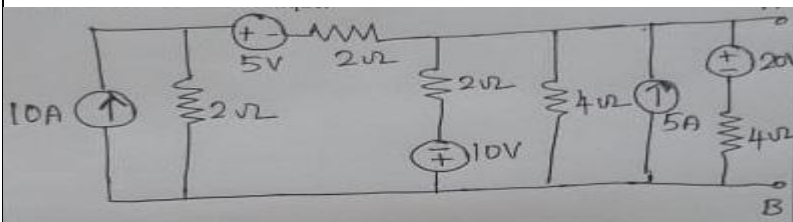4a Transform the network given in Figure into a single voltage source using source transformation technique.




[5] CO L2
2

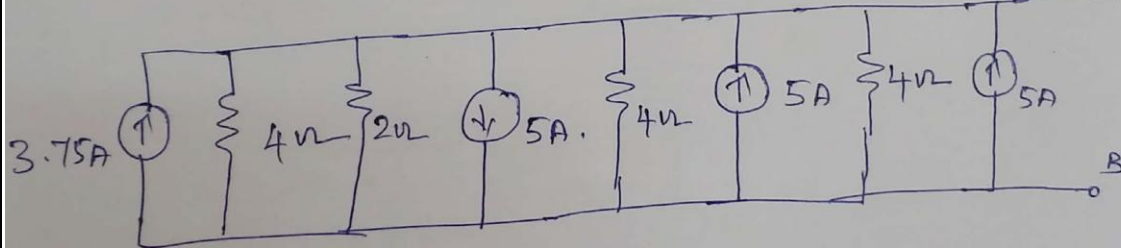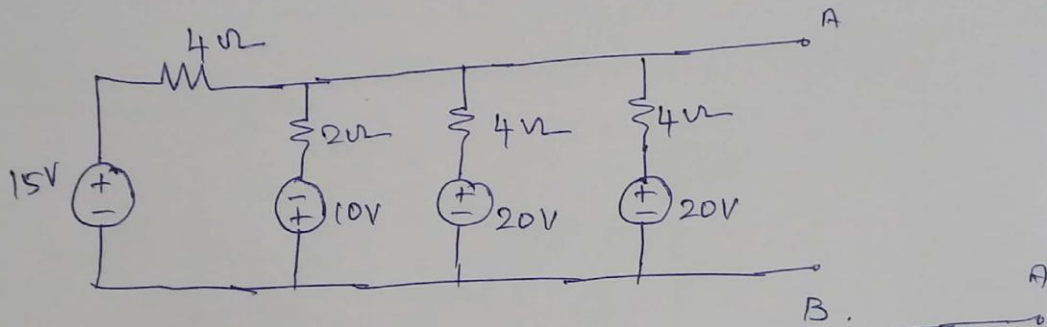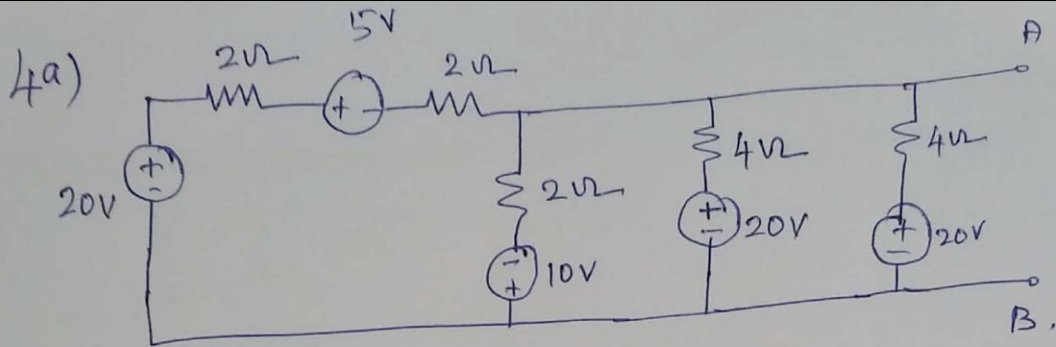

$$I = 3.75 - 5 + 5 + 5 = 8.75 \text{ A}$$

$$\frac{1}{R_T} = \frac{1}{4} + \frac{1}{2} + \frac{1}{4} + \frac{1}{4} = 1.25$$


$$R_T = \frac{1}{1.25} = 0.8 \Omega$$

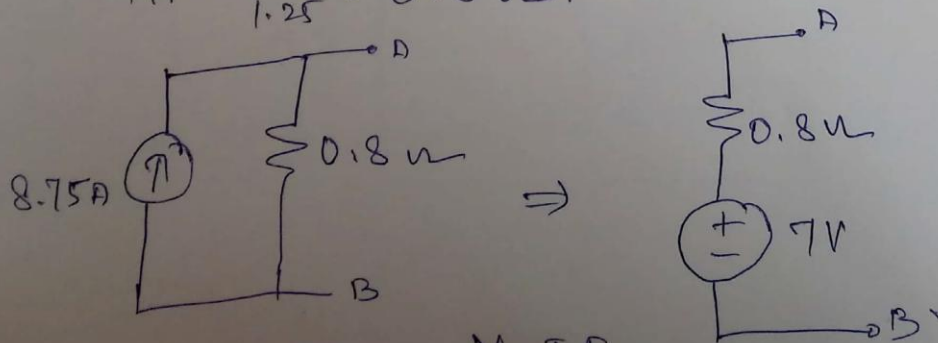

$$V = IR = 8.75 \times 0.8 = 7 \text{ V}$$

4b Find V_x in the circuit shown in Figure using source transformation.

[5] CO L3
2

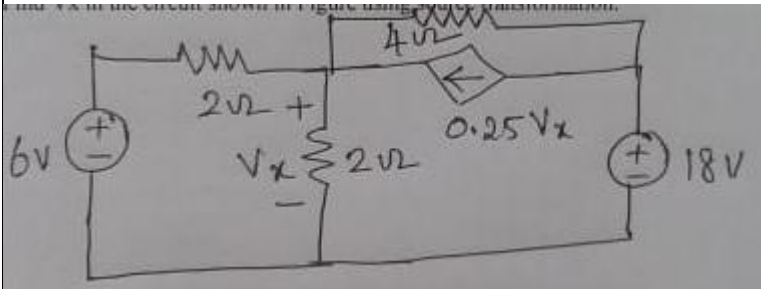

5) Find V_x using source transformation

(i) $6V, 2\Omega$ into current source.

(ii) $0.25V_x, 4\Omega$ into voltage source.

(iii) $2\Omega \parallel 2\Omega$.


$V = IR$
 $= 0.25V_x \times 4$
 $= V_x$

$\frac{2 \times 2}{2+2} = 1\Omega$

Handwritten calculations on the right page:
 (iv) Write KVL ABCDEFA
 $3 - 5i - V_x - 18 = 0$
 $-15 - 5i - V_x = 0$ (1)
 KVL for ABFEA
 $3 - 1xi - V_x = 0$
 $3 - i - V_x = 0$
 $V_x = 3 - i$ (2)
 Sub (2) in (1)
 $-15 - 5i - (3 - i) = 0$
 $-15 - 5i - 3 + i = 0$
 $-4i - 18 = 0$
 $4i = -18$
 $i = \frac{-18}{4} = -4.5A$
 $V_x = 3 - (-4.5)$
 $V_x = 7.5V$
 $i = -4.5A$

5. Find equivalent resistance R_{ab} using star/delta or delta/star conversion.

[10] CO L3
2

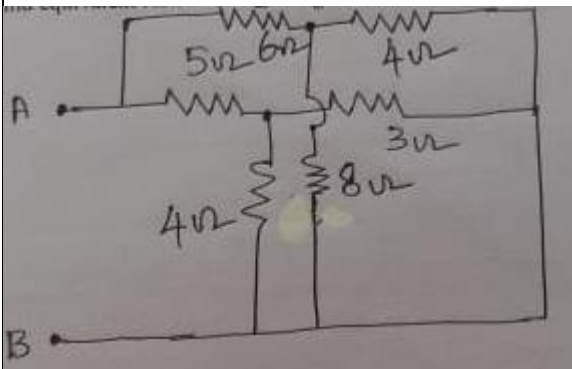


$R_a = \frac{6 \times 4}{4} = 6 \Omega$
 $R_b = \frac{4 \times 8}{4} = 8 \Omega$
 $R_c = \frac{4 \times 8}{4} = 8 \Omega$

(ii) p q r s Y into Δ

$R_a = \frac{6 \times 4 + 4 \times 8 + 8 \times 6}{8} = \frac{24 + 32 + 48}{8} = \frac{104}{8} = 13 \Omega$
 $R_b = \frac{104}{4} = 26 \Omega$
 $R_c = \frac{104}{8} = 13 \Omega$

$R_{ab} = 26 \Omega \parallel (13 \Omega \parallel 15.67 \Omega \parallel 9.4 \Omega)$
 $R_{ab} = 26 \parallel (13 \parallel 6.17 \parallel 6.09)$
 $R_{ab} = 26 \parallel 9.78$
 $R_{ab} = \frac{26 \times 9.78}{26 + 9.78} = 7.17 \Omega$
 $R_{ab} = \frac{7.17 \times 17.33}{7.17 + 17.33} = 6.09 \Omega$
 $R_{ab} = \frac{15.67 \times 26}{15.67 + 26} = 9.78 \Omega$
 $R_{ab} = \frac{9.78 \times 12.26}{9.78 + 12.26} = 5.44 \Omega$

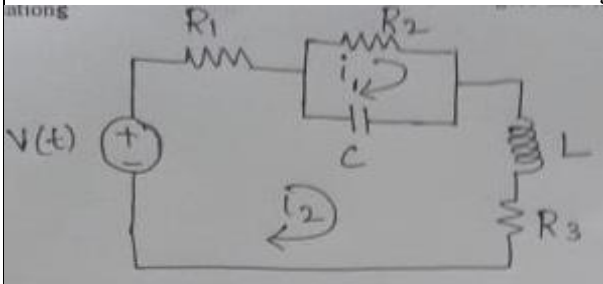6. Construct dual network for the circuit shown in Figure and write the equilibrium equation.



5) Write equilibrium equations using KVL, draw its dual and write its equilibrium equation.

$v = iR$
 $v = L \frac{di}{dt}$
 $v = \frac{1}{C} \int i dt$

KVL Equations

to Mesh 1

$$i_1 R_1 + \frac{1}{C} \int (i_1 - i_2) dt = 0 \quad \text{--- (1)}$$

Mesh 2

$$i_2 R_2 + \frac{1}{C} \int (i_2 - i_1) dt + L \frac{di_2}{dt} + i_2 R_3 = v(t) \quad \text{--- (2)}$$

Dual Network

$I = \frac{v}{R} = vG$
 $I = \frac{1}{L} \int v dt$
 $I = C \frac{dv}{dt}$

KCL

Node 1

$$V_1 \frac{1}{R_2} + \frac{1}{L} \int (V_1 - V_2) dt = 0 \quad \text{--- (1)}$$


Node 2

$$V_2 \frac{1}{R_3} + C \frac{dV_2}{dt} + V_2 \frac{1}{R_2} + \frac{1}{L} \int (V_2 - V_1) dt = I(t) \quad \text{--- (2)}$$

[10] 2 CO L3

7. Find current i_a using superposition theorem.

[10] CO L3
3

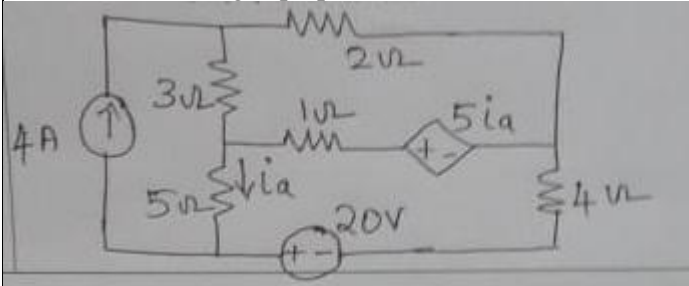

KVL for Loop 1
 $4 = 5i_0$
 $i_0 = 4A$

KVL for Loop 2
 $2i_2 + 3(i_2 - i_1) + 1(i_2 - i_3) = 5i_0$
 $i_1 - i_3 = i_0$
 $-3i_1 + 6i_2 - i_3 = 5i_0$
 $i_1 - i_3 = i_0$
 $4 - i_3 = i_0$
 $i_3 = 4 - i_0$; $i_1 = 4A$

Sum (1)
 $-3 \times 4 + 6i_2 - (4 - i_0) = 5i_0$
 $-12 + 6i_2 - 4 + i_0 = 5i_0$
 $6i_2 - 16 = 4i_0$
 $3i_2 - 2i_0 = 8$ (2)

KVL for Loop 3
 $5(i_3 - i_1) + 1(i_3 - i_2) + 4i_3 = -5i_0$
 $i_1 = 4A$; $i_3 = 4 - i_0$
 $5(i_3 - 4) + 1(i_3 - i_2) + 4i_3 = -5i_0$
 $10i_3 - 20 + i_2 = -5i_0$
 $i_3 = 4 - i_0$
 $10(4 - i_0) - 20 + i_2 = -5i_0$
 $40 - 10i_0 - 20 + i_2 = -5i_0$
 $-i_2 - 5i_0 = -20$ (3)
 $i_2 + 5i_0 = 20$ (4)
 $(2) \times 3 \Rightarrow 3i_2 - 2i_0 = 24$
 $(4) \times 3 \Rightarrow 3i_2 + 15i_0 = 60$
 $-17i_0 = -36$
 $i_0 = \frac{36}{17} = 2.1176A$

(ii) Using 20V, Replace 4A

$i_0 = -12$

KVL for Loop 1
 $2i_1 + 3i_1 + 1(i_1 - i_2) = 5i_0$
 $6i_1 - i_2 = 5i_0$
 $6i_1 + i_0 = 5i_0$
 $6i_1 - 4i_0 = 0$ (1)

KVL for Loop 2
 $1(i_2 - i_1) + 5i_2 + 4i_2 = 20 - 5i_0$
 $10i_2 - i_1 = 20 - 5i_0$
 $i_2 = -i_0$
 $-10i_0 - i_1 = 20 - 5i_0$
 $-i_1 + 5i_0 = 20$ (2)

$i_0 = -3.53A$ (1) $\Rightarrow 6i_1 - 4i_0 = 0$
 $(2) \times 6 \Rightarrow -6i_1 - 30i_0 = 120$
 $-34i_0 = 120$
 $i_0 = \frac{120}{-34}$
 $i_0 = -3.53A$

(ii) Algebraic Sum
 Using 4A: $i_0' = 3.06A$
 Using 20V: $i_0'' = -3.53A$
 $i_0 = i_0' + i_0''$
 $= 3.06 - 3.53$
 $i_0 = -0.47A$

4) Using superposition theorem, determine V_L