

Solutions of Internal Assessment Test - I

| | | | | |
|------|-----------------------|---------|-------|--------|
| Sub: | DIGITAL SYSTEM DESIGN | | Code: | 18EE35 |
| Sem: | 3rd | Branch: | EEE | |

1. Distinguish prime implicants and essential prime implicants. Determine prime implicants and essential prime implicants of $Y=f(a,b,c,d)=\pi M(0,1,4,5,8,9,11)+d(2,10)$ and obtain the final expression.


Solution:

→ Prime Implicants

① In K-map, after grouping the cells, the sum terms having the minterm that appears are called prime implicant groups. And the minterms are known as prime implicant.

② All prime implicants are not essential prime implicants.

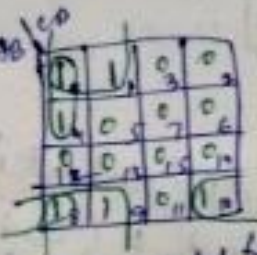③ Example: $f(A, B, C, D)$
 $= \bar{A}\bar{C}\bar{D} + A\bar{B}D + \bar{B}C$



Cell, 0, 1, 4, 5, 8, 9, 10 are all from prime implicant group.

Essential Prime Implicants

① In K-map, after grouping the cell, it is observed that some cells may appear in only one prime implicant groups. These are known as essential prime implicants.

② All essential prime implicants are the prime implicants.

③ Example:
 from the cells, 1, 4, 9, 10 are appeared only in one prime implicant group.

$$Y = f(a, b, c, d) = \sum m(1, 4, 5, 8, 9, 11) + d(2, 10)$$
 (POS)

Prime implicants (N)

$$N = (a+c)(b+c)(\bar{a}+b)$$

Essential Prime Implicants, $N = (a+c)(\bar{a}+b)$

Extra \rightarrow Implementation: —

2. Find a minimum SOP solution using Quine-McCluskey method $F(a,b,c,d) = \sum m(2,3,4,5,13,15) + d(8,9,10,11)$.

Solution:

Step 1 : List all minterms in binary form.

| Minterms | Binary representation | | | |
|-----------|-----------------------|---|---|---|
| m_2 | 0 | 0 | 1 | 0 |
| m_3 | 0 | 0 | 1 | 1 |
| m_4 | 0 | 1 | 0 | 0 |
| m_5 | 0 | 1 | 0 | 1 |
| m_{13} | 1 | 1 | 0 | 1 |
| m_{15} | 1 | 1 | 1 | 1 |
| dm_8 | 1 | 0 | 0 | 0 |
| dm_9 | 1 | 0 | 0 | 1 |
| dm_{10} | 1 | 0 | 1 | 0 |
| dm_{11} | 1 | 0 | 1 | 1 |

Step 2 : Arrange the minterms according to number of 1's.

| Minterms | Binary representation | | | |
|----------|-----------------------|---|---|---|
| m_2 | 0 | 0 | 1 | 0 |
| m_4 | 0 | 1 | 0 | 0 |
| m_8 | 1 | 0 | 0 | 0 |
| m_3 | 0 | 0 | 1 | 1 |
| m_5 | 0 | 1 | 0 | 1 |
| m_9 | 1 | 0 | 0 | 1 |
| m_{10} | 1 | 0 | 1 | 0 |
| m_{11} | 1 | 0 | 1 | 1 |
| m_{13} | 1 | 1 | 0 | 1 |
| m_{15} | 1 | 1 | 1 | 1 |

Step 3 :

| Minterm | Binary representation | | | |
|----------|-----------------------|---|---|---|
| 2, 3 ✓ | 0 | 0 | 1 | - |
| 2, 10 ✓ | - | 0 | 1 | 0 |
| 4, 5 | 0 | 1 | 0 | - |
| 8, 10 ✓ | 1 | 0 | - | 0 |
| 8, 9 ✓ | 1 | 0 | 0 | - |
| 3, 11 ✓ | - | 0 | 1 | 1 |
| 5, 13 | - | 1 | 0 | 1 |
| 9, 13 ✓ | 1 | - | 0 | 1 |
| 9, 11 ✓ | 1 | 0 | - | 1 |
| 10, 11 ✓ | 1 | 0 | 1 | - |
| 13, 15 ✓ | 1 | 1 | - | 1 |
| 11, 15 ✓ | 1 | - | 1 | 1 |


Step 4 :


| Minterm | Binary representation | | | |
|---------------|-----------------------|---|---|---|
| 2, 3, 10, 11 | - | 0 | 1 | - |
| 8, 9, 10, 11 | 1 | 0 | - | - |
| 9, 11, 13, 15 | 1 | - | - | 1 |

Scanned with
CamScanner

Step 5 :

| Prime implicants | | | | Binary representation | | | |
|------------------|-----------|-----------|---------------|-----------------------|---|---|---|
| \bar{a} | b | \bar{c} | 4, 5 | 0 | 1 | 0 | - |
| b | \bar{c} | d | 5, 13 | - | 1 | 0 | 1 |
| \bar{b} | c | | 2, 3, 10, 11 | - | 0 | 1 | - |
| a | \bar{b} | | 8, 9, 10, 11 | 1 | 0 | - | - |
| a | d | | 9, 11, 13, 15 | 1 | - | - | 1 |

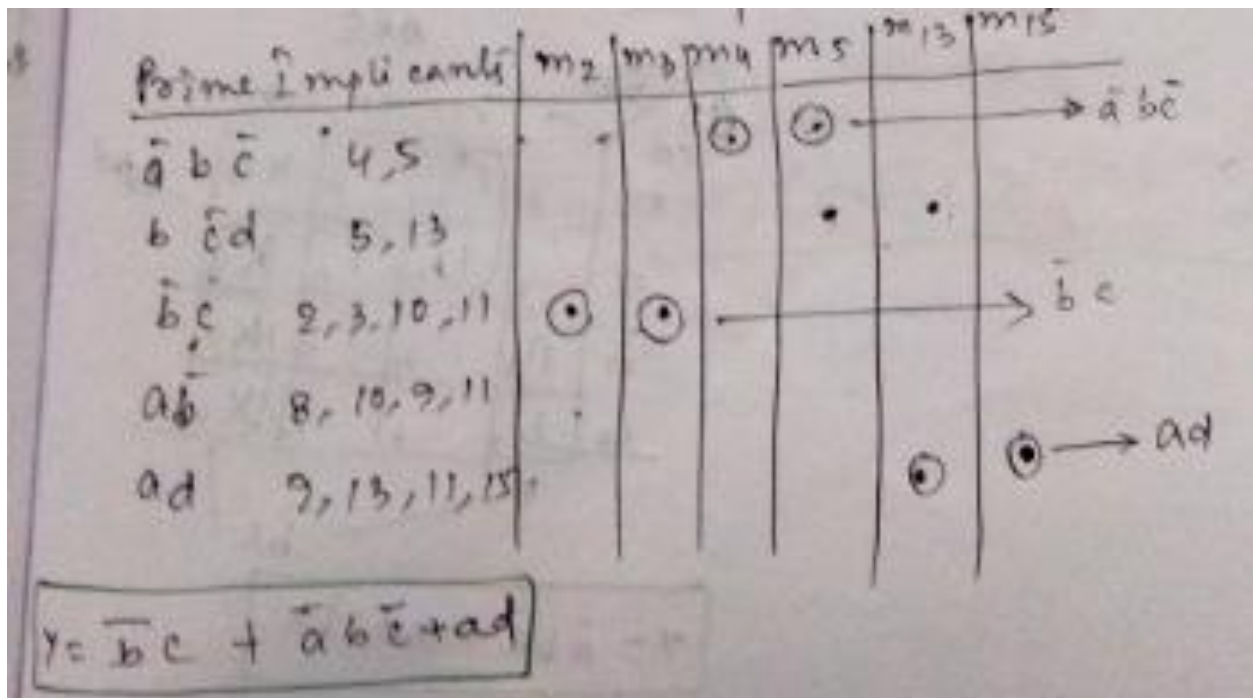

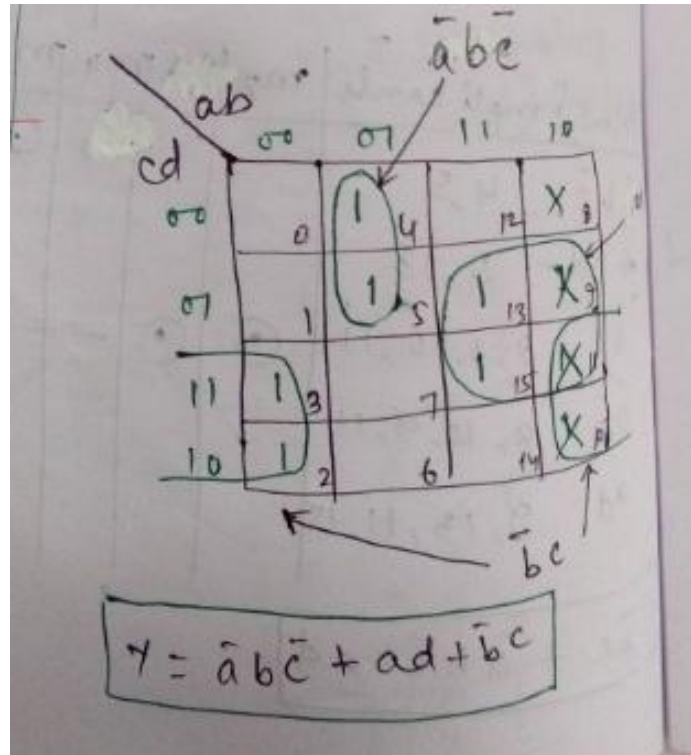

3. Place the following equations into proper canonical forms:

(a) $P=f(a,b,c) = ab' + ab' + bc$

(b) $T= f(a,b,c) = (a+b')(b'+c)$

Solution:

→ (a) $P = f(a,b,c) = ab' + ab' + bc$
 $= ab'(c+c') + ab'(c+c') + bc(a+a')$
 $= ab'c + ab'c' + ab'c + ab'c' + abc + a'bc$
 $= ab'c + ab'c' + abc + a'bc$
 ∴ Canonical form of equation (a) is

$f(a,b,c) = ab'c + ab'c' + abc + a'bc$


$$\begin{aligned}
 \textcircled{b} \quad T = f(a, b, c) &= (a+b')(b+c) \\
 &= (a+b'+c \cdot c')(b'+c+a \cdot a') \\
 &= (a+b'+c)(a+b'+c')(a+b'+c) \\
 &\quad (a'+b'+c) \\
 &= (a+b'+c)(a+b'+c')(a'+b'+c)
 \end{aligned}$$


\therefore Canonical form of equation (b) is

$$f(a, b, c) = (a+b'+c)(a+b'+c')(a'+b'+c)$$

4. Implement the function using active low output dual 2:4 decoder line decoder IC 74139
 i) $F_1(A, B, C) = \sum m(0, 1, 2, 5)$ ii) $F_2(A, B, C) = \pi M(1, 3, 4, 7)$

Solution:

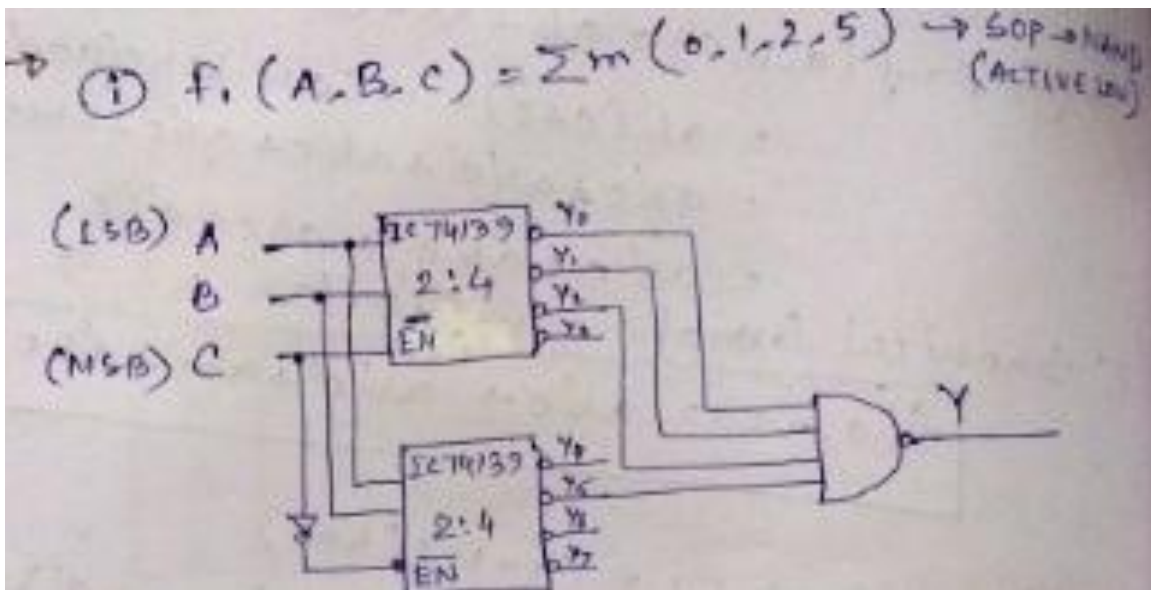

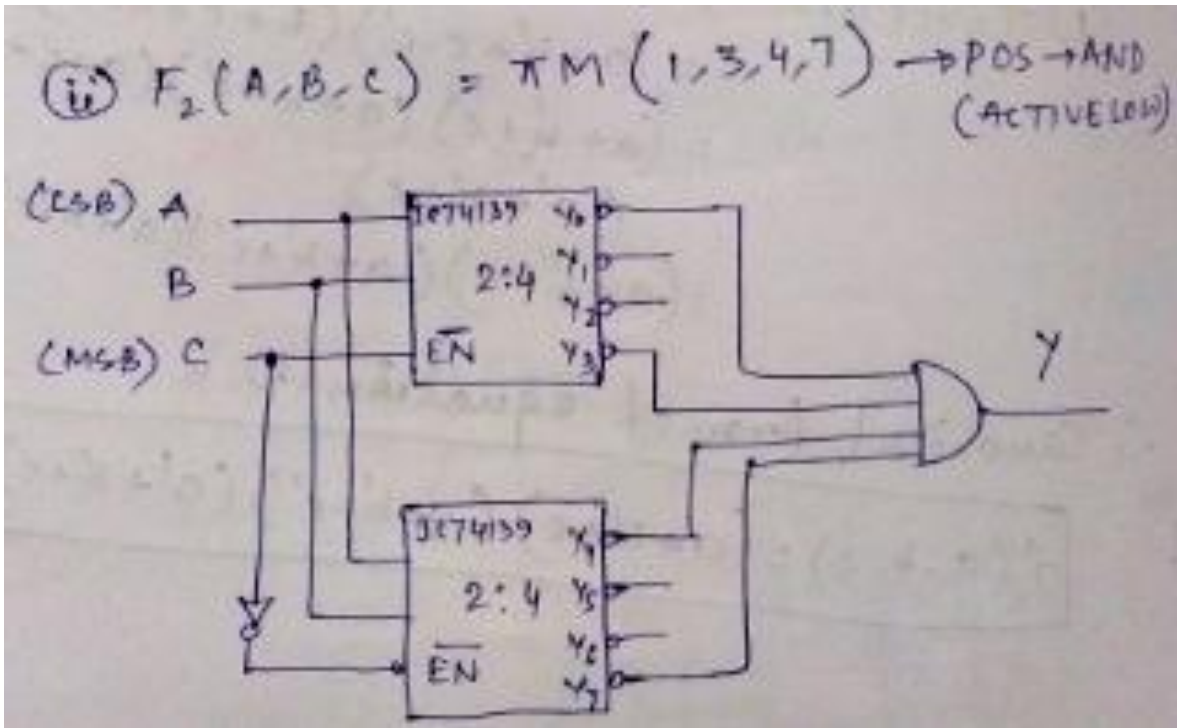

5. What is the problem associated with the parallel adder? Explain the method of correcting it, with suitable circuit equations.

Solution:

The parallel adder is ripple carry adder in which the carry output of each full-adder stage is connected to the carry input of the next higher-order stage. Therefore, the sum and carry outputs of any stage cannot be produced until the input carry occurs; this leads to a time delay in the addition process. This delay is known as **carry propagation delay**.

One method of speeding up this process by eliminating inter stage carry delay is called **look ahead-carry addition**. This method utilizes logic gates to look at the lower-order bits of the augend and addend to see if a higher-order carry is to be generated. It uses two functions: carry generate and carry propagate.

Consider the circuit of the full-adder shown in Fig. 2.11.1. Here, we define two functions: carry generate and carry propagate.

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

The output sum and carry can be expressed as

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$


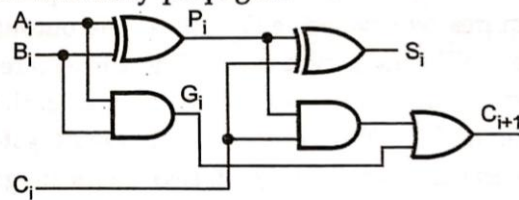


Fig. 2.11.1 Full-adder circuit

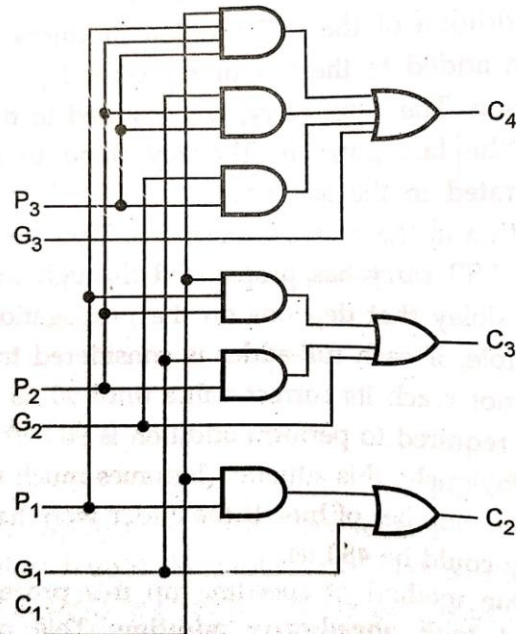G_i is called a carry regardless of the input with the propagation. Now the Boolean follows.



with A_i and B_i are one, the term associated with C_i can be written as

Fig. 2.11.2 Logic diagram of a look ahead carry generator

$$C_2 = G_2 + P_2 C_1$$

$$C_3 = G_3 + P_3 C_2 = G_3 + P_3 (G_2 + P_2 C_1) = G_3 + P_3 G_2 + P_3 P_2 C_1$$

$$C_4 = G_4 + P_4 C_3 = G_4 + P_4 (G_3 + P_3 G_2 + P_3 P_2 C_1)$$

$$C_4 = G_4 + P_4 G_3 + P_4 P_3 G_2 + P_4 P_3 P_2 C_1$$

Scanned with CamScanner

From the above Boolean function it can be seen that C_4 does not have to wait for C_3 and C_2 to propagate; in fact C_4 is propagated at the same time as C_2 and C_3 .

6. Realize the following Boolean function $Y=f(w,x,y,z)=\Sigma(0,1,5,6,7,10,15)$ using :
 i) 16 to 1 MUX ii) 8:1 MUX iii) 4:1 MUX.

Solution:

