

--	--	--	--	--	--	--	--	--	--	--



Internal Test -1 September 2019

Sub:	Electrical and Electronic Measurements						Code:	18EE36	
Date:	07/09 /2019	Duration:	90 mins	Max Marks:	50	Sem:	III	Branch:	EEE
Note: Answer any <b>FIVE</b> full questions with neat diagram wherever necessary.									

		Marks	OBE	
			CO	RBT
1	With neat sketch explain Kelvin's double bridge and obtain an expression for balancing condition. Write down the advantage and disadvantage.	[10]	CO1	L1
2	With necessary sketch, explain megger.	[10]	CO1	L1
3	What do you mean by sensitivity? Derive an expression for galvanometer current under unbalanced condition.	[10]	CO1	L2
4	With proper phasor diagram, derive the balancing equation for Anderson's bridge.	[10]	CO1	L2
5	With proper phasor diagram, explain the Maxwell's Inductance capacitance bridge. Write the advantage and disadvantage.	[10]	CO1	L2
6	Write a short note on	[5]	CO1	L2
	(a) Shielding of bridges (b) Hay's bridge	[5]	CO1	L2

*Hadhi*

*S. P. Ma lib*


*54 copies*





Solution

① Balancing Cond<sup>n</sup>

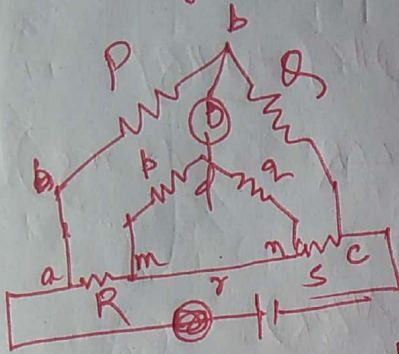

$$E_{ab} = \frac{P}{P+Q} E_{ac}$$

$$E_{ac} = IR + \frac{(P+Q)r}{P+Q+r} I + Is$$

$$= I \left[ R + \frac{(P+Q)r}{P+Q+r} + S \right]$$

$$R = \frac{P}{Q} S + \frac{qr}{P+Q+r} \left[ \frac{P}{Q} - \frac{P}{Q} \right]$$


$$\therefore \frac{P}{Q} = \frac{P}{Q}$$

$$\therefore R = \frac{P}{Q} S$$

adv: low value of  $R$ .


disadv Extra ratio arms are there.

②

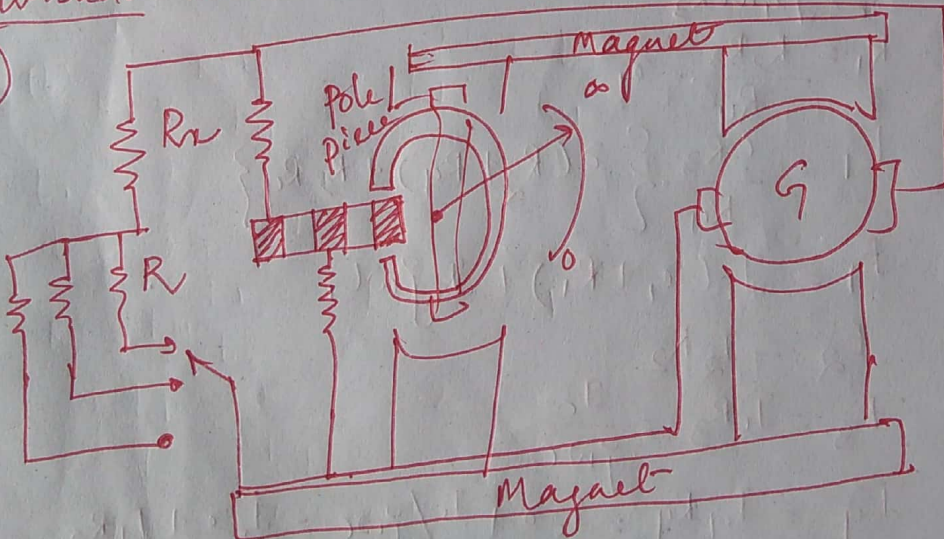




3

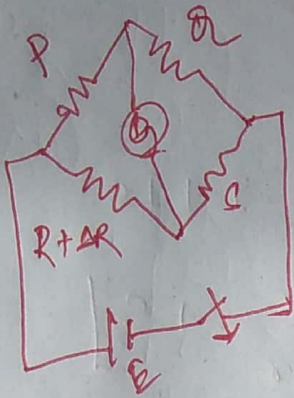

$$E_0 = E_{ad} - E_{cb}$$

$$= E \left[ \frac{R+AR}{R+AR+S} - \frac{P}{P+Q} \right] \quad \because R=S=P=Q$$

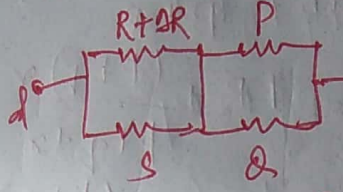
$$\therefore E_0 = E \left[ \frac{AR}{4R} \right] \quad \because AR \ll CR$$



$$R_0 = [(R+AR) \parallel S] + [P \parallel Q]$$

$$R_0 = \left[ \frac{RS}{R+S} + \frac{PQ}{P+Q} \right] \quad \left[ \because \Delta R \ll CR \text{ so; } AR \text{ neg.} \right]$$

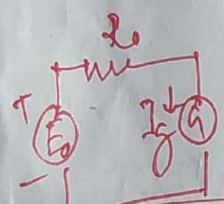For a bridge with equal arms:  
 $P=Q=R=S \quad \therefore R_0 = R$



$$\therefore I_g = \frac{E_0}{R_0 + G}$$

$$I_g = \frac{E_0}{R_0 + G} \quad \text{; Equal arm; } I_g = \frac{E_0}{R_0 + G}$$

$$S \approx S_0 \frac{ESAR}{(R+S)^2}$$

$$\therefore S_0 = \frac{S^2}{R_0 + G}$$


$$S = \frac{S^2 ESAR}{(R_0 + G)^2 (R+S)^2}$$

$$= \frac{S^2 E AR}{4RCR + G}$$

$$S_B = \frac{S^2 ESAR}{(R+S)^2} \quad S_B = \frac{S^2 E}{4(R+S)}$$

$P=Q=R=S$

4) Anderson's Bridge

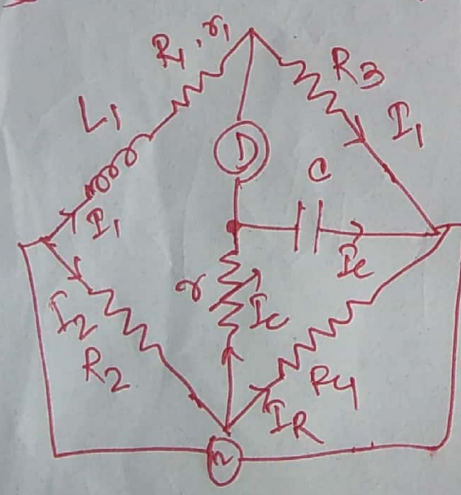

$$I_c = \int I_1 \omega C R_3$$

$$R_1 = \frac{R_2 R_3}{R_4} - r_1$$

$$L_1 = \frac{C R_3}{R_4} \left\{ r_1 (R_2 + R_4) + R_2 R_4 \right\}$$


$$E_1 = I_1 (r_1 + R_1) + I_1 j \omega L_1$$

$$E_2 = I_2 R_2$$

$$E_3 = I_3 R_3 = \frac{I_c}{j \omega C}$$


$$E_4 = I_4 R_4 = I_c r_1 + I_c / j \omega C = I_c r_1 + I_1 R_3$$

$$I_2 = I_3 + I_4$$

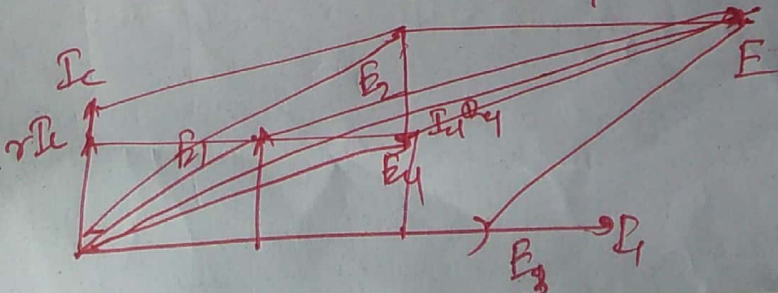




6(b) Hay's bridge

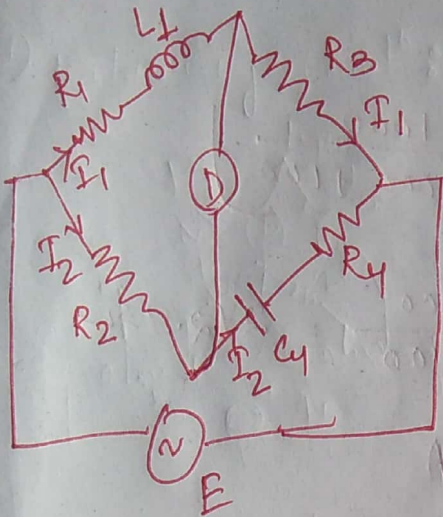

$$I_1 = \frac{R_1}{\omega^2 C_3 R_4}$$

$$R_1 = \frac{\omega^2 C_3^2 R_4 R_2 R_3}{1 + R_4^2 \omega^2 C_3^2}$$
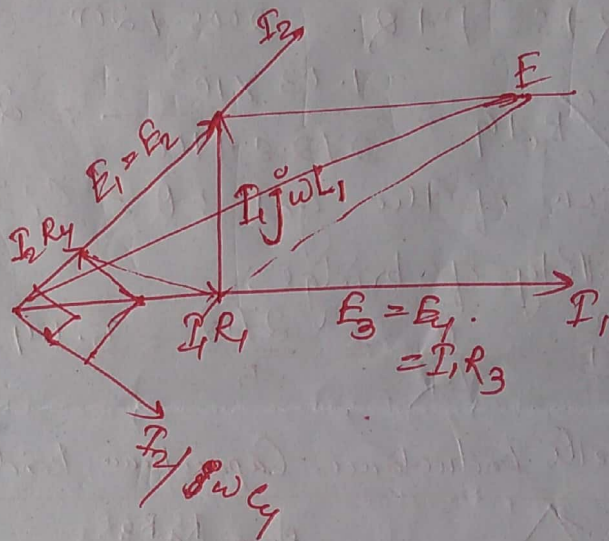
$$L_1 = \frac{R_2 R_3 C_3}{1 + \omega^2 R_4^2 C_3^2}$$



7(b)  $R_1 = \frac{R_2 R_3}{R_4}$  &  $L_1 = \frac{R_2 L_3}{R_4}$

$$\frac{L_1}{L_3} = \frac{R_2}{R_4} = \frac{R_1}{R_3}$$

$$R_2 = R_4 \frac{L_1}{L_3} = 750 \times \frac{0.22}{0.1} = 1650 \Omega$$

$$\& \frac{L_1}{L_3} = \frac{R_2}{R_4} = 2.2$$

$$\therefore \frac{R_1}{R_3} = \frac{20}{40} = 0.5$$

$$\therefore \frac{R_1 + \alpha_1}{R_3} = 2.2 \quad \alpha_1 = 2.2 \times 40 - 20 = 68 \Omega$$



$$7(a) R = \left( \frac{P}{Q} \right) S = \frac{1000}{100} \times 200 = 2000 \Omega$$

$$\Delta R = 2005 - 2000 = 5 \Omega$$

$$E_0 = E \left[ \frac{R}{R+S} - \frac{P}{P+Q} \right] = 5 \left[ \frac{2005}{2005+200} - \frac{1000}{1000+100} \right]$$

$$= 1.03 \times 10^{-3} \text{ V}$$

$$R_0 = \frac{RS}{R+S} + \frac{PQ}{P+Q} = \frac{2005 \times 200}{2005+200} + \frac{1000 \times 100}{1000+100} = 272.8 \Omega$$


$$I_g = \frac{E_0}{R_0+G} = \frac{1.03 \times 10^{-3}}{272.8+100} = 2.77 \mu\text{A}$$

Deflection of the gal. ;  $\theta = S_i I_g = 10 \times 2.77 = 27.7 \text{ mm}/\Omega$

Sensitivity of bridge ;

$$S_B = \frac{\theta}{\Delta R} = \frac{27.7}{5} = 5.54 \text{ mm}/\Omega$$

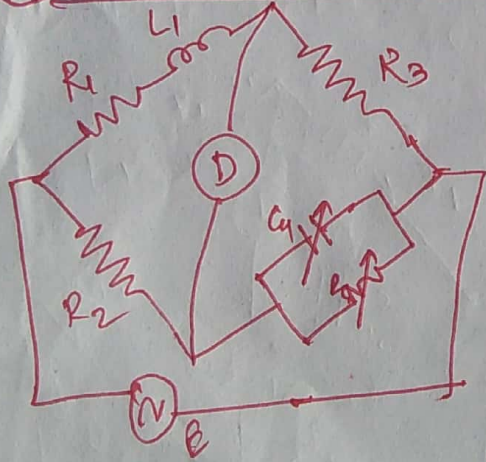5) Maxwell's Inductance-Capacitance Bridge



$$R_1 = \frac{R_2 R_3}{R_4}$$

$$L_1 = C_4 R_2 R_3$$

$$E_1 = I_1 R_1 + I_1 j \omega L_1$$

$$E_2 = I_2 R_2$$

$$E_3 = I_3 R_3$$

$$E_4 = I_4 R_4 = \frac{I_C}{j \omega C_4}$$

