



USN

--	--	--	--	--	--	--	--	--	--

10EC46

Fourth Semester B.E. Degree Examination, Dec.2019/Jan.2020

Linear ICs and Applications

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Define the following parameters and mention their typical values for 741 op-amp:
(i) CMRR (ii) Slew rate (iii) Input off set voltage (06 Marks)
- b. Explain the methods of dealing with input offset voltage and current of an op-amp.(05 Marks)
- c. The difference of two input signals is to be amplified by a factor of 37. Each input has an amplitude of 50 mV. Using a LF353 op-amp design a suitable circuit. (05 Marks)
- d. A 741 op-amp uses a $\pm 15V$ supply with a 2 mV, 120 Hz ripple voltage super imposed. Calculate the amplitude of the output voltage produced by the power supply ripple. Assume $PSRR = 30 \mu V/V$. (04 Marks)
- 2 a. Compare direct coupled and capacitor coupled op-amp circuits. (04 Marks)
- b. Explain the method of increasing the input impedance of a non-inverting amplifier with necessary derivation. (08 Marks)
- c. Design an capacitor coupled inverting amplifier using a 741 op-amp for $A_v = 50$, $V_o = 2.5 V$, $R_L = 250 \Omega$ and to have a signal frequency range of 10 Hz to 1 kHz. Assume $I_{B(max)} = 0.5 \mu A$ for 741 op-amp. (08 Marks)
- 3 a. Explain the slew rate effect on output pulse rise time and amplitude. (06 Marks)
- b. Determine the upper cut off frequency for:
(i) a voltage follower circuit using a 741 op-amp (06 Marks)
(ii) a unity gain inverting amplifier using a 741 op-amp. (06 Marks)
- c. Sketch a circuit to show the Z_{in} mod method of frequency compensation and explain its operation. (08 Marks)
- 4 a. Compare the performance of a differential input-output amplifier with difference amplifier and draw the circuit of both. (06 Marks)
- b. Draw the circuit diagram of a precision FWR using precision HWR and Summing circuit and explain its operation. (08 Marks)
- c. What is the problem associated with simple voltage source? With the circuit, explain how it is overcome by precision voltage source. (06 Marks)

PART – B

- 5 a. Describe the working of a sample and hold circuit. (06 Marks)
- b. Explain how op-amp can be used as a log amplifier and also discuss saturation current and temperature compensation. (08 Marks)
- c. Design a RC phase shift oscillator for an output frequency of 3.5 kHz. Assume supply of $\pm 12 V$ and $I_1 = 50 \mu A$. (06 Marks)

- 6 a. Explain the operation of a inverting Schmitt triggering circuit using two diodes gives different UTP and LTP. (08 Marks)
- b. Design an op-amp Astable Multivibrator to have an output frequency of 400 Hz. Use a 741 op-amp with supply of $\pm 18V$. Assume (UTP) = 0.5V, $R_2 = 1M\Omega$ and $C_1 = 0.1 \mu F$. (08 Marks)
- c. Mention the advantages of Active filter over passive filters. (04 Marks)
- 7 a. What are the advantages of IC voltage regulators? (04 Marks)
- b. Using 7805 IC design a current source to deliver 0.2 A current to a 22Ω , 10 W load. Assume $I_Q = 4.2 \text{ mA}$. (06 Marks)
- c. How is current boosting achieved in a 723 IC? (06 Marks)
- d. Mention the advantages of switching regulators. (04 Marks)
- 8 a. Design a 555 astable multivibrator to operate at 5 kHz with a duty cycle of 40%. Assume $c = 0.01 \mu F$. (08 Marks)
- b. Draw the block diagram of the PLL and explain the functions of each block. (08 Marks)
- c. The basic step of a 9-bit DAC is 10.3 mV. If 000 000 000 represents 0V. What output is produced if the input is 101101111? (04 Marks)
