

USN

--	--	--	--	--	--	--	--	--	--

10EC63

Sixth Semester B.E. Degree Examination, Dec.2019/Jan.2020
Microelectronics Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO full questions from each part.

PART – A

- 1 a. Derive an expression for drain to source current from I-V characteristics for cut-off, triode and saturation regions of MOSFET. (12 Marks)
- b. For a $0.8\mu\text{m}$ process technology with aspect ratio 10, $t_{\text{ox}} = 8\text{nm}$, $\mu_n = 450 \times 10^8 \mu\text{m}^2/\text{vs}$ and $v_t = 0.7\text{V}$
 - i) Find C_{ox} and K'_n
 - ii) Calculate the value of V_{GS} and $V_{\text{DS}(\text{min})}$ needed to operate the transistor in the saturation region with a dc current $I_D = 100\mu\text{A}$.
 - iii) For the device to operate as 1000Ω resistor, find the values of V_{GS} required for very small V_{DS} . (08 Marks)
- 2 a. Consider a CS amplifier which has $g_m = 2\text{MA/V}$, $r_o = 50\text{K}\Omega$, $R_D = 10\text{K}\Omega$, $R_G = 10\text{M}\Omega$, $R_L = 20\text{K}\Omega$ and $R_{\text{sig}} = 500\text{K}\Omega$. Calculate R_{in} , G_v , A_v , A_{v_o} and R_{out} . (10 Marks)
- b. Explain any three types of biasing methods in MOS amplifier circuits. (10 Marks)
- 3 a. Explain the operation of MOS current steering circuit and mention its advantages. (10 Marks)
- b. Explain the two different types of scaling process of MOSFET in detail. (10 Marks)
- 4 a. Explain the CMOS implementations of CS amplifiers, also draw its I-V characteristics of active load and determine its small signal voltage gain. (10 Marks)
- b. Explain the circuit of MOS cascade amplifiers and hence obtain an expression for short circuit transconductance. (10 Marks)

PART – B

- 5 a. Explain the operation of a MOS differential pair with common mode input voltage. (08 Marks)
- b. Explain the operation of a two stage CMOS Op-Amp configuration. (06 Marks)
- c. A MOS differential pair operated at a bias current of 0.8mA employs a transistors with $W/L = 10$ and $\mu_n c_{\text{ox}} = K'_n = 0.2\text{mA/V}^2$ using $R_D = 5\text{K}\Omega$ and $R_{\text{SS}} = 25\text{K}\Omega$. Find the differential gain, the common mode gain and the common mode rejection ratio (in dB) if the output is taken single ended and the circuit is perfectly matched. (06 Marks)
- 6 a. Explain the general structure of feedback amplifiers and also explain the properties of negative feedback. (08 Marks)
- b. With relevant circuits of series-shunt feedback amplifier, derive the expression for input resistance and output resistance. (08 Marks)
- c. Explain the effect of feedback on the amplifier poles. (04 Marks)

1 of 2

24 JAN 2020

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

10EC63

- 7 a. Draw the sample and hold circuit using Op-Amp and explain it. (09 Marks)
b. With neat circuit diagram, explain antilog amplifiers. (06 Marks)
c. Design a non-inverting amplifier with a gain of 2 at the maximum output voltage of 10V and the current in the voltage divider to be $10\mu\text{A}$. (05 Marks)
- 8 a. Explain the pull-up and pull-down networks used in CMOS logic circuits. (08 Marks)
b. Explain the dynamic operation of a CMOS inverter. (06 Marks)
c. Implement $F = \overline{AB + CD}$ using AOI. (06 Marks)

* * * * *

24 JAN 2020