



10EE751

Seventh Semester B.E. Degree Examination, Dec.2019/Jan.2020

HVDC Transmission

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Compare AC and DC transmission on the basis of (i) Economics of transmission and (ii) Stability of the system. (10 Marks)
b. With a neat sketch, explain the HDVC links and why the bipolar line is commonly used. (10 Marks)
- 2 a. Draw the schematic diagram of typical HVDC converter station and explain the function of each component. (10 Marks)
b. With relevant figures, explain the constitution of EHV-AC and HVDC links. (10 Marks)
- 3 a. Explain three phase two way rectifier circuit with waveform and obtain:
i) Average of direct voltage
ii) Peak-peak ripple
iii) PIV
iv) Aggregate valve rating
v) VI rating of transformer primary and secondary (14 Marks)
b. Write any three properties of converter circuits. (06 Marks)
- 4 a. Write brief note on “six pulse rectifier”. Mention its performance parameters. (10 Marks)
b. Which is the best suited circuit for HVDC transmission? Why? (04 Marks)
c. Draw the schematic and waveforms of twelve pulse rectifier. (06 Marks)

PART – B

- 5 a. Derive an expression for average DC voltage in Graetz circuit with an overlap of less than 60 degrees. (10 Marks)
b. Draw the equivalent circuits of inverter and write the equations for average of direct current and voltage interms of β and γ . (10 Marks)
- 6 a. Discuss constant current versus constant voltage control in DC transmission line. (05 Marks)
b. Enumerate the desired features of control for a HVDC converter station. (08 Marks)
c. Explain various forms of grid pulses. (07 Marks)
- 7 a. Explain constant extinction angle control with the help of schematic and necessary equations. (10 Marks)
b. Describe combined characteristics of Rectifier and Inverter. (10 Marks)
- 8 a. Explain the functions of Smoothing Reactor. (06 Marks)
b. Explain the current oscillations and applications of anode dampers. Why damper is less effective if it is connected to cathode side? Explain. (10 Marks)
c. Explain Re-energization of DC line. (04 Marks)

FEB 4 2020

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.