

# CBCS SCHEME



USN

--	--	--	--	--	--	--	--	--	--

17EE53

## Fifth Semester B.E. Degree Examination, Dec.2019/Jan.2020 Power Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- Explain any five types of power electronics converter system and also specify the form of input and output waveform. (10 Marks)
  - With block diagram, explain the peripheral effects of power electronic equipments. (06 Marks)
  - Discuss the major industrial applications of power electronic converter circuits. (04 Marks)

OR

- Briefly explain the different types of power diodes. (08 Marks)
  - With circuit diagram and waveform explain uncontrolled single phase full wave rectifier with RL load. (08 Marks)
  - Compare the advantages and disadvantages of bridge rectifier and rectifier with center tapped transformer. (04 Marks)

### Module-2

- With neat circuit diagram, explain steady state and switching characteristics of power MOSFET. (12 Marks)
  - A BJT is specified to have  $\beta$  in the range 8 to 40 load resistance  $R_C = 11\Omega$ , the DC supply voltage is  $V_{CC} = 200\text{volts}$  and the input voltage to the base circuit is  $V_{BB} = 10\text{ volts}$ . If  $V_{CE(\text{sat})} = 1\text{ volt}$  and  $V_{BE(\text{sat})} = 1.5\text{ volt}$ , find:
    - The value of  $R_B$  that result in saturation with an ODF of 5.
    - The forced  $\beta$  value and
    - Power loss in the transistor. (08 Marks)

OR

- With necessary waveform explain the switching characteristics of IGBT. (06 Marks)
  - Discuss the importance of providing isolation of gate/base drive from power circuits and explain the two methods. (06 Marks)
  - Sketch the structure of n-channel enhancement type MOSFET and explain its working principle. (08 Marks)

### Module-3

- Explain the V-I characteristics of SCR also define : i) Holding current ii) Latching current. (06 Marks)
  - Explain different methods of turning ON of thyristor. (08 Marks)
  - For the circuit shown in Fig.Q5(c). If the latching current is 4mA calculate the minimum width of gate pulse required properly turn ON the SCR. (06 Marks)

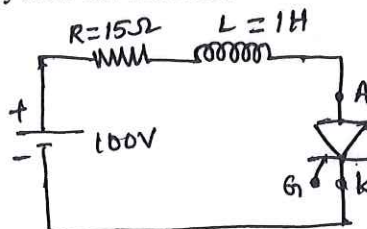


Fig.Q5(c)

1 of 2

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

11 JAN 2020

OR

- 6 a. Derive an expression for the anode current of thyristor with the help of two transistor analogy. (10 Marks)  
 b. With circuit diagrams and waveforms, explain the methods of protection of SCR. (10 Marks)

**Module-4**

- 7 a. With the help of circuit diagram and wave forms, explain the working of single – phase full converter with R–L load. (10 Marks)  
 b. A single phase full wave AC voltage controller has an input voltage of 230V and load resistance of  $10\Omega$ . The firing angle is  $45^\circ$ , calculate :  
 i) RMS output voltage  
 ii) The output power  
 iii) The input power factor. (10 Marks)

OR

- 8 a. With circuit diagram and waveforms explain  $1\phi$  dual converter. (10 Marks)  
 b. With circuit diagram and waveform, explain the operation of  $3\phi$  full converters. (10 Marks)

**Module-5**

- 9 a. Explain the working of step-up chopper. Draw the relevant waveforms, derive an expression for average output voltage. (08 Marks)  
 b. Write a note on performance parameters of chopper. (04 Marks)  
 c. A stepdown chopper with resistive load has a resistive load of  $10\Omega$  and the input voltage is  $V_s = 220V$ . When the converter switch remains ON its voltage drop is 2V and the chopping frequency is  $f = 1KHz$ , if the duty cycle is 50% determine :  
 i) Average output voltage  
 ii) RMS output voltage  
 iii) Chopper efficiency  
 iv) Effective input resistance. (08 Marks)

OR

- 10 a. With circuit diagram, explain the operation of a single phase–full bridge inverter supplying a resistive load. (10 Marks)  
 b. Explain any two modulation technique available for voltage control of a single phase inverter. (10 Marks)

\*\*\*\*\*