

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17ELN15/25

First/Second Semester B.E. Degree Examination, Dec.2019/Jan.2020

Basic Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- a. Define the following diode parameters :
i) Static resistance ii) Dynamic resistance iii) Reverse saturation current
iv) Peak Inverse voltage v) Knee voltage. (05 Marks)
- b. With circuit diagram and neat sketch, explain the common base input and output characteristics for pnp transistor. (08 Marks)
- c. A full wave rectifier with a transformer secondary voltage $60V - 0 - 60V$, supplies a load resistance $R_L = 2k\Omega$. The diode forward resistance R_f is 10Ω . Determine
i) maximum value of current in conducting diodes ii) dc value of current through R_L
iii) output dc voltage and iv) PIV across each diode. (07 Marks)

OR

- a. With a neat circuit diagram and waveforms, explain the working of Bridge rectifier. (08 Marks)
- b. A 9V reference source is to use a series connected zener diode and a resistor connected to 30V supply. If zener diode with $V_Z = 9V$, $I_{ZT} = 20mA$ is selected, then determine the value of series resistance and calculate the circuit current when the supply voltage drops to 27V. (05 Marks)
- c. Define Common – base current gain and Common – emitter current gain of transistor. Derive the relationship between them. If a transistor has $I_C = 3mA$, $I_E = 3.03mA$, then find β of transistor. (07 Marks)

Module-2

- a. With circuit diagram and necessary equations, explain the base bias circuit. (05 Marks)
- b. For the voltage divider bias circuit using silicon transistor, $V_{cc} = 18V$, $R_1 = 33K\Omega$, $R_2 = 12K\Omega$, $R_c = 1.2K\Omega$ and $R_E = 1K\Omega$. Using approximate analysis, determine V_E , V_C , V_B , I_C and V_{CE} . (08 Marks)
- c. With a neat circuit diagram, derive an equation for output voltage of non inverting amplifier using op - amp. (07 Marks)

OR

- a. For the circuit shown in fig.Q4(a), find the Q – point values and draw the dc load line. The transistor has $V_{BE} = 0.7V$ and $\beta = 50$. (07 Marks)

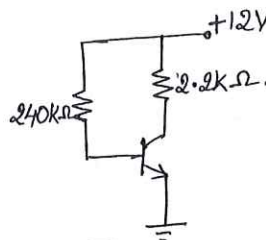
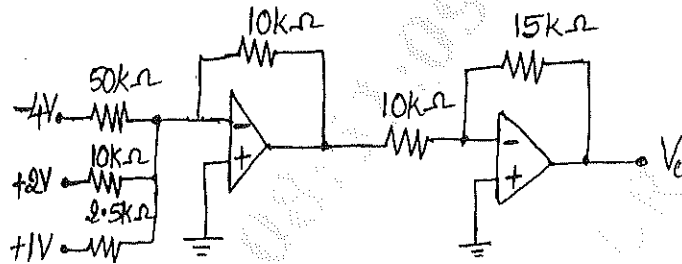


Fig.Q4(a)

- b. Mention the characteristics of ideal op – amp. (05 Marks)
 c. Calculate the output voltage for the circuit shown in fig:Q4(c). (08 Marks)

Fig.Q4(c)

**Module-3**

- 5 a. Convert the following : i) $(283.728)_{10} = (?)_8$. ii) $(AB.5E)_{16} = (?)_8$. (06 Marks)
 b. Simplify $Y = \bar{A}BC + A\bar{B}C + ABC$ and then realize using
 i) basic gates only ii) NOR gates only. (08 Marks)
 c. Explain half adder circuit and realize using basic gates. (06 Marks)

OR

- 6 a. Subtract i) $(1011)_2 - (110)_2$ using 1's complement
 ii) $(1001)_2 - (1110)_2$ using 2's complement. (06 Marks)
 b. Draw the symbol and write the truth table of the exclusive – NOR gate and EX – OR gate.
 Realize the same using basic gates also. (06 Marks)
 c. Simplify the following Bodean expressions :
 i) $Y = A + \bar{A}B + ABC + A\bar{C}$ ii) $Y = (A + \bar{B} + \bar{C})(A + \bar{B} + C)$.
 and realize using basic gates. (08 Marks)

Module-4

- 7 a. What is flipflop? Explain the operation of clocked RS flip flop. (06 Marks)
 b. Explain the operation of NOR gate latch. (06 Marks)
 c. With a neat block diagram, describe 8051 microcontroller. (08 Marks)

OR

- 8 a. Explain the operation of NAND gate latch. (05 Marks)
 b. List the salient features of 8051 micro controller. (07 Marks)
 c. Interface stepper motor to 8051 microcontroller with a neat block diagram. Explain its working principle, full step and half step sequence. (08 Marks)

Module-5

- 9 a. Explain the block diagram of communication system. (06 Marks)
 b. The total power content of an AM wave is 2.64KW at a modulation index of 80%.
 Determine the power content of i) carrier ii) each sideband. (04 Marks)
 c. Write a note on i) thermistor ii) photo electric transducer. (10 Marks)

OR

- 10 a. Give a comparison of AM and FM. (06 Marks)
 b. With a neat circuit diagram, explain the demodulation of AM signal. (06 Marks)
 c. Give the classification of transducers. Also mention the desirable properties of a good transducer. (08 Marks)
