

--	--	--	--	--	--	--	--	--	--	--

Internal Assessment Test - I


Sub:	OPERATIONAL AMPLIFIERS AND LINEAR ICs						Code:	15EE46	
Date:	13/03/2018	Duration:	90 mins	Max Marks:	50	Sem:	4 TH	Branch:	EEE

Answer Any FIVE FULL Questions

		Marks	OBE	
			CO	RBT
1	With a block diagram explain the different stages of a typical Operational amplifier. Define slew rate, CMRR and input offset voltage.	10	CO1	L2
2	Derive the expression for closed loop gain, Ideal closed loop gain, Input resistance and output resistance of a voltage series feedback amplifier with circuit diagrams.	10	CO1	L2
3	Demonstrate an Instrumentation amplifier with transducer bridge input. Derive the expression of output voltage for the same.	10	CO1	L2
4	Design a two stage wide band pass filter and band reject filter having $f_L=200\text{Hz}$ and $f_H=1\text{kHz}$ and pass band gain of 4. Calculate Q value and center frequency. Assume capacitor values for high pass section=0.05uF and for the low pass section=0.01uF. Draw the circuit diagram.	10	CO6	L3
5	For the second order LPF, show that the pass band voltage gain is equal to 1.586 and also obtain the expression for high cut off frequency f_H . Draw the circuit diagram.	10	CO6	L2
6	A peaking amplifier has the following values $R_1=1\text{k}\Omega$, $L=100\mu\text{H}$ with a 3Ω internal resistance. Given $C=0.01\mu\text{F}$, $R_F=6.8\text{k}\Omega$, and $R_L=10\text{k}\Omega$. Determine (a) the peak frequency f_p , (b) the gain of the amplifier at f_p and the bandwidth of the amplifier.	10	CO1	L3
7	Design a first order and second order Low pass Butterworth filter with cut off frequency 1.2kHz.	10	CO6	L3
8	Explain how an Op-amp can be used as a non-inverting summer and subtractor.	10	CO1	L2

Solution

1.

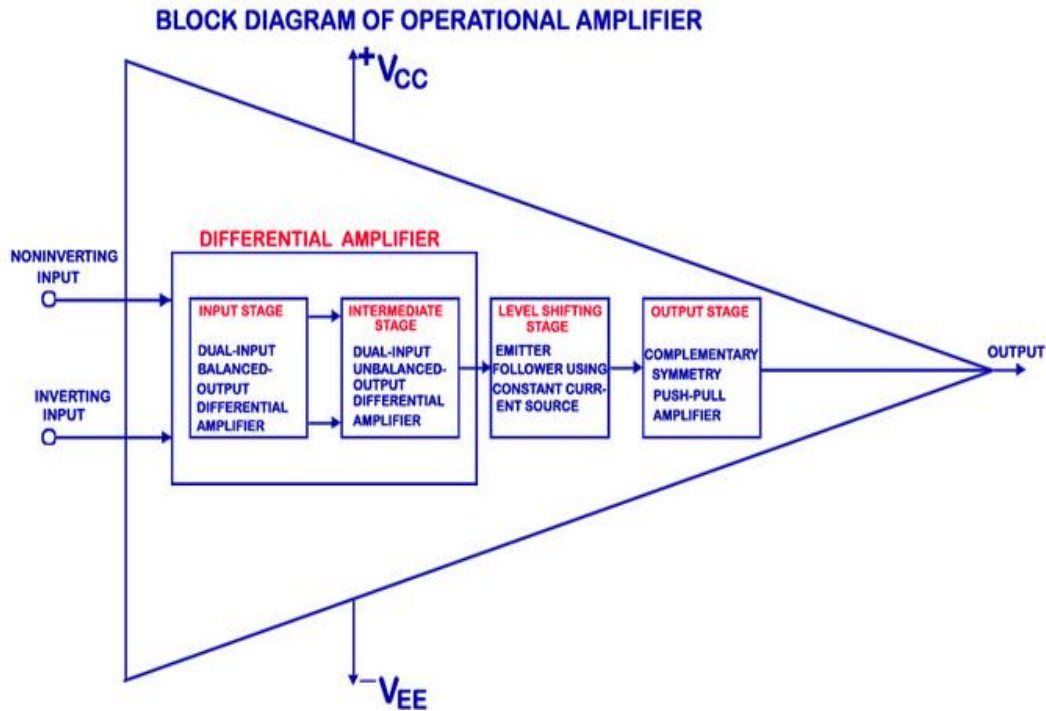

(4 marks)

Slew Rate : The slew rate is the maximum rate of change of output voltage caused by a step input voltage and is usually specified in $V/\mu S$. For example $1V/\mu S$ slew rate means that the output rises or falls by 1V in one microseconds. Ideally slew rate is infinite which means that op-amp's output should be changed instantaneously in response to input step voltage. Practical op-amps are available with slew rates from $0.1V/\mu S$ to well above $1000V/\mu S$.


CMRR : It can be defined as the ratio of the differential gain A_D to the common mode gain A_{CM} that is, $CMRR = A_D/A_{CM}$.

Input Offset Voltage Defined. The **input offset voltage** is defined as the **voltage** that must be applied between the two **input** terminals of the **op amp** to obtain zero volts at the output. (2+2+2 marks)

2.

(1) Voltage - series feedback amplifier

7

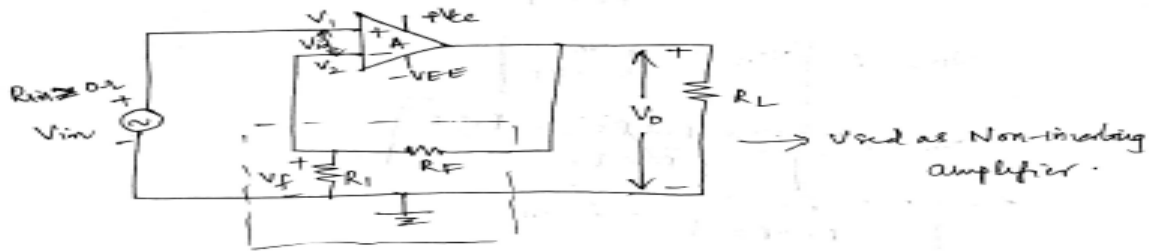

open loop voltage gain $(A = \frac{V_o}{V_{id}})$
 closed loop voltage gain $A_F = \frac{V_o}{V_{in}}$
 gain of feedback circuit $B = \frac{V_f}{V_o}$

Negative feedback

$V_{id} = V_{in} - V_f$
 $V_{in} \rightarrow$ input voltage V_f - feedback voltage $V_{id} =$ diff. \uparrow p.v.
 feedback always like input voltage (180°).

closed loop voltage gain

$$A_F = \frac{V_o}{V_{in}} \quad V_o = A(V_{in} - V_f)$$

from fig $V_i = V_{in}$

$$V_o - V_f = V_o \times \frac{R_I}{R_I + R_F}$$

$$V_o = A \left[V_{in} - \frac{R_I V_o}{R_I + R_F} \right]$$

$$V_o = \frac{A}{A} \left[\frac{V_{in}(R_I + R_F) - R_I V_o}{R_I + R_F} \right]$$

$$V_o \left[1 + \frac{R_I}{R_I + R_F} \right] = A V_{in}$$

$$V_o = \frac{A(R_I + R_F) V_{in}}{R_I + R_F + A R_I}$$


$$A_F = \frac{V_o}{V_{in}} = \frac{A(R_I + R_F)}{R_I + R_F + A R_I}$$

A is very large (10^5)

$$A R_I \gg (R_I + R_F) \quad \text{so} \quad R_I + R_F + A R_I \approx A R_I$$

$$A_F = \frac{V_o}{V_{in}} = \frac{A(R_I + R_F)}{A R_I} = \frac{1 + R_F/R_I}{1} \quad (\text{Ideal})$$

Input resistance with feedback

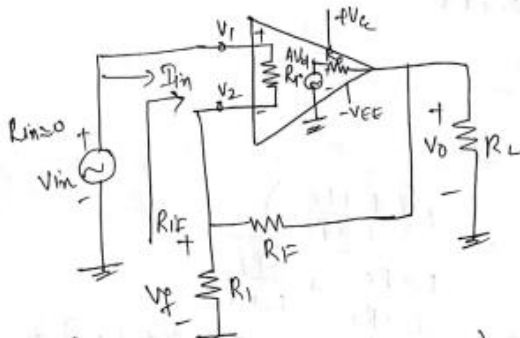

R_i is \uparrow resistance (open-loop)
 R_{iF} = input resistance with feedback.

$$R_{iF} = \frac{v_{in}}{I_{in}} = \frac{v_{in}}{(v_{id}/R_i)}$$

$$v_{id} = \frac{v_o}{A} \quad v_o = \frac{A}{1+AB} v_{in}$$


~~$$R_{iF} = \frac{v_{in}}{\frac{v_o}{A}}$$~~

$$R_{iF} = \frac{v_{in}}{\frac{v_o}{A} \times \frac{1}{R_i}}$$

$$R_{iF} = A R_i \cdot \frac{v_{in}}{v_o}$$

$$= A R_i \cdot \frac{v_{in}}{\frac{A}{1+AB} v_{in}}$$

$$R_{iF} = R_i (1+AB)$$

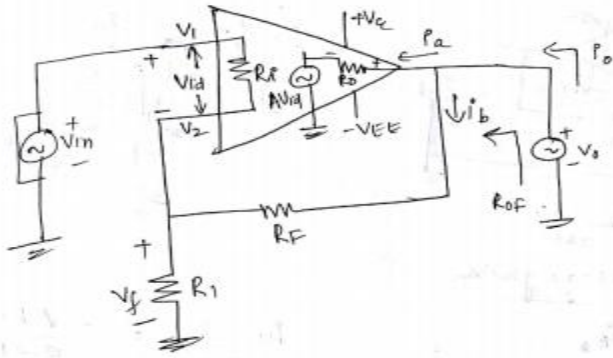

$$R_{of} = \frac{v_0}{i_0} \quad P_o = i_a + i_b$$

$$[(R_f + R_1) \parallel R_i] \gg R_o \quad i_a \gg i_b$$

$$i_0 \approx i_a \quad v_0 - R_o i_0 - A v_{id} = 0$$


$$i_0 = \frac{v_0 - A v_{id}}{R_o}$$

$$v_{id} = v_1 - v_2 = 0 - v_f = -\frac{R_1 v_0}{R_1 + R_f} = -B v_0$$

$$i_0 = \frac{v_0 + AB v_0}{R_o}$$

$$R_{of} = \frac{v_0}{(v_0 + AB v_0) / R_o} = \frac{R_o}{1 + AB}$$

3

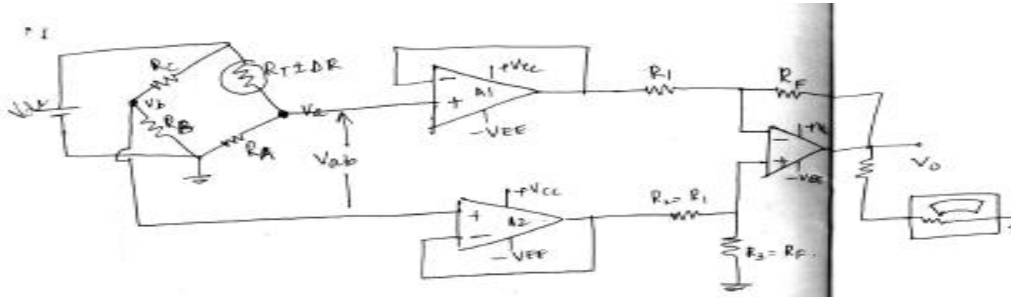

Resistance changes as physical energy
 $R_T \pm \Delta R$

$$V_a = V_b$$

$$\frac{R_b \cdot V_{dc}}{R_b + R_c} = \frac{R_a \cdot V_{dc}}{R_a + R_T}$$

$$R_b (R_a + R_T) = \frac{R_a}{R_T} (R_b + R_c)$$

$$R_a R_b + R_b R_T = R_a R_b + R_a R_c$$

$$R_b R_T = R_a R_c$$

$$\boxed{\frac{R_c}{R_b} = \frac{R_T}{R_a}}$$

When resistance changes

V_a

$$V_a = \frac{R_a \cdot V_{dc}}{R_a + (R_T + \Delta R)}$$

15

$$V_b = \frac{R_b \cdot V_{dc}}{R_b + R_c}$$

$$V_a \approx V_b = V_{ab} = V_a - V_b$$

$$V_{ab} = \frac{R_a \cdot V_{dc}}{R_a + R_T + \Delta R} - \frac{R_b \cdot V_{dc}}{R_b + R_c}$$

$$R_a = R_b = R_c = R_T = R$$

$$V_{ab} = \frac{R \cdot V_{dc}}{R + R + \Delta R} - \frac{R \cdot V_{dc}}{R + R}$$

$$\frac{R \cdot V_{dc}}{2R + \Delta R} - \frac{R \cdot V_{dc}}{2R}$$

$$= R \cdot V_{dc} \left[\frac{2R - 2R - \Delta R}{2R(2R + \Delta R)} \right]$$

$$= R \cdot V_{dc} \left[\frac{-\Delta R}{2R(2R + \Delta R)} \right] = - \left[\frac{\Delta R \cdot V_{dc}}{2(2R + \Delta R)} \right]$$

$$V_o = V_{ab} \left(\frac{-R_F}{R_i} \right) = \left(\frac{-R_F}{R_i} \right) \left(\frac{-\Delta R \cdot V_{dc}}{2(2R + \Delta R)} \right)$$

$$2R + \Delta R \approx 2R \quad V_o \approx \frac{R_F}{R_i} \frac{\Delta R}{4R} V_{dc}$$

$$\boxed{V_o < \Delta R}$$

4.

$$4) \quad f_L = 200 \text{ Hz} \quad f_H = 1 \text{ kHz} \quad A_V = 4$$


$$C_1 = 0.05 \mu\text{F} \quad C_2 = 0.01 \mu\text{F}$$

$$f_L = \frac{1}{2\pi R_1 C_1} \quad R_1 = \frac{1}{2\pi f_L C_1} = \frac{1}{2\pi \times 200 \times 0.05 \mu\text{F}}$$

$$= 15.91 \text{ k}\Omega$$

$$f_H = \frac{1}{2\pi R_2 C_2} \quad R_2 = \frac{1}{2\pi f_H C_2} = \frac{1}{2\pi \times 1 \times 10^3 \times 0.01 \times 10^{-6}}$$

$$= 15.91 \text{ k}\Omega$$

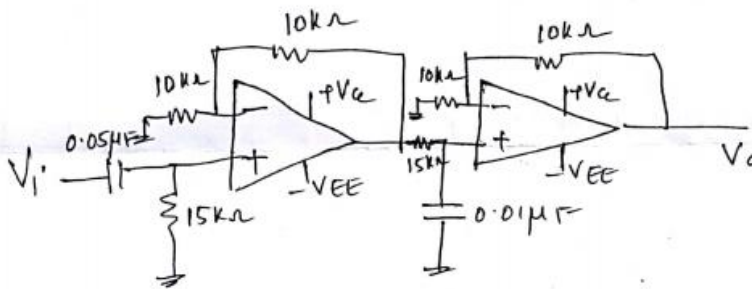

5.

For deriving the expression for the cut-off frequency, let us use the Laplace transform method.

The input RC network can be represented in the Laplace domain as shown in Fig. 2.6.2.

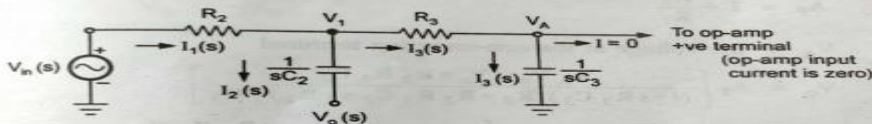


Fig. 2.6.2

$$I_1 = I_2 + I_3 \quad \dots (2.6.1)$$

$$\frac{V_{in} - V_1}{R_2} = \frac{V_1 - V_o}{\left(\frac{1}{sC_2}\right)} + \frac{V_1 - V_A}{R_3} \quad \dots (2.6.2)$$

Using potential divider rule, we can write,

$$V_A = V_1 \left[\frac{\frac{1}{sC_3}}{R_3 + \frac{1}{sC_3}} \right] \quad \dots (2.6.3)$$

$$V_A = \frac{V_1}{1 + sR_3 C_3}$$

$$V_1 = V_A (1 + sR_3 C_3)$$

Substituting in (2.6.2) and solving for V_A , we get

$$\frac{V_{in} - V_A (1 + sR_3 C_3)}{R_2} = \frac{V_A (1 + sR_3 C_3) - V_o}{\left(\frac{1}{sC_2}\right)} + \frac{V_A (1 + sR_3 C_3) - V_A}{R_3}$$

$$\frac{V_{in}}{R_2} + V_o (sC_2) = V_A \left[\frac{(1 + sR_3 C_3)}{R_2} + sC_2 (1 + sR_3 C_3) + \frac{(1 + sR_3 C_3)}{R_3} \right]$$

$$\therefore \frac{V_{in}}{R_2} + V_o (sC_2) = V_A \left[\frac{R_3 (1 + sR_3 C_3) + R_2 R_3 s C_2 (1 + sR_3 C_3) + R_2 (1 + sR_3 C_3) - R_2}{R_2 R_3} \right]$$

$$\therefore (R_2 V_{in} + V_o s R_2 R_3 C_2) = V_A [(1 + sR_3 C_3) (R_3 + R_2 R_3 s C_2 + R_2) - R_2]$$

$$V_A = \frac{R_2 V_{in} + V_o s R_2 R_3 C_2}{[(1 + sR_3 C_3) (R_3 + R_2 R_3 C_2 s + R_2) - R_2]} \quad \dots (2.6.1)$$

Now, for op-amp in non-inverting configuration,

$$V_o = A_F V_A \quad \dots (2.6.2)$$

where $A_F = 1 + \frac{R_f}{R_1}$

and $V_A =$ the voltage at the non-inverting terminal

$$V_o = A_F \left[\frac{R_3 V_{in} + V_o s R_2 R_3 C_2}{(1 + sR_3 C_3) (R_3 + R_2 R_3 C_2 s + R_2) - R_2} \right]$$

$$\frac{A_F R_3 V_o}{(1 + sR_3 C_3) (R_3 + R_2 R_3 C_2 s + R_2) - R_2} = V_o \left[1 - \frac{s R_2 R_3 C_2}{(1 + sR_3 C_3) (R_3 + R_2 R_3 C_2 s + R_2) - R_2} \right]$$

$$A_F R_3 V_{in} = V_o [(1 + sR_3 C_3) (R_3 + R_2 R_3 C_2 s + R_2) - R_2 - s R_2 R_3 C_2]$$

$$\frac{V_o}{V_{in}} = \frac{A_F}{s^2 + \frac{(R_3 C_3 + R_2 C_2 + R_2 C_2 - A_F R_2 C_2) s}{R_2 R_3 C_2 C_3} + \frac{1}{R_2 R_3 C_2 C_3}} \quad \dots (2.6.3)$$

As the order of s in the gain expression is two, the filter is called **second order filter**. The standard form of the transfer function of any second order system is

$$\frac{V_o(s)}{V_{in}(s)} = \frac{A}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

Note: For $R_2 = R_3 = R$ and $C_2 = C_3 = C$, the transfer function takes the form

$$\frac{V_o(s)}{V_{in}(s)} = \frac{A_F}{s^2 + \frac{3 - A_F}{RC} s + \frac{1}{R^2 C^2}} \quad \dots (2.6.12)$$

From this we can write that,

$$\xi = \text{damping factor} = \frac{3 - A_F}{2} \quad \dots (2.6.13)$$

Now, for second order Butterworth filter, the middle term required is $\sqrt{2} = 1.414$, from the normalised Butterworth polynomial.

$$3 - A_F = \sqrt{2} = 1.414$$

$$A_F = 1.586 \quad \dots (2.6.14)$$

Thus, to ensure the **Butterworth response**, it is necessary that the gain A_F is 1.586.

$$1.586 = 1 + \frac{R_f}{R_1}$$

$$R_f = 0.586 R_1 \quad \dots (2.6.15)$$

6.

Solⁿ (a) $f_p = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{10^{-4} \times 10^{-8}}} = \frac{1}{2\pi \times 10^{-6}} = \boxed{159 \text{ KHZ}}$

(b) Gain of the amplifier at f_p ,

$$A_F = -\frac{R_F \parallel R_p}{R_i} \quad \left\{ \begin{array}{l} R_p = Q_{\text{coil}}^2 \times R \\ \text{and} \end{array} \right.$$

$$\left[\begin{array}{l} * Q_{\text{coil}} = \frac{2\pi f L}{R} = \frac{2\pi \times 159 \text{ K} \times 10^{-4}}{3} \times R = Q_{\text{coil}} \} \\ = \frac{99.9}{3} \\ Q_{\text{coil}} = \underline{\underline{33.3}} \end{array} \right.$$

$$\left[\begin{array}{l} * R_p = Q_{\text{coil}}^2 \times R \\ = (33.3)^2 \times R = \\ = 1108.89 \times 3 = \underline{\underline{3.326 \text{ K}\Omega}} \end{array} \right. \quad \begin{array}{l} \text{inverting} \\ \uparrow \end{array}$$

$$A_F = - \frac{6.8 \text{ K} \times 3.3 \text{ K}}{(6.8 \text{ K} + 3.3 \text{ K})} \Big/ 1 \text{ K}\Omega = - \frac{2.22 \text{ K}\Omega}{1 \text{ K}\Omega} = \boxed{-2.22}$$

(c) $B.W = \frac{f_p}{Q_p} = \frac{159 \text{ KHZ}}{32.87}$ $\frac{R_p}{X_L} = \frac{3.3 \text{ K}}{2\pi \times 15.9}$ $Q_p = \frac{6.8 \text{ K} \times 33.032}{6.8 \text{ K} + 33.032}$

$B.W = 4.8 \text{ KHZ}$ $= 33.032$ $= 32.87$

7.

⊗) First order low pass

$$f = \frac{1}{2\pi RC}$$

$$f = 1.2 \text{ KHz}$$

$$\text{Let } C = 0.01 \mu\text{F}$$

$$C = \frac{1}{2\pi f R}$$

$$= \frac{1}{2\pi \times 1.2 \times 10^3 \times 0.01 \times 10^{-6}}$$

$$= 13 \text{ k}\Omega$$

Second order LPF



$$R_1 = R_2 = R$$

$$C_1 = C_2 = C$$


$$\text{Let } C = 0.0047 \mu\text{F}$$

$$R = \frac{1}{2\pi \times 1.2 \times 10^3 \times 0.0047 \times 10^{-6}}$$

$$= 28 \text{ k}\Omega$$

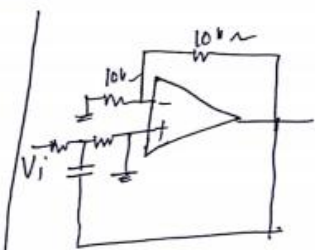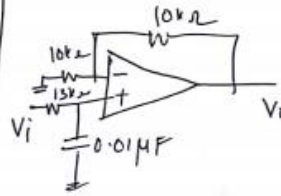

8.

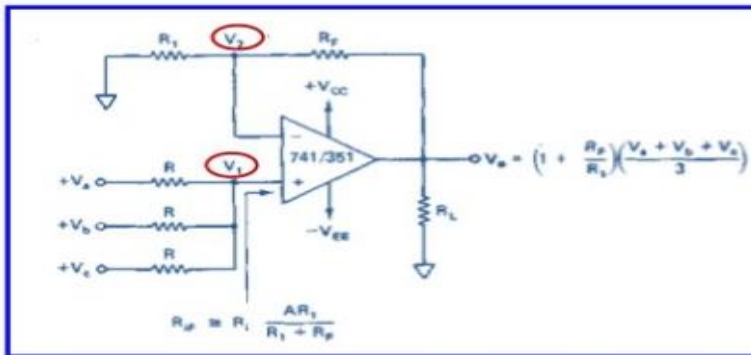

Non-inverting Summing Amplifier

Therefore, using the **superposition theorem**, the voltage $V_2 = V_1$
 V_b & $V_c = 0$. Net resistance
 $= R + R/2$

$$V_1 = \frac{R/2}{R + R/2} V_a + \frac{R/2}{R + R/2} V_b + \frac{R/2}{R + R/2} V_c$$


$$V_1 = \frac{R/2}{3R/2} V_a + \frac{R/2}{3R/2} V_b + \frac{R/2}{3R/2} V_c$$

$$V_1 = \frac{V_a}{3} + \frac{V_b}{3} + \frac{V_c}{3} = \frac{V_a + V_b + V_c}{3}$$

$$\text{If } R_f = 2R_i, 1 + R_f/R_i = 3$$

$$V_o = V_a + V_b + V_c$$

(b) Subtractor (differential amplifier).

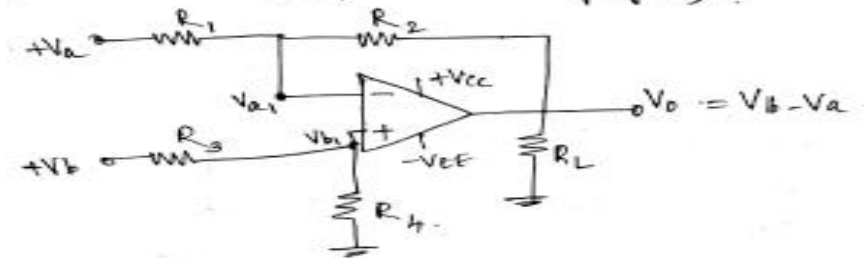

Applying superposition theorem,
considering V_a , $V_b = 0$.

$$V_{o1} = -\frac{R_2}{R_1} V_a$$

considering V_b , $V_a = 0$.

$$V_{b1} = \frac{V_b \times R_4}{R_3 + R_4}$$

$$V_{o2} = \left(1 + \frac{R_2}{R_1}\right) V_{b1} = \left(1 + \frac{R_2}{R_1}\right) \times \left(\frac{R_4}{R_3 + R_4}\right) V_b$$

$$= \left(\frac{R_1 + R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_b$$

If $R_1 = R_2$ and $R_3 = R_4$.

$$V_{o1} = -V_a \quad V_{o2} = +V_b$$

$$V_o = V_{o1} + V_{o2} = V_b - V_a$$

$$\boxed{V_o = V_b - V_a}$$