

--	--	--	--	--	--	--	--	--	--	--

Internal Assessment Test - III

Sub:	<b>OPERATIONAL AMPLIFIERS AND LINEAR ICs</b>						Code:	15EE46			
Date:	22/05/2018	Duration:	90 mins	Max Marks:	50	Sem :	4th A	Branch:	EEE		
Answer Any FIVE FULL Questions											
								Marks	OBE		
									CO	RBT	
1a	Design a triangular waveform generator to produce $\pm 2$ V, 1kHz output. Use $\pm 15$ V supply and explain the operation with help of waveforms.						10	CO5	L3		
OR											
1b	Explain the circuit of a full wave precision rectifier using half wave rectifier and summing circuit. Demonstrate the input and output waveforms.						10	CO3	L2		
2a	Design a Inverting Schmitt trigger to have $UTP=+2$ V and $LTP=-3$ V using uA741 Op-amp with supply voltage $V_{cc}=\pm 15$ V.						10	CO4	L3		
OR											
2b	Explain the working of a 4 bit R-2R ladder type DAC. An 8 bit DAC has resolution of 20mV/LSB. Find $V_{oFS}$ and $V_o$ if the input is $(10000000)_2$ .						10	CO2	L3		
3a	Demonstrate the working of a non inverting comparator with positive and negative reference voltage and voltage to current converter with floating load.						10	CO4	L2		
OR											
3b	Explain the working of successive approximation ADC and dual slope ADC with block diagram						10	CO2	L2		
4	Explain the operation of PLL with help of block diagram. Explain each block in detail.						10	CO6	L2		
5	Sketch the internal circuit diagram of 555 monostable multivibrator .Draw the required waveforms and explain its operation						10	CO6	L2		
6	Design a astable multivibrator using 555 timer for a frequency of 1kHz and duty cycle of 70%.Use $C=0.1\mu F$ .Discuss any two applications of IC555.						10	CO6	L3		

Solution

1a.

$$R_1 = \frac{V_{sat}}{I_1} = \frac{14}{100\mu A} = \frac{14}{100 \times 10^{-6}} = \frac{14}{10^{-4}} \approx 140\text{ k}\Omega \text{ (120 k}\Omega\text{)}$$

$$R_3 = R_1 = 120\text{ k}\Omega$$

$$R_2 = \frac{V_{TP}}{I_1} = \frac{2}{100\mu A} = \frac{2}{10^{-4}} = 20\text{ k}\Omega \approx \underline{\underline{18\text{ k}\Omega}}$$

$$Q = CV \quad C = \frac{Q}{V} = \frac{I_1 t}{\Delta V}$$


$$t = \frac{1}{2f} = \frac{100 \times 10^{-6} \times 500 \times 10^{-6}}{4} = 12500 \times 10^{-12}$$

$$= 500 \times 10^{-3} = 0.5 \times 10^{-3}$$

$$= 0.12500 \times 10^{-7}$$

$$= \underline{\underline{0.01\mu F}}$$

1b.

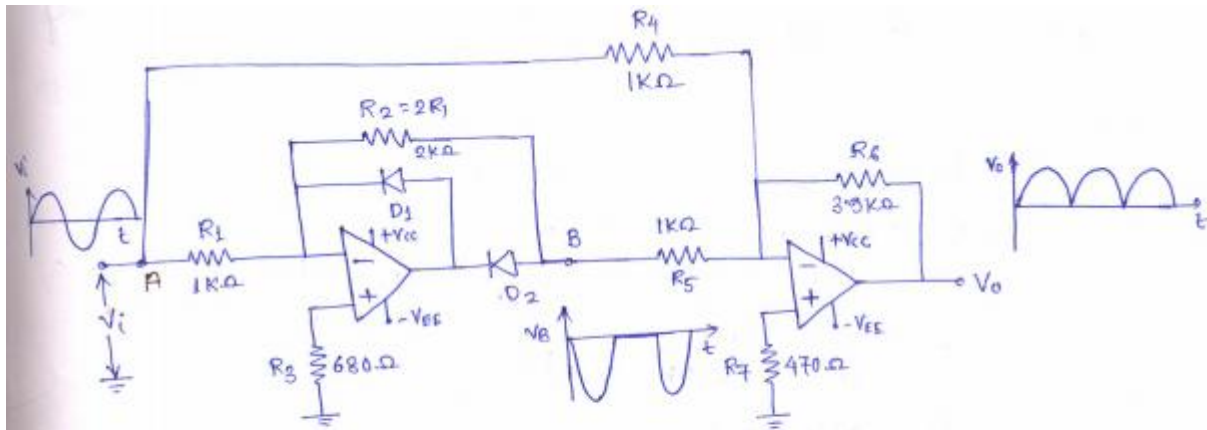

The above circuit is a combination of half-wave rectifier with gain = 2 and an inverting amplifier with gain = 3.9

The above circuit is a combination of half-wave rectifier with gain=2 and an inverting adder with gain=3.9

during +ve half-cycle

Voltage at terminal A =  $+V_i$   
 while that at terminal B is  $-2V_i$ .  
 [Diode  $D_1$  is off and  $D_2$  is on]

A4 College Book

~~output~~ The output of the summing circuit, with  $R_4 = R_5$

$$\begin{aligned} V_o &= -\frac{R_6}{R_4} (V_A + V_B) \\ &= -\frac{R_6}{R_4} (V_i - 2V_i) \\ &= -\frac{R_6}{R_4} (-V_i) = \frac{R_6}{R_4} V_i \end{aligned}$$

during -ve half-cycle

$V_A = -V_i$   
 $V_B = 0$  as  $D_1$  is on and  $D_2$  is off.

consequently the output is,

$$V_o = -\frac{R_6}{R_4} (V_A + V_B) = -\frac{R_6}{R_4} (-V_i + 0)$$

$$\boxed{V_o = +\frac{R_6}{R_4} V_i}$$


2a.

$$\begin{aligned} UTP &= +2 \\ LTP &= -3 \end{aligned}$$

$$R_1 = \frac{UTP}{I_1} = \frac{+2}{500\mu A} = 4k\Omega (3.9k\Omega)$$

$$UTP = \frac{V_o \times R_1 (V_o - V_D)}{R_1 + R_2} \Rightarrow R_2 = \underline{\underline{22k\Omega}}$$
 
$$LTP = \frac{(V_o - V_D) \times R_1}{R_1 + R_3} \Rightarrow R_3 = \underline{\underline{15k\Omega}}$$



## R-2R Ladder DAC

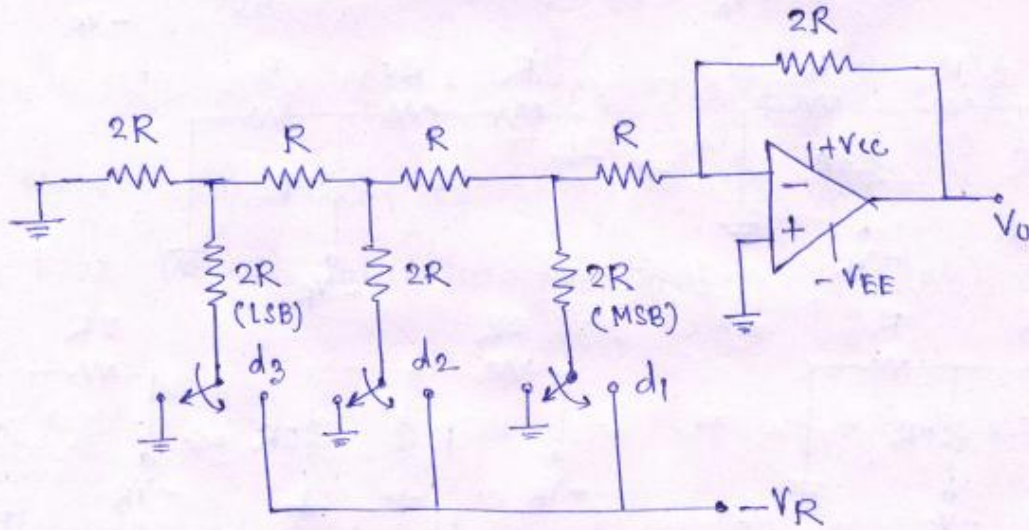


Fig- R-2R Ladder type DAC


The range for  $R$  is  $2.5\text{K}\Omega$  to  $10\text{K}\Omega$ .

For simplicity, consider a 3-bit DAC, where  $d_1, d_2, d_3$  corresponds to the binary word input to the DAC.

$-V_R$  is the reference voltage.

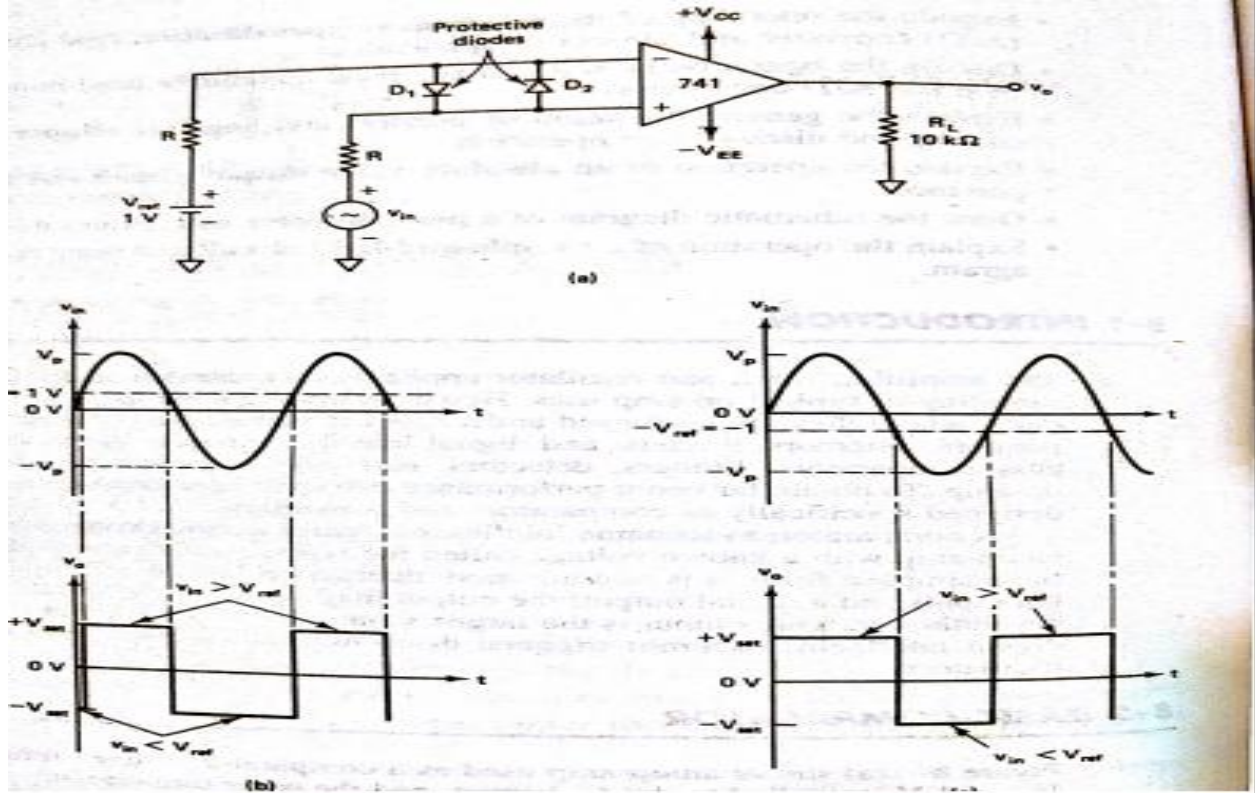
The feedback resistance is  $2R$ . The network consist of R-2R network connected with the op-amp.





3b

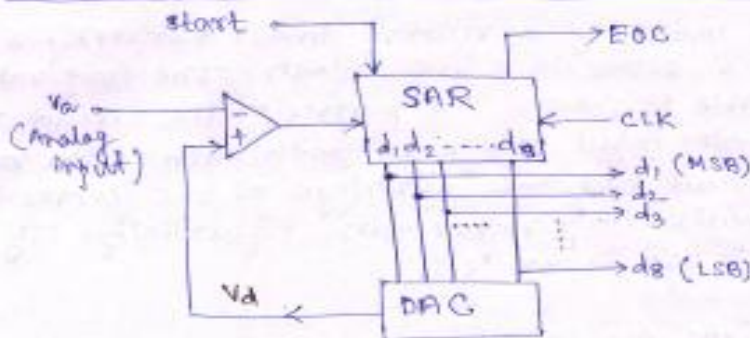Successive Approximation type A/D converter





Functional diagram of the successive approximation ADC.

The conversion sequence for a typical analog input is shown below.

correct digital representation	successive approximation resistor output $v_d$ at different stages in conversion	comparator output
11010100	10000000	1
	11000000	1
	11100000	0
	11010000	1
	11011000	0
	11010100	1
	11010110	0
	11010101	0
	11010100	

## Dual slope ADG

 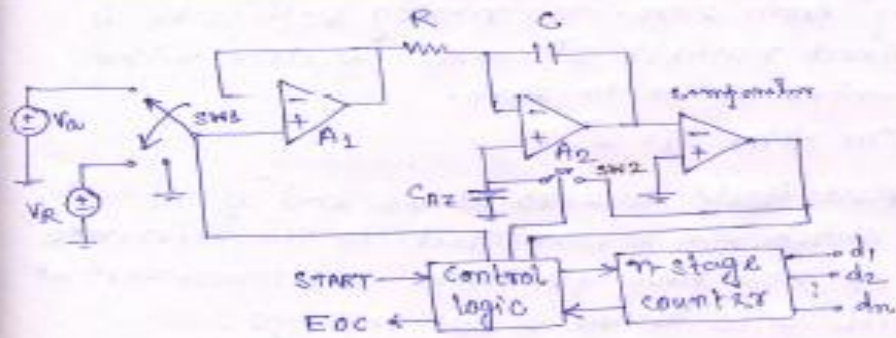


## Phase-locked loop (PLL)

Phase-locked loop is an important building block of linear systems. PLLs are available as inexpensive monolithic IC. NE565 is the IC for PLL.

### Basic principles



The basic block schematic of the PLL is shown. The feedback system consists of

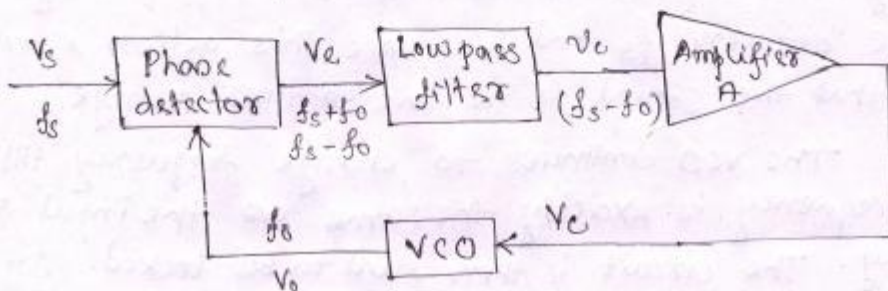- (i) Phase detector/comparator.
- (ii) A low pass filter.
- (iii) An error amplifier.
- (iv) A voltage controlled oscillator.



5.

## Monostable Multivibrator

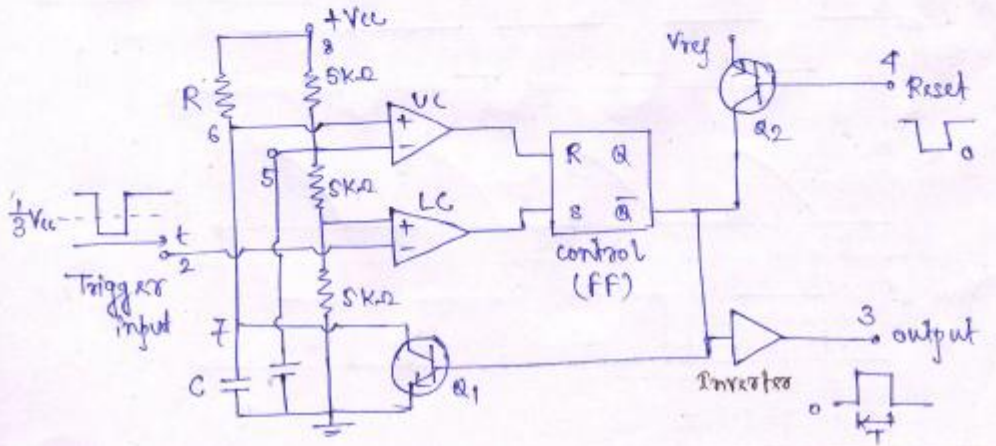 

6.

Solution

$$f = \frac{1.45}{(R_A + 2R_B)C} = 1 \times 10^3$$

$$\text{or, } (R_A + 2R_B) \times 0.1 \times 10^{-6} = \frac{1.45}{1 \times 10^3} \quad \left[ \begin{array}{l} \text{Assume select,} \\ C = 0.1 \mu\text{F} \end{array} \right]$$

$$\text{or, } R_A + 2R_B = 14.5 \times 10^3 = 14.5 \text{ K}\Omega \quad \text{--- (1)}$$

$$D = \frac{R_A + R_B}{R_A + 2R_B} = 0.6$$

$$\text{or, } R_A + R_B = 0.6 (R_A + 2R_B) = 0.6 \times 14.5 \text{ K}\Omega = 8.7 \text{ K}\Omega \quad \text{--- (2)}$$

Let, Using eq (1) and (2) we get,

$$R_B = (14.5 - 8.7) \text{ K}\Omega = 5.8 \text{ K}\Omega \approx 5.6 \text{ K}\Omega$$

$$R_A = 8.7 - 5.6 = 3.1 \text{ K}\Omega \approx 3.3 \text{ K}\Omega$$

