

# 2002 SCHEME

USN

--	--	--	--	--	--	--	--	--	--

EC74

## Seventh Semester B.E. Degree Examination, June/July 2011 VLSI Circuits

Time: 3 hrs.

Max. Marks:100

**Note: 1. Answer any FIVE full questions.  
2. Missing data may be suitably assumed.**

- 1 a. Explain the importance of full custom and semicustom design styles upon the design cycle time and achievable circuit performance. (06 Marks)
- b. Write the node voltages equations at nodes  $V_1$ ,  $V_2$  and  $V_3$  for fig. Q1(b)(i) and fig. Q1(b)(ii).

 


Fig. Q1(b)(i)

 


Fig. Q1(b)(ii)

Assume the threshold voltage of each of the transistor to be  $V_{th}$ . (06 Marks)

- c. Design 4 : 1 Mux using transmission gates. Also write the advantages and disadvantages of transmission gates. (08 Marks)
- 2 a. Design a CMOS logic gate for the function:  $f = \overline{(a \cdot b + a \cdot c + b \cdot d)}$  using the smallest number of transistors. (04 Marks)
- b. Derive the expression for the linear resistance  $R_n$  of nFET. (06 Marks)
- c. Draw the stick diagram layout for the Boolean function  $z = \overline{(A(D + E) + BC)}$  using Euler path approach. (10 Marks)
- 3 a. Discuss drawn and effective dimensions of MOSFET. (04 Marks)
- b. Write a note on design hierarchies. (08 Marks)
- c. Design the circuit and layout for a CMOS gate that implements the function,  $F = \overline{(a \cdot b \cdot c + a \cdot d)}$  using the fewest number of transistors and a compact layout style. (08 Marks)
- 4 a. Explain the five regions of VTC of an inverter. Also, derive the midpoint voltage equation  $V_m$  for the same. (12 Marks)
- b. Find the total capacitance at the output for the fig. Q4 (b). The give parameter are,  
 $L = 1 \mu\text{m}$  (drawn),  $L_0 = 0.1 \mu\text{m}$ ,  $V_{dd} = 5 \text{ V}$ ,  $C_{ox} = 2.70 \text{ fF}/\mu\text{m}^2$

pFET :  $k_p' = 60 \mu\text{A}/\text{V}^2$     nFET :  $k_n' = 150 \mu\text{A}/\text{V}^2$

$V_{TOP} = -0.7 \text{ V}$

$V_{TON} = 0.6 \text{ V}$

$G = 1.05 \text{ fF}/\mu\text{m}^2$

$G = 0.86 \text{ fF}/\mu\text{m}^2$

$G_{sw} = 0.32 \text{ fF}/\mu\text{m}$

$G_{sw} = 0.24 \text{ fF}/\mu\text{m}$

(08 Marks)

## Q4 (b) Contd....

 


Fig. Q4 (b)

- 5 a. Explain different types of power dissipation taking place in a CMOS inverter. (06 Marks)
- b. A CMOS NAND2 is designed using identical nFETs with a value of  $\beta_n = 2\beta_p$ ; the pFETs are the same size. The power supply is chosen to be  $V_{dd} = 5\text{ V}$  and the device threshold voltages are given as  $V_{tn} = 0.60\text{ V}$  and  $V_{tp} = -0.70\text{ V}$ .
- Find the midpoint voltage  $V_m$  for the case of simultaneous switching.
  - What would be the midpoint voltage for an inverter made with the same  $\beta$  - specification? (06 Marks)
- c. Derive the rise time and fall time equations for NAND2 gate. (08 Marks)
- 6 a. Derive the minimized total delay equation in an inverter cascade to drive large capacitive load. (12 Marks)
- b. Design a digital BiCMOS circuit that implements the function of NAND2 gate. Also discuss the dependence of CMOS and BiCMOS circuits on gate delay and external load capacitance. (05 Marks)
- c. Define : i) Logical effort      ii) Electrical effort      iii) Absolute delay time (03 Marks)
- 7 a. Explain the cascading problem in dynamic CMOS logic circuit. (05 Marks)
- b. Draw the pseudo-nMOS circuit that provide the logic operation,  $f = (a \cdot b + c)$ . (04 Marks)
- c. Explain mirror circuits with example. (08 Marks)
- d. Explain the term charge sharing. (03 Marks)
- 8 Write short notes on:
- General overview of design hierarchy. (07 Marks)
  - Clocking and data flow control. (07 Marks)
  - Clocked CMOS. (06 Marks)

\*\*\*\*\*