

2002 SCHEME

CS33



Third Semester B.E. Degree Examination, June/July 2014 Logic Design

Max. Marks: 100

Note: Answer any FIVE full questions.

- 1 a. Express the following Boolean function as sum of minterms and product of max terms
 $F(x, y, z) = (xy + z)(xz + y)$. (04 Marks)
- b. Reduce the expression using appropriate formula
 $F = A[B + \overline{C}(A \cdot B + \overline{AC})]$. (04 Marks)
- c. Define the following, with an example :
 i) DOS ii) Canonical SOP iii) Disjunctive canonical form. (06 Marks)
- d. Prove NOR and NAND gate are an universal gates. (06 Marks)
- 2 a. Reduce the following expression using K-Map and implement it using basic gates :
 $F(A, B, C, D) = \pi M(0, 1, 2, 6, 8, 10, 11, 12)$. (08 Marks)
- b. Reduce the following function using K - MAP technique and identify prime implicants and essential prime implicants.
 $F(A, B, C, D) = \sum m(0, 12, 3, 6, 7, 13, 15)$. (06 Marks)
- c. Obtain the real minimal expression for $F = \sum m(1, 2, 4, 6, 7)$, using K - MAP and implement it using universal gates. (06 Marks)
- 3 a. Obtain the minimal expression for $F = \sum m(1, 3, 13, 15) + \sum d(8, 9, 10, 11)$ using the Quine Mc Clusky method. (12 Marks)
- b. Simplify the following equation using MEV method :
 $F(W, X, Y, Z) = \sum m(2, 4, 5, 10, 11, 14) + \sum d(7, 8, 9, 12, 13, 15)$. (08 Marks)
- 4 a. Explain the TTL with totem - Pole output stage. (06 Marks)
- b. Explain with the help of circuit diagram the tristate TTL logic. (08 Marks)
- c. Explain with the help of circuit diagram the working of two input CMOS NOR gate. (06 Marks)
- 5 a. Design two bit binary comparator. (07 Marks)
- b. Explain the concept of carry look ahead adder. (07 Marks)
- c. Show how the PLA circuit shown below would be programmed to implement full adder. (06 Marks)

 


Fig. Q5(c)

6. a. Implement $F(w, x, y, z) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$ using 8 : 1 MUX. (07 Marks)
- b. Bring out the differences between combinational and sequential circuits. (05 Marks)
- c. Explain Master-Slave JK-FF with the help of timing diagram. (08 Marks)
7. a. What are shift registers, explain the different forms of shift registers. (10 Marks)
- b. Design a synchronous MOD - 6 counter. (10 Marks)
8. a. Obtain a reduced state table and reduced state diagram for the sequential machine whose state diagram is shown below : (08 Marks)

 


Fig. Q8(a)

- b. Bring out the comparison between synchronous sequential circuit and asynchronous sequential. (06 Marks)
- c. Write a note on the following clocked sequential circuit models : (06 Marks)
 - i) Moore model
 - ii) Mealy model.

CMRIT LIBRARY
BANGALORE - 560 037
