
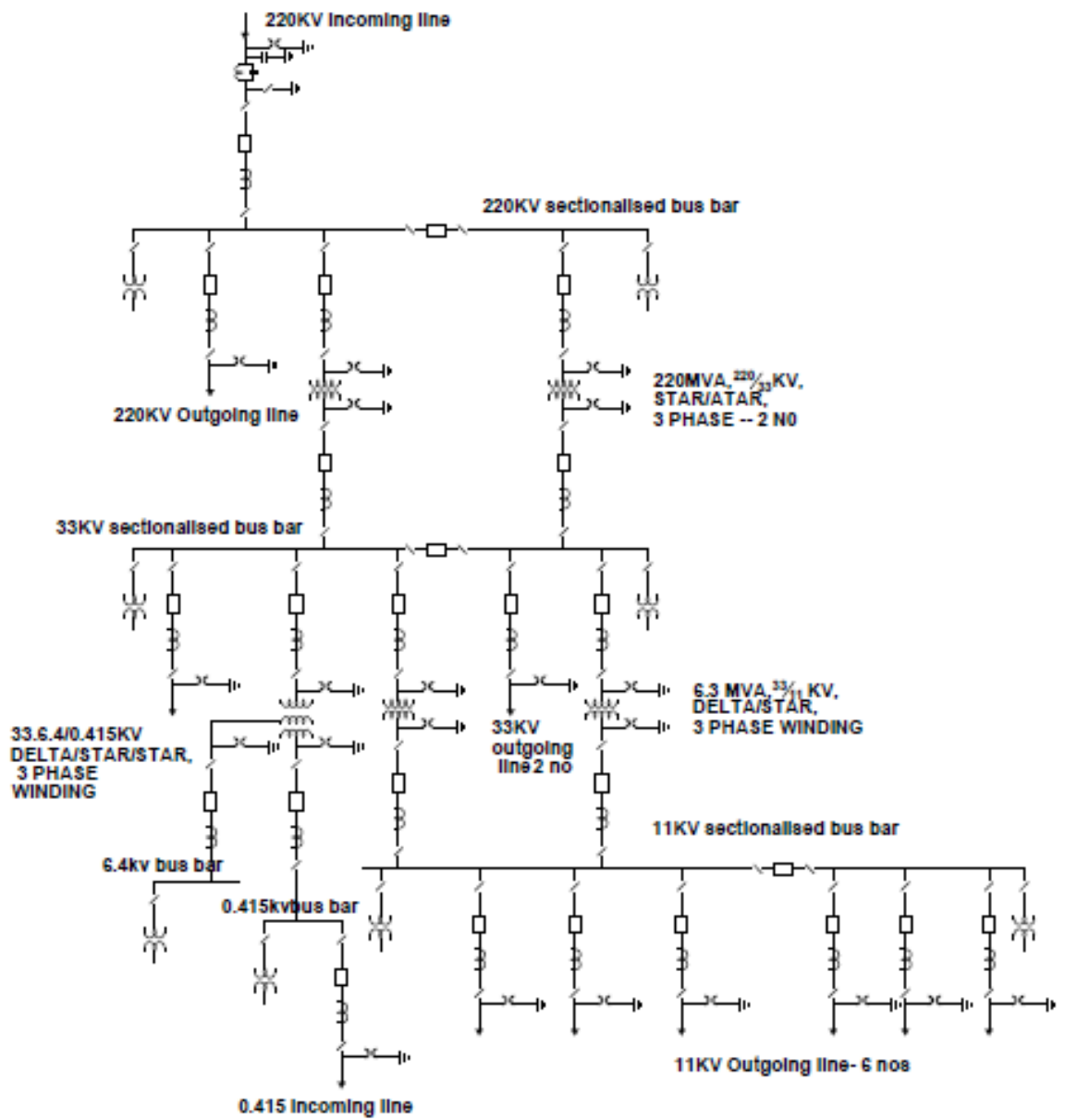


CMR INSTITUTE OF TECHNOLOGY		USN <input type="text"/>								
Internal Assesment Test – I- March 2017								CMR		
Sub:	COMPUTER AIDED ELECTRICAL DRAWING						Code:	10EE65		
Date:	30.03.2017	Duration:	90 mins	Max Marks:	50	Sem:	6	Branch:	EEE	
<b>Note: Q.1 is compulsory. Answer Q.2 OR Q.3.</b> Any missing data may be assumed, but must be stated clearly. Use standard notations only. Neat sketches must be drawn wherever necessary.										
								Marks	OBE	
									CO	R B T
1)	<p>Draw the single line diagram of 220/11 kV distribution substation having the following equipments :</p> <p>a. Incoming line: 220 kV-----1 no.</p> <p>b. Outgoing feeders : 11 kV---- 6 no's 220kV----- 1no 33kV---- 2 no's</p> <p>c. Transformers: 220MVA,220/33kV, Y/Y, 3-ph,50Hz--- 2no.s 6.3 MVA, 33/11 kV, Δ/ Y, 3-ph, 50 Hz-- 2no.s 33/6.4/0.415 kV, delta/star/star, 3 winding-- 1 no.</p> <p>d. Bus bars: 220 kV sectionalized single bus, 33 kV&amp; 11 kV are sectionalized single bus, 6.4 kV, 0.415 kV are single bus</p> <p>e. Coupling condenser, wave trap, and earth switches are to be provided at incoming lines</p> <p>f. Indicate the position of CT, PT, IS, CB and LA.</p>						20	CO605.1 & CO605.3	L2 L2	
2)	Draw the developed winding diagram for a 16 slot, 4 pole, double layer, simplex, progressive lap winding. Show the equalizer ring connection. Draw the sequence diagram.						30	CO605.2	L2	
<b>OR</b>										
3)	Draw the developed DC wave winding diagram for the following data: slots = 20, poles = 4, single layer, simplex winding.						30	CO605.2	L2	



② Draw the developed winding diagram of 16 slots, 4 pole, double layer, simplex, progressive lap winding.


① No: of slots / pole =  $16/4 = 4$  slots.

② No: of conductors / pole =  $32/4 = 8$  conductors

③ 
$$y_b = \frac{Z}{P} \pm k$$

$$= 8 + 1 \quad [ \text{To have full pitch coil} ]$$

$$\therefore y_b = 9$$

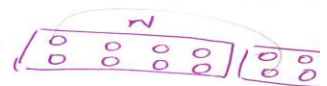

④ 
$$y_b - y_f = \pm 2x$$

$$9 - y_f = 2$$

$$\therefore y_f = 7$$

⑤ winding table :-

1	↗	10
3	↘	12
5	↗	14
7	↘	16
9	↗	18
11	↘	20
13	↗	22
15	↘	24
17	↗	26
19	↘	28
21	↗	30
23	↘	32
25	↗	2
27	↘	4
29	↗	6
31	↘	8



③ Draw the developed winding diagram for the following data  
 Slots = 20, Pole = 4, Single layer, simplex, progressive wdg

① No. of conductors =  $S \times n$   
 =  $20 \times 1$  [  $n = \text{single layer} = 1$  ]

② 
$$Y_c = \frac{Z + 2x}{P} = \frac{20 + 2}{4} = \frac{22}{4} = 5.5$$


③ Since it is a fractional consider 1 coil as dummy coil



④  $\therefore$  No. of conductor =  $20 - 2 = 18$

⑤ 
$$Y_c = \frac{18 + 2}{4} = \frac{20}{4} = 5$$

⑥  $Y_c = 5$  (odd integer) =  $Y_b = Y_f = 5$


⑦ winding table:

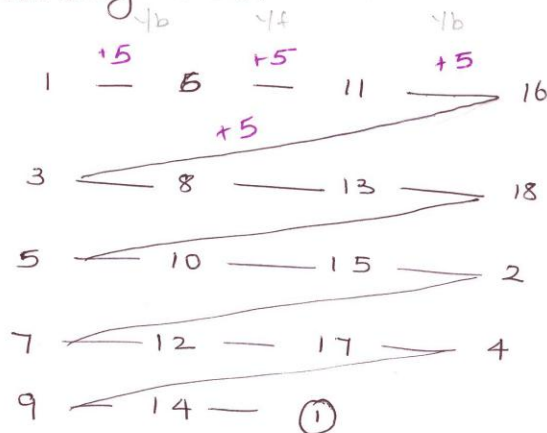

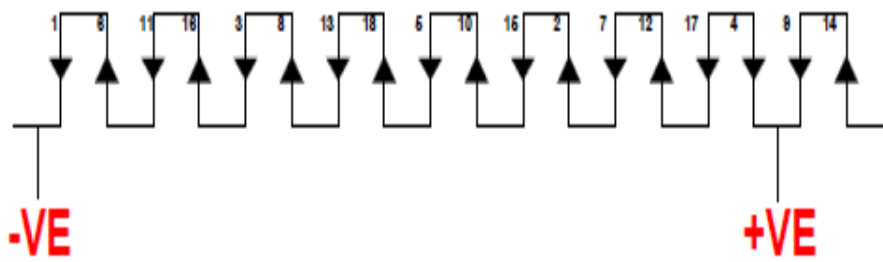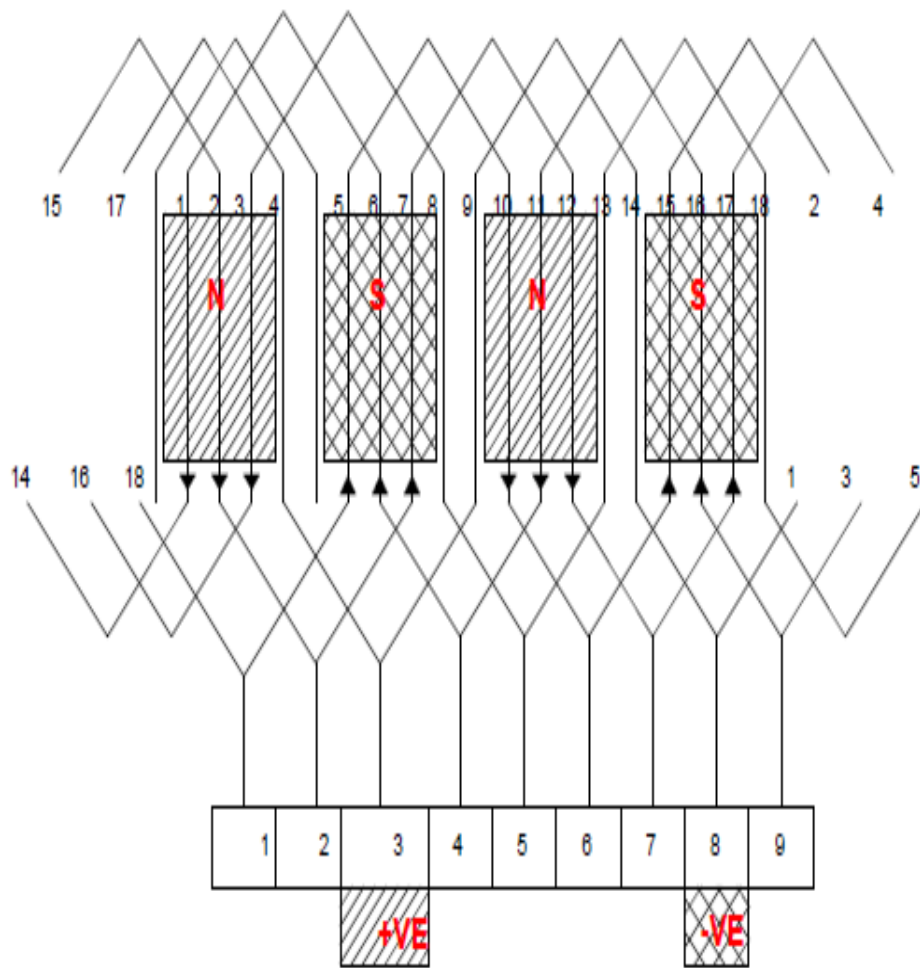



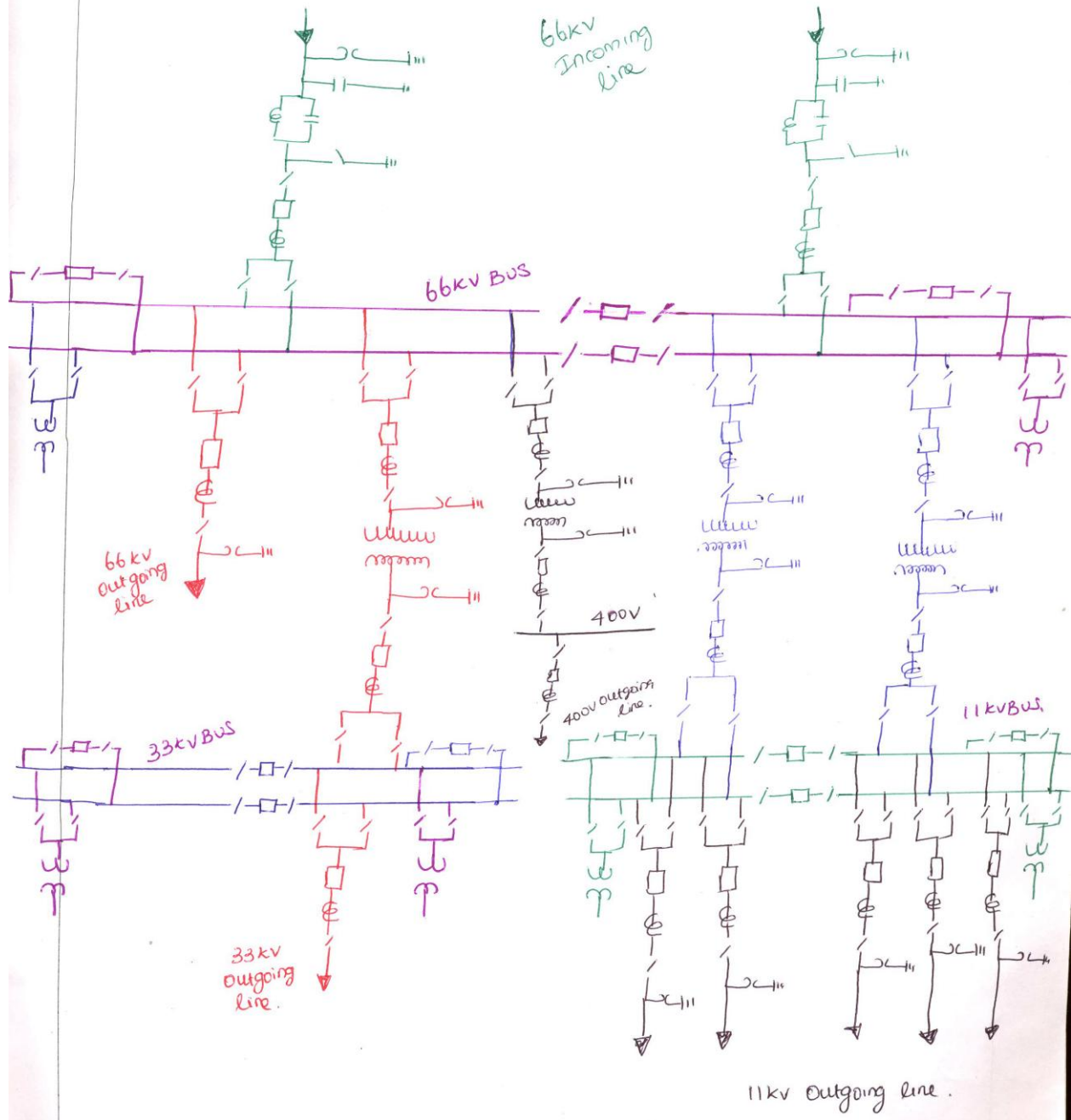① Draw the single line Diagram of 66kv Substation.





② Draw the Developed winding diagram for an 18 slot, 4 Pole, double layer, duplex, progressive lap winding.

① NO: OF SLOTS / pole =  $18/4 = 4.5$

② NO: OF CONDUCTORS =  $S \times n = 18 \times 2 = 36$

③  $\therefore$  NO: OF CONDUCTORS / pole =  $36/4 = 9$

④  $Y_b = z/p \pm k$




$Y_b = 9$


$Y_b - Y_f = +2 \cdot x$

$Y_b - Y_f = 4$

$Y_f = 5$

⑤ Winding table.

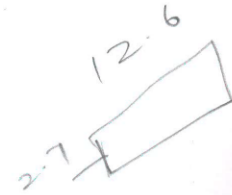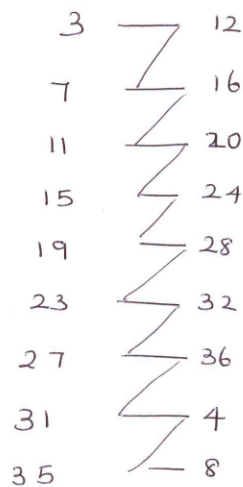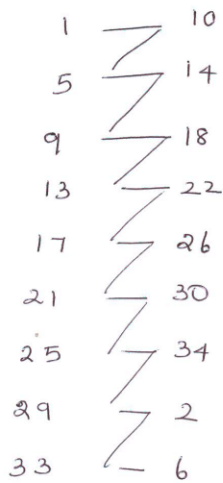

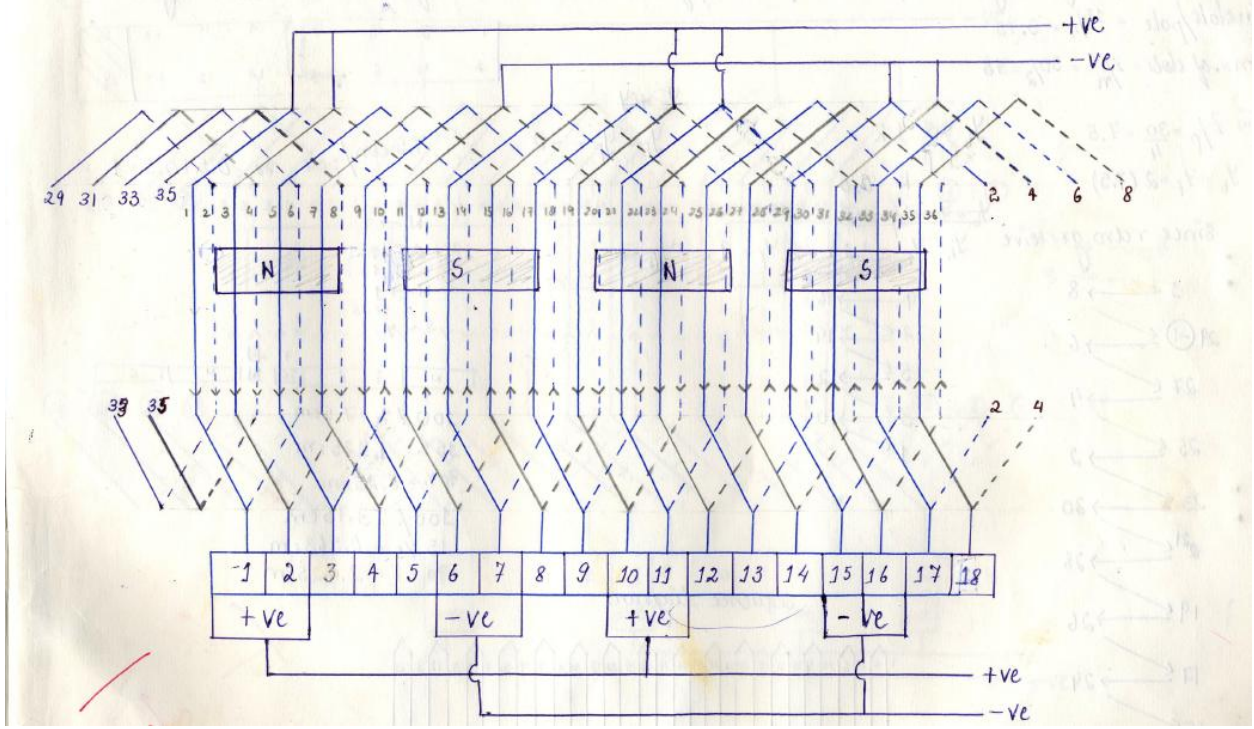

11) No of coils = 20, no of poles = 4, type - double layer simplex, retrogressive wave



$$y_c = \frac{40 - 2}{4} = 9.5$$


$$\text{new } Z = 40 - 2 = 38$$

$$y_c = \frac{38 - 2}{4} = 9$$

$$y_b = y_f = 9$$

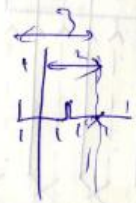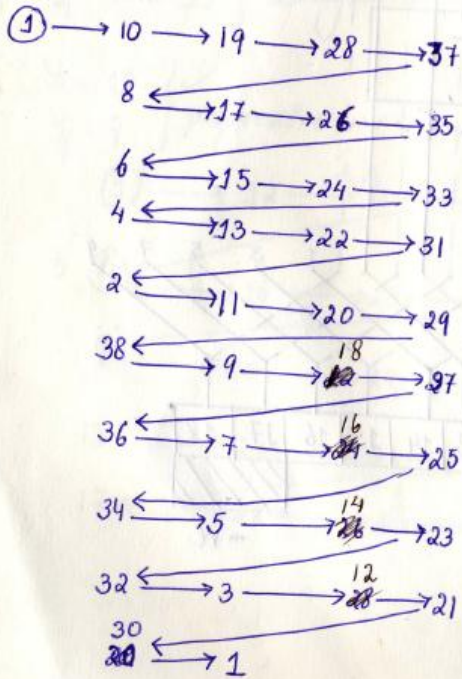
100% → 20  
~~60%~~  
 70% → 14  
 15% → 3  
~~65%~~  
 75% → 20 → 15



CMR INSTITUTE OF TECHNOLOGY		USN <input type="text"/>								
Internal Assesment Test – I- March 2017								CMR		
Sub:	COMPUTER AIDED ELECTRICAL DRAWING						Code:	10EE65		
Date:		Duration:	90 mins	Max Marks:	50	Sem:	6	Branch:	EEE	
<b>Note: Q.1 is compulsory. Answer Q.2 OR Q.3.</b> Any missing data may be assumed, but must be stated clearly. Use standard notations only. Neat sketches must be drawn wherever necessary.										
								Marks	OBE	
									CO	R B T
1)	Draw the Single line Diagram of a Generating station having the following details a) Generators: 50MVA, 11 kV, 3 phase, 50HZ, ----- 5 nos b) Transformers: .50MVA, 11/132 kV, 3 phase, ----- 2no's c) Transformer (auxiliary): 500kVA, 11000/400V, ----- 2 no's d) Transformers (reverse): 1MVA 132/11kV, -----1 no's e) Bus bars : 132 kV double bus bar, 11 kV double bus sectionalized with bus coupler, 400V single bus f) Outgoing lines:132kV-----2no's,11kV --- 5 no, 400v --- 1no, g) Also indicate positions of CT, PT, Isolating Switches, Lightning arrestors and circuit breakers.						20	CO605.1 & CO605.3	L2 L2	
2)	Draw the developed winding diagram for a 14 slot, 4 pole, double layer, simplex, progressive lap Winding. Show the equalizer ring connection. Draw the sequence diagram.						30	CO605.2	L2	
<b>OR</b>										
3)	Draw the developed DC wave winding diagram for the following data: slots =18, poles = 4, double Layer, duplex winding. Draw the sequence diagram and show the brush position.						30	CO605.2	L2	



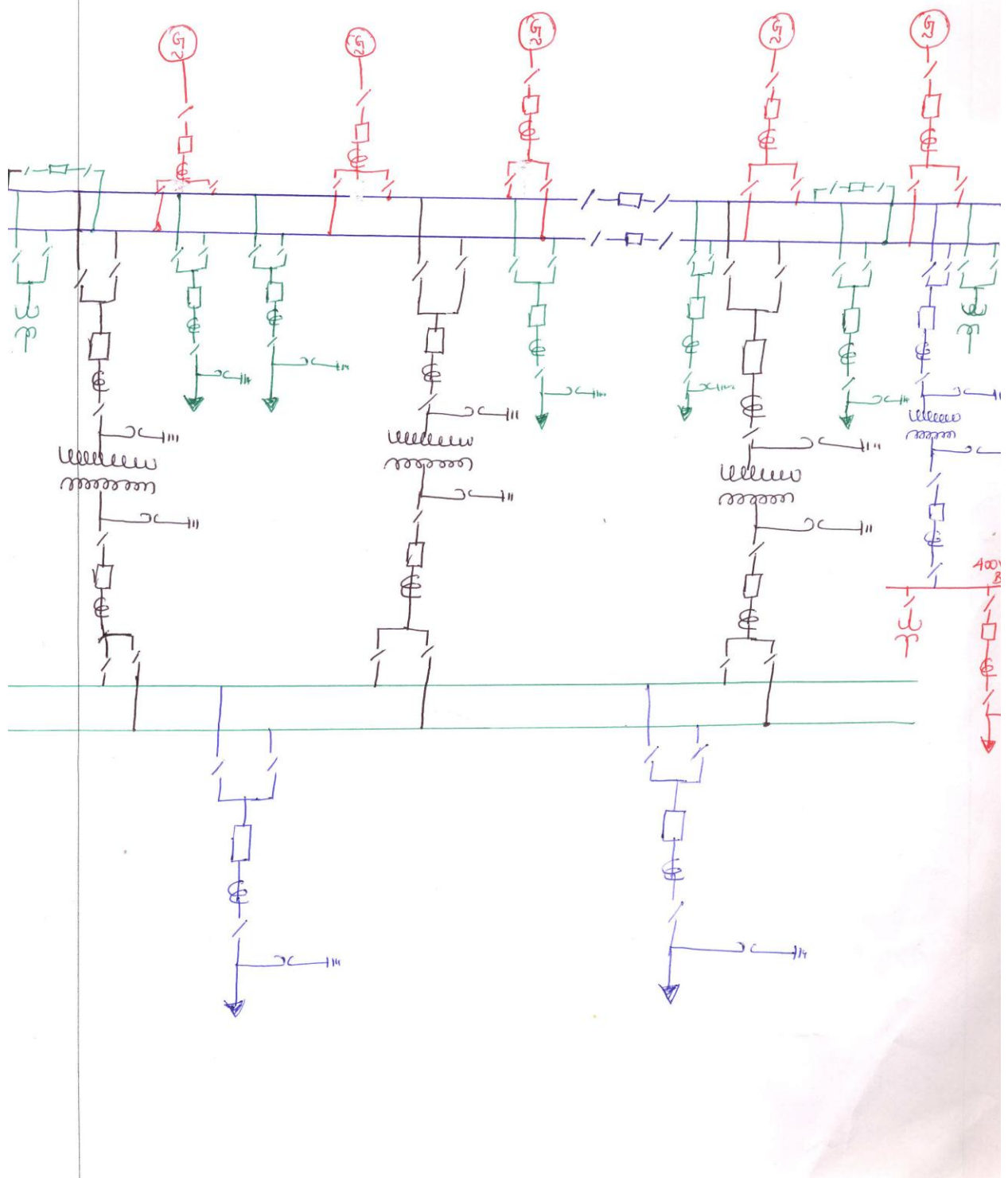Draw single line diagram of a Generating station:



② Draw the developed winding diagram for a 14 slot, 4 pole, double layer, Simplex, Progressive lap winding.

① No. of slots =  $14/4 = 3.5$

② no. of conductors =  $14 \times 2 = 28$

∴ conductors/pole =  $28/4 = 7$

③  $Y_b = Z/p \pm k$

$Y_b = 7$


$Y_b - Y_f = +2 \cdot x \Rightarrow Y_b - Y_f = 2 \Rightarrow 7 - Y_f = 2$

$Y_f = 5$

④  $Y_b = 7$  ;  $Y_f = 5$

⑤ Winding table:

1	—	8
3	—	10
5	—	12
7	—	14
9	—	16
11	—	18
13	—	20
15	—	22
17	—	24
19	—	26
21	—	28
23	—	2
25	—	4
27	—	6
<u>29</u>		

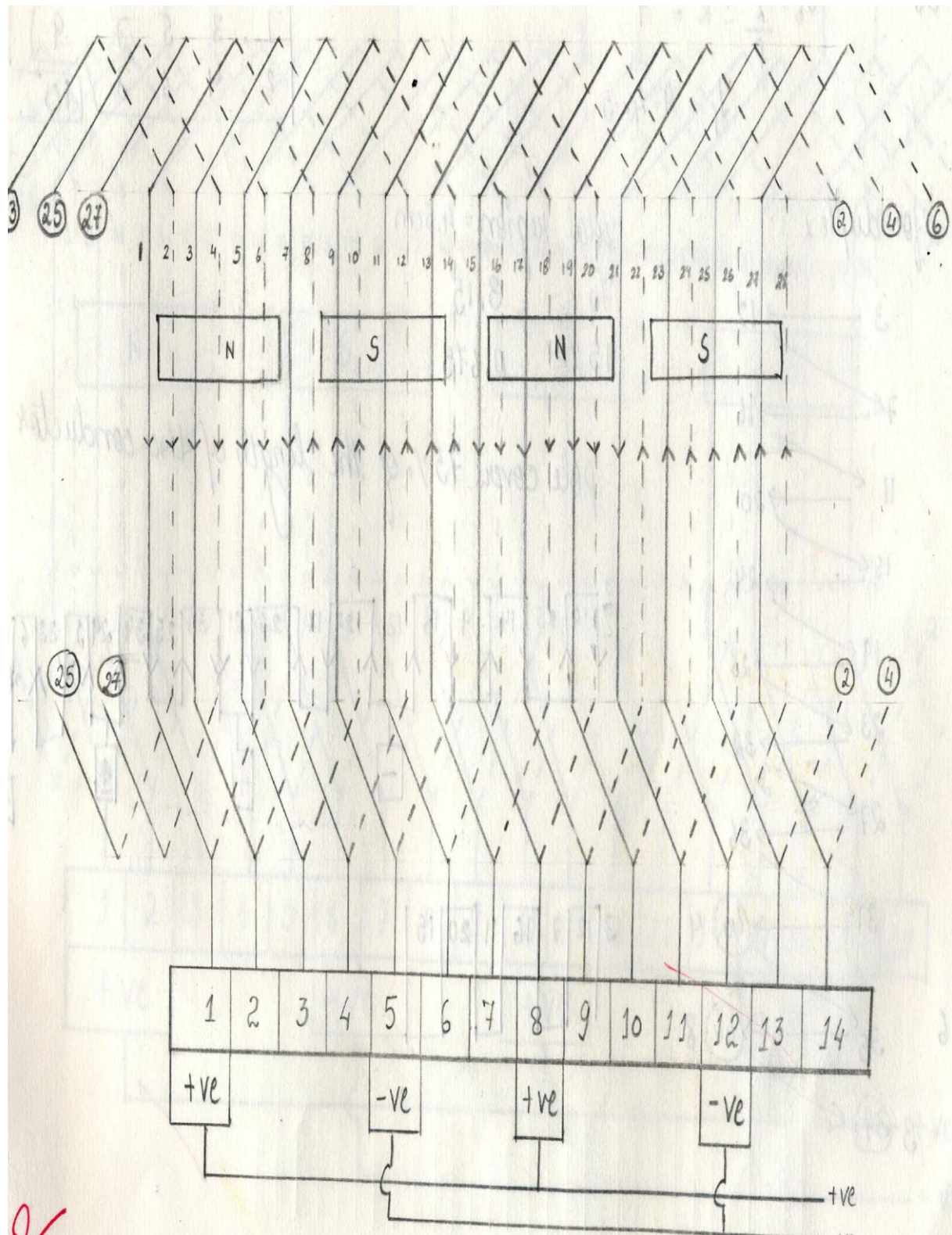

1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26 27 28

N

S

N

S

1	2	3	4	5	6	7	8	9	10	11	12	13	14
---	---	---	---	---	---	---	---	---	----	----	----	----	----

+ve	-ve	+ve	-ve
-----	-----	-----	-----

+ve

③ Draw the Developed winding diagram for the following data.  
 Slots = 18 pole = 4 double layer, duplex, winding.

① No: of slots/p =  $\frac{18}{4} = 4.5$ .

② No: of conductors =  $18 \times 2 = 36$

③ 
$$Y_c = \frac{Z \pm 2 \cdot x}{P} = \frac{36 \pm 4}{4} = \frac{40}{4} = 10$$

④  $Y_c = 10$  [even integer]

$\therefore Y_b = Y_c + 1 = 10 + 1 = 11$

$Y_f = Y_b - 2 = 11 - 2 = 9$

$\therefore Y_b = 11 ; Y_f = 9$

Winding table:

1	—	12	—	21	—	32
5	—	16	—	25	—	36
9	—	20	—	29	—	4
13	—	24	—	33	—	8
17	—	28	—	①		
3	—	14	—	23	—	34
7	—	18	—	27	—	2
11	—	22	—	31	—	6
15	—	26	—	35	—	10
19	—	30	—	③		



