

Internal Assessment Test - III

Sub:	OPERATIONAL AMPLIFIERS AND LINEAR ICs	Code:	15EE46
Date:	31 / 05/ 2017	Duration:	90 mins
		Max Marks:	50
		Sem:	IV
		Branch:	EEE

Note: (i) Answer either Q1 completely or Q2 completely (ii) Q3, Q4 and Q5 is compulsory

		Marks	CO	RBT
1 (a)	List the characteristics of ideal Op-amp. Demonstrate the working of Op-amp as inverting and non-inverting amplifier with circuit diagram and design.	[10]	C406.1	L1
1(b)	Discuss the operation of Op-amp as voltage series and voltage shunt feedback amplifier. Derive the closed loop gain, input resistance and output resistance of the same.	[10]	C406.1	L1
OR				
2(a)	Design a inverting Schmitt trigger to have UTP=+3V and LTP=-5V using an Op-amp uA741 IC with supply voltage $V_{cc} = \pm 15V$.	[10]	C406.4	L3
2(b)	Demonstrate with circuit diagram voltage to current converter with grounded load and current to voltage converter.	[10]	C406.5	L1
3	Explain the working of PLL with block diagram. Explain the function of each block in detail.	[10]	C406.6	L1
4	Explain the working of Astable multivibrator using 555 timer with internal diagram and required waveforms.	[10]	C406.6	L2
5	List the different applications of 555 timer. Explain any 2 applications in detail.	[10]	C406.6	L2


Answer

1(a)

The characteristics of an ideal op-amp are -

- Open loop voltage gain $A_{OL} = \infty$
- Input impedance $R_i = \infty$
- output impedance $R_o = 0$
- Bandwidth $BW = \infty$
- Zero offset i.e. $V_o = 0$ if $V_1 = V_2 = 0$

Non inverting amplifier

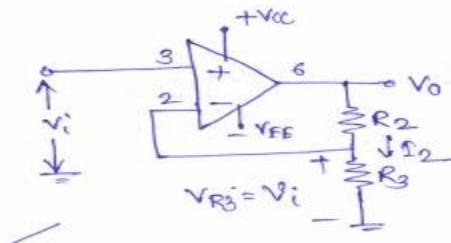

Applying KCL at port no. 2 we get, $I_{R2} = I_{R3}$

$$\frac{V_{R3}}{R_3} = \frac{V_0 - V_i}{R_2}$$


$$\text{or, } \frac{V_i}{R_3} = \frac{V_0 - V_i}{R_2}$$

$$\text{or, } V_i \left(\frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{V_0}{R_2}$$

$$\text{or, } \frac{V_0}{V_i} = R_2 \cdot \frac{R_2 + R_3}{R_2 R_3} = \left(1 + \frac{R_2}{R_3} \right)$$

$$\therefore \boxed{A_V = \frac{V_0}{V_i} = \left(1 + \frac{R_2}{R_3} \right)}$$

Inverting amplifier

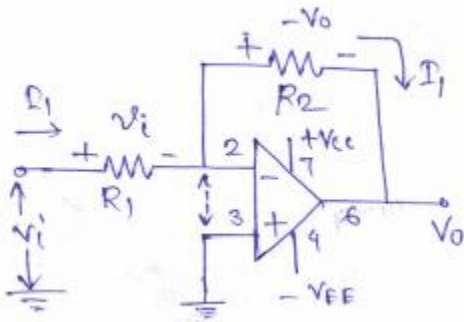

now, applying KCL at node 2 we get,


$$\frac{V_i}{R_1} = \frac{0 - V_0}{R_2}$$

$$\text{or, } A_V = \frac{V_0}{V_i} = -\frac{R_2}{R_1}$$

$$\therefore \boxed{A_V = -\frac{R_2}{R_1}}$$

1(b)

(1) Voltage - series feedback amplifier

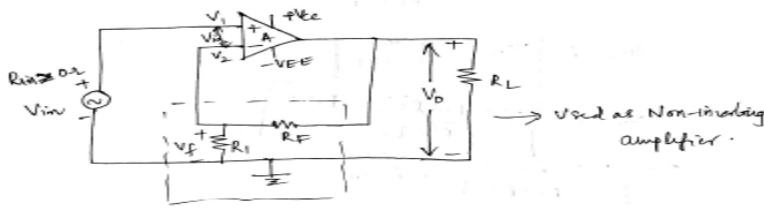

open loop voltage gain $(A = \frac{V_o}{V_{id}})$
 closed loop voltage gain $A_F = \frac{V_o}{V_{in}}$
 gain of feedback circuit $B = \frac{V_f}{V_o}$

Negative feedback

$V_{id} = V_{in} - V_f$
 $V_{in} \rightarrow$ input voltage V_f - feedback voltage $V_{id} =$ diff. i/p V.
 feedback always lags input voltage (180°).

closed loop voltage gain

$$A_F = \frac{V_o}{V_{in}} \quad V_o = A(V_{in} - V_f)$$

from fig $V_i = V_{in}$

$$V_o = V_f = \frac{V_o \times R_1}{R_1 + R_F}$$

$$V_o = A \left[V_{in} - \frac{R_1 V_o}{R_1 + R_F} \right]$$

$$V_o = \frac{A \left[V_{in}(R_1 + R_F) - R_1 V_o \right]}{R_1 + R_F}$$

$$V_o \left[1 + \frac{R_1}{R_1 + R_F} \right] = A V_{in}$$

$$V_o = \frac{A (R_1 + R_F) V_{in}}{R_1 + R_F + A R_1}$$

$$A_F = \frac{V_o}{V_{in}} = \frac{A (R_1 + R_F)}{R_1 + R_F + A R_1}$$

A is very large (10^5)

$A R_1 \gg (R_1 + R_F)$ so $R_1 + R_F + A R_1 \approx A R_1$

$$A_F = \frac{V_o}{V_{in}} = \frac{A (R_1 + R_F)}{A R_1} = \frac{1 + R_F}{R_1} \text{ (Ideal)}$$

$$B = \frac{V_f}{V_o} = \frac{R_1}{R_1 + R_F}$$


8

Comparing A & B



$$A_F = \frac{1}{B}$$

$$A_F = \frac{A(R_1 + R_F)}{R_1 + R_F + AR_1} = \frac{A \left(\frac{R_1 + R_F}{R_1 + R_F} \right)}{\frac{R_1 + R_F}{R_1 + R_F} + \frac{AR_1}{R_1 + R_F}}$$

$$A_F = \frac{A}{1 + A \cdot B}$$

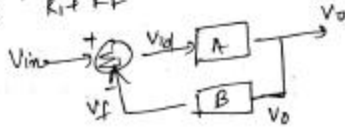

Voltage shunt feedback amplifier

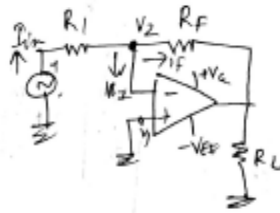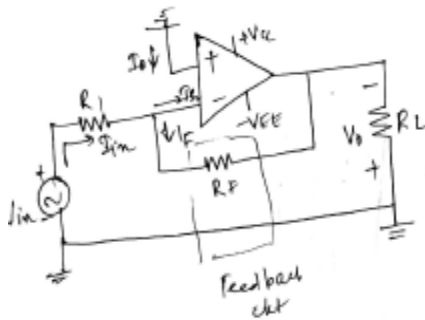

closed loop voltage gain

$$i_{in} = i_f + i_{i_b}$$

$$i_{i_b} \ll i_{in} \approx i_f$$

$$\frac{V_{in} - V_2}{R_1} = \frac{V_2 - V_o}{R_F}$$

$$V_1 - V_2 = V_o/A$$

$$V_1 = 0 \quad V_2 = -\frac{V_o}{A}$$

$$\frac{V_{in} + V_o/A}{R_1} = \frac{-\frac{V_o}{A} - V_o}{R_F}$$

$$A_F = \frac{V_o}{V_{in}} = \frac{-AR_F}{R_1 + R_F + AR_1}$$

$$AR_1 \gg R_1 + R_F$$

$$A_F = \frac{V_o}{V_{in}} = \frac{-R_F}{R_1}$$

2(a)

$UTP = +3V$ $LTP = -5V$ $V_{CC} = \pm 15V$


$R_3 = \frac{UTP}{I_1} = \frac{3}{500\mu A} = 6 \times 10^3 \Omega = 6k\Omega (5.6k\Omega)$

$UTP = \frac{V_{out} \times R_3}{R_1 + R_3}$ $LTP = \frac{V_{out} \times R_3}{R_2 + R_3}$

$3 = \frac{14 \times 5.6k\Omega}{R_1 + 5.6k\Omega}$ $3(R_1 + 5.6k\Omega) = 14 \times 5.6k\Omega$
 $3R_1 + 16.8k\Omega = 78.4k\Omega$
 $3R_1 = 61.6k\Omega$
 $R_1 = 20.5k\Omega (18k\Omega)$


$5 = \frac{14 \times 5.6k\Omega}{R_2 + 5.6k\Omega}$ $5R_2 + 28k\Omega = 78.4k\Omega$
 $5R_2 = 50.4k\Omega$
 $R_2 = 10k\Omega$

2(b) voltage to current converters

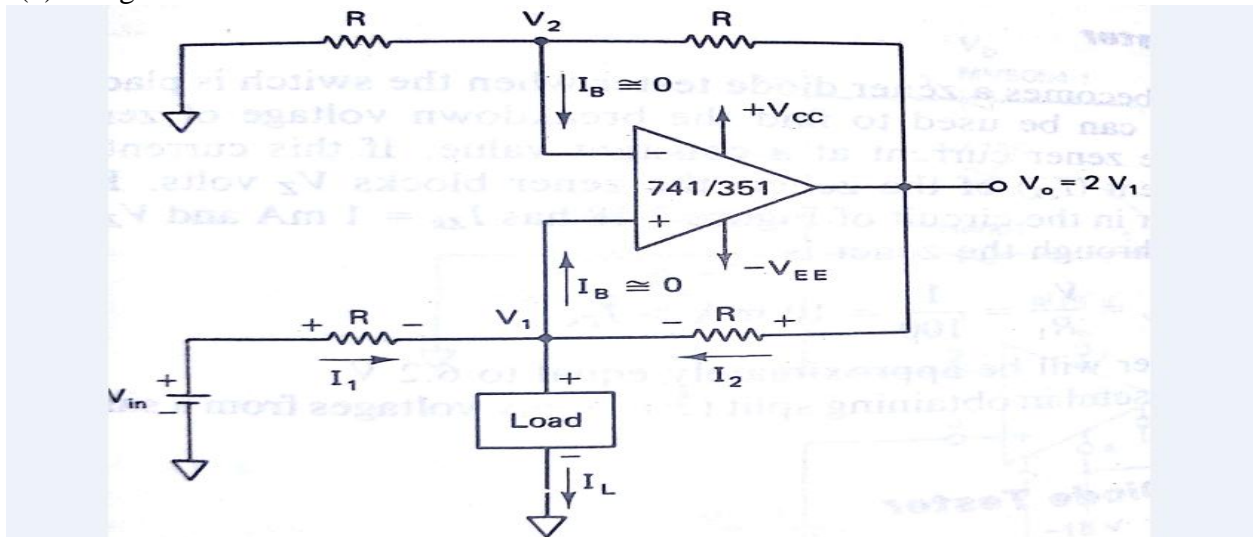


Current to voltage converters
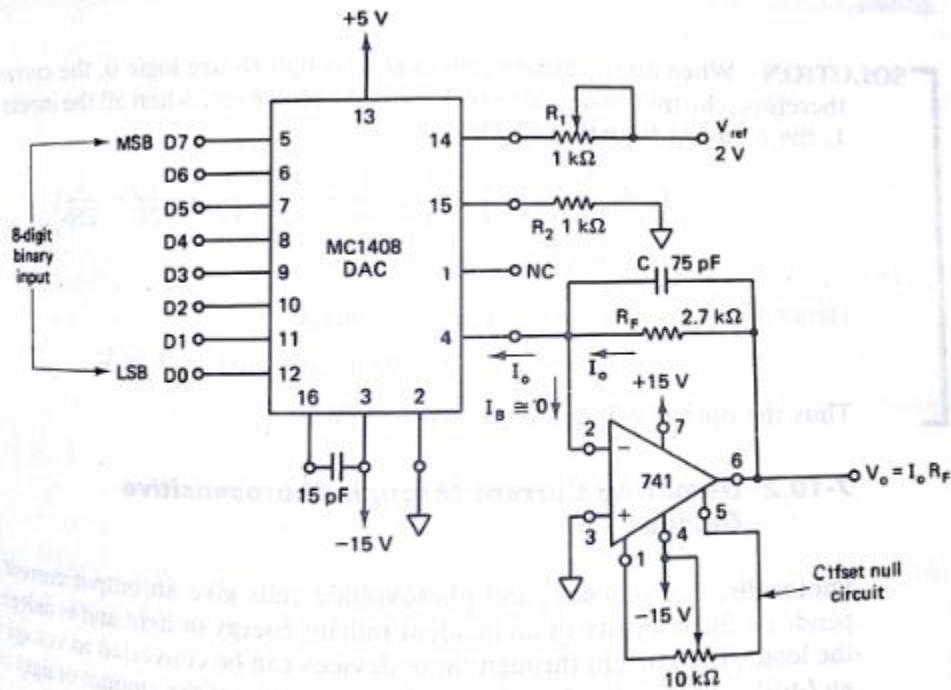
$$I_o = \frac{V_{ref}}{R_1} \left(\frac{D_7}{2} + \frac{D_6}{4} + \frac{D_5}{8} + \frac{D_4}{16} + \frac{D_3}{32} + \frac{D_2}{64} + \frac{D_1}{128} + \frac{D_0}{256} \right) \quad (7-22a)$$




$$I_o = \frac{V_{ref}}{R_1} \left(\frac{D_7}{2} + \frac{D_6}{4} + \frac{D_5}{8} + \frac{D_4}{16} + \frac{D_3}{32} + \frac{D_2}{64} + \frac{D_1}{128} + \frac{D_0}{256} \right)$$


Figure 7-20 DAC using current-to-voltage converter.

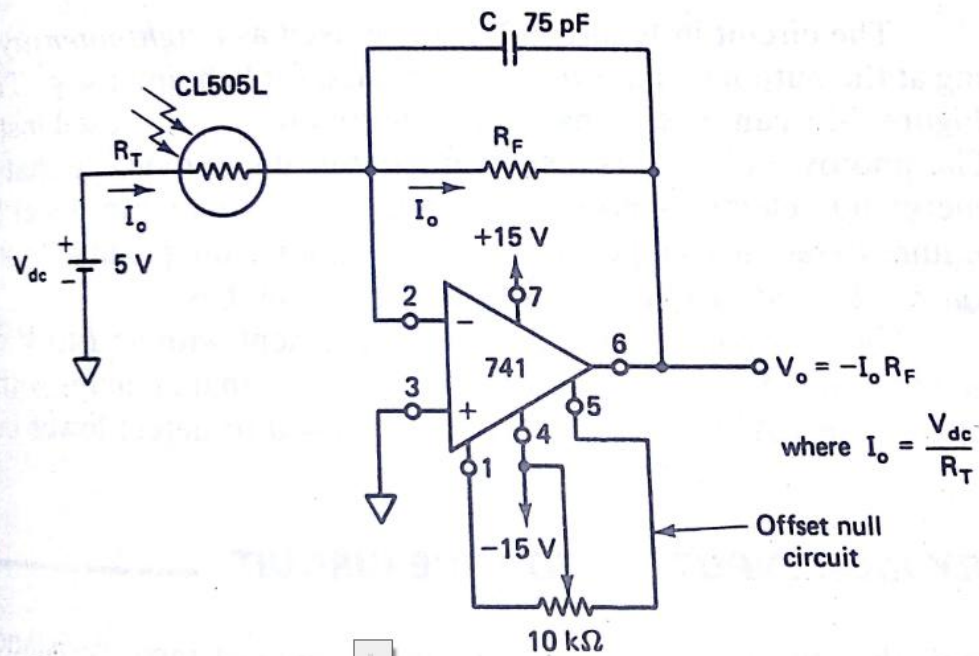

3

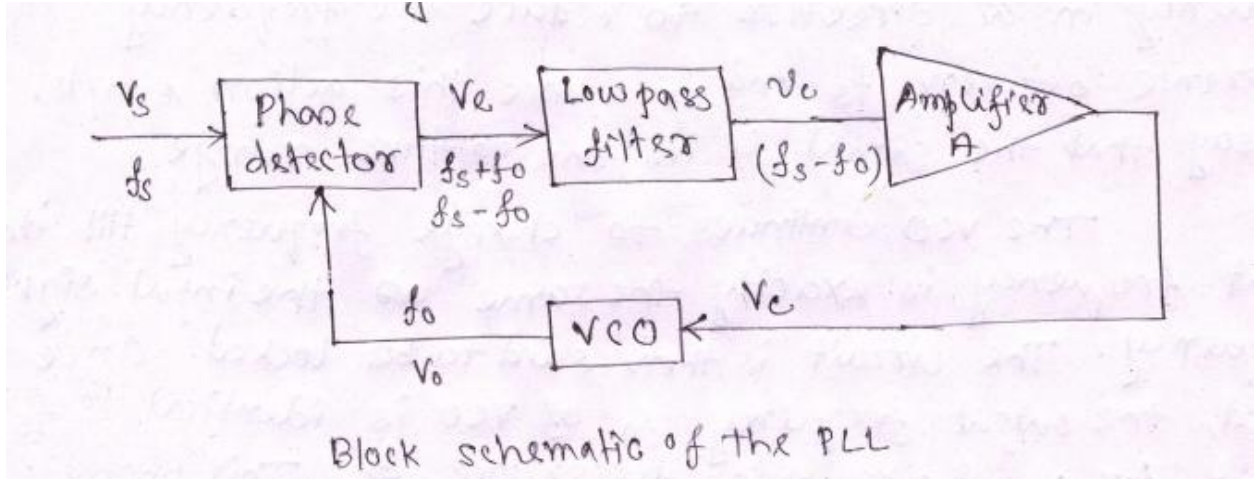

4

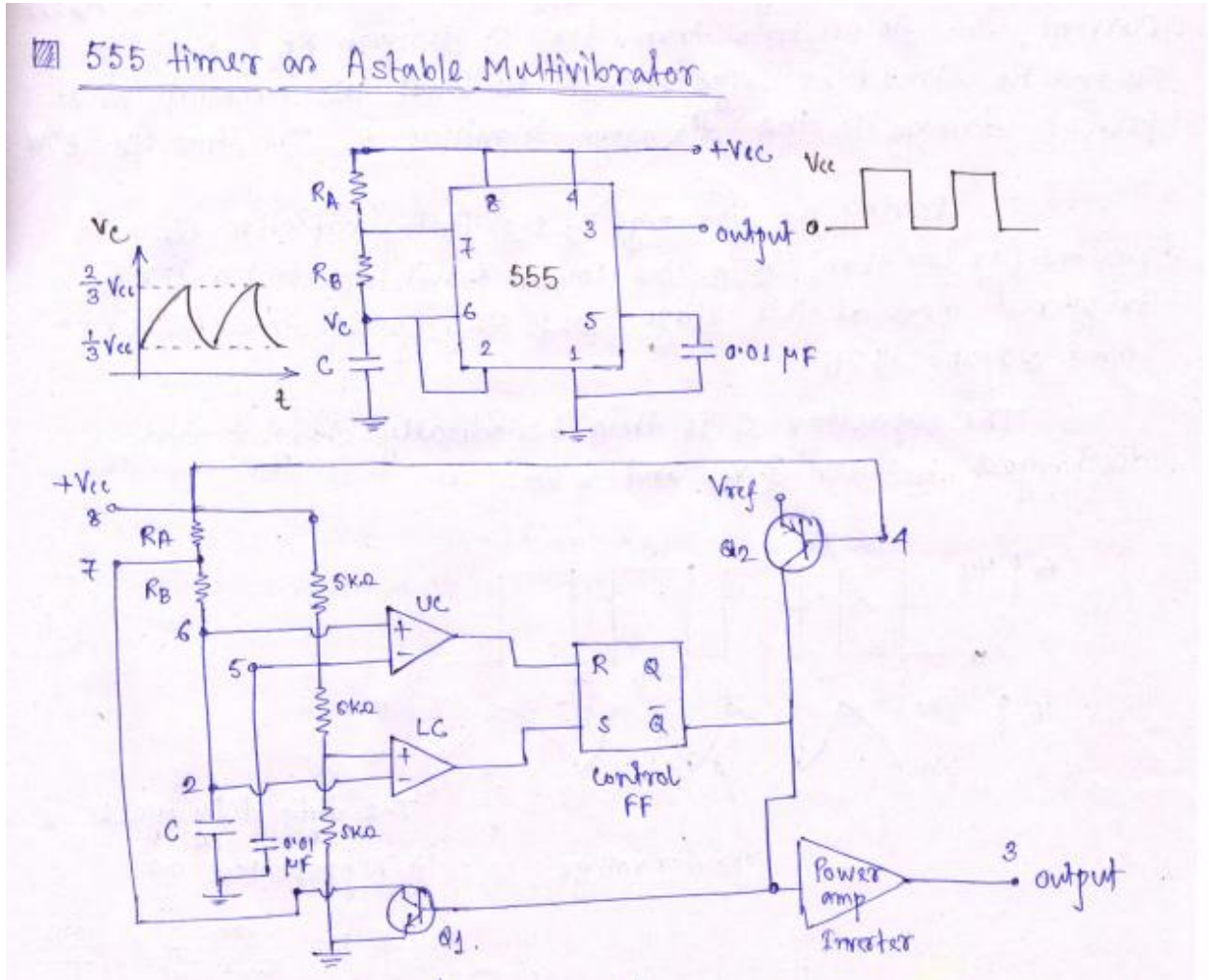

5

