

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EVE14

## First Semester M.Tech. Degree Examination, Dec.2019/Jan.2020 VLSI Testing

Time: 3 hrs.

Max. Marks: 100

**Note: Answer FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. Explain breaks and transistor stuck – ON fault in CMOS with example. (10 Marks)
- b. Explain various types of bridging fault with example. (10 Marks)

OR

- 2 a. What is temporary fault? Write state diagram of Markov model with explanation. (05 Marks)
- b. Explain simulation process with block diagram. (05 Marks)
- c. Explain the various types of simulators. (10 Marks)

### Module-2

- 3 a. For Fig Q3(a), using Boolean difference technique :
  - i) Detect s-a-0 and s-a-1 on g
  - ii) Determine partial Boolean difference for y-l-n-f

 


Fig Q3(a)

- b. Using Reed – Muller Expansion technique, find test sets for function,  $F = WX + WY + XY$  and implement the design. (08 Marks)
- c. Explain Three – Level OR – AND – OR design with example. (06 Marks)

OR

- 4 a. Find test pattern for line 6 s-a-0, using D – algorithm for Fig Q4(a).

 


Fig Q4(a)

- b. Define PODEM. Explain the working of PODEM. (05 Marks)
- c. What is the significance of FAN with respect to PODEM? Explain FAN concept with example. (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

11 3 FEB 2020

**Module-3**

- 5 a. List and explain various possible faults in PLA. Write PLA design for  $f_1 = x_1x_2 + x_1'x_2'$  and  $f_2 = \bar{x}_1x_2$ . (10 Marks)
- b. What is redundancy? Explain the concept and classification of redundancy with example. (10 Marks)

**OR**

- 6 a. For a given state table shown in Table Q6(a), find
- Response for 010 condition
  - Homing sequence
  - Distinguishing sequence

Present state	Input/NS	
	X = 0	X = 1
A	B, 0	D, 0
B	A, 0	B, 0
C	D, 1	A, 0
D	D, 1	C, 0

Table Q6(a)

(10 Marks)

- b. Explain the various phases involved in checking experiment based on sequential circuit structure. (05 Marks)
- c. What is synchronizing sequence? Find synchronizing sequence for Table Q6(c)

Present state	Input/NS	
	X = 0	X = 1
A	B, 1	C, 0
B	A, 0	D, 1
C	B, 0	A, 0
D	C, 1	A, 1

Table Q6(c)

(05 Marks)

**Module-4**

- 7 a. Define controllability and observability with respect to sequential circuit testing. Explain with example circuit. (08 Marks)
- b. With diagram, explain the working of crosscheck and cross check grid. (06 Marks)
- c. Explain Boundary scan architecture. (06 Marks)

**OR**

- 8 a. Explain clocked Hazard free latches in LSSD. (10 Marks)
- b. Illustrate the significance of partial scan. Design partial scan for a combinational logic. (10 Marks)

**Module-5**

- 9 a. Explain Pseudo – Random pattern Generator for BIST with example. (10 Marks)
- b. List and explain various types of output response analysis. (10 Marks)

**OR**

- 10 a. Explain various test algorithms for RAM. (10 Marks)
- b. Explain BIST structure for SRAM. (10 Marks)

\* \* \* \* \*