

USN

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

**CMRIT LIBRARY**  
BANGALORE - 560 037

14EVE421

**Fourth Semester M.Tech. Degree Examination, June/July 2018**

**Advances in VLSI Design**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions.**

- 1 a. Compare CMOS and Bi-CMOS technology. (05 Marks)  
b. Derive an expression for the pinch off voltage in a MESFET with an active layer thickness of  $t$ . (10 Marks)  
c. Analyze the working of MOSFETs as switches. (05 Marks)
- 2 a. Calculate the threshold voltage for a realistic n-channel MIS device given the following:  
 $N_a = 10^{17} \text{ cm}^{-3}$ ,  $Q_i = 10^{11} \text{ g/cm}^2$ ,  $d = 20 \text{ nm}$  and  $\phi_{ms} = -0.95 \text{ V}$  (10 Marks)  
b. Analyze the working of a MODFET with neat diagrams. (10 Marks)
- 3 a. With the help of a neat diagram analyze the working of an ideal and non-ideal MIS structure. (10 Marks)  
b. Bring out the effect of decrease in the physical separation between the source and the drain, with relevant equations, in a MOSFET. (10 Marks)
- 4 a. Determine the thickness of the Si active layer in a partially depleted SOI device if the layer is only 50% depleted in equilibrium. Assume that the Schottky barrier height is 0.72 eV, the effective density of states within the conduction band is  $N_c = 3.22 \times 10^{19} \text{ /cm}^3$ , and the doping concentration is  $10^{16} \text{ /cm}^3$ . Assume that all of the donors are ionized. (10 Marks)  
b. Analyze the working of carbon nano tubes with relevant diagrams. Also bring out the advantages and disadvantages of the same. (10 Marks)
- 5 a. Derive the equation for propagation time of a long polysilicon line. (10 Marks)  
b. Design a NAND and NOR gate (Two input) using nMOS pass transistor. (10 Marks)
- 6 a. Analyze the concept of charge sharing. Give a methodology to overcome this problem. (10 Marks)  
b. With relevant diagrams analyze the latch up problem in bulk CMOS technology. (10 Marks)
- 7 a. Analyze a clocking circuit working principle. Also bring out the mechanism of clock generation, clock distribution and clocked storage elements with relevant diagrams. (10 Marks)  
b. Design a 3-input tally circuit with pass transistors. (10 Marks)
- 8 a. Using NOR-NOR logic implement  $Y = (A + B + C)(D + E + F)$ . (10 Marks)  
b. Analyze the working of RAM based FPGA with neat diagrams. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

\*\*\*\*\*  
**CMRIT LIBRARY**  
BANGALORE - 560 037