

# CMRIT Library

## CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

16/17EVE12

### First Semester M.Tech. Degree Examination, Dec.2017/Jan.2018

### Digital VLSI Design

CMRIT LIBRARY  
BANGALORE - 560 037

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing one full question from each module.

#### Module-1

- Derive the MOSFET current equation in different regions of operation and plot the current voltage characteristics of an n-channel MOSFET. (08 Marks)
  - What is MOSFET scaling? Explain in brief the types of scaling indicating the effect of scaling on derive characteristics. (08 Marks)

OR

- Explain the working of resistance load inverter with necessary circuit diagram and voltage transfer characteristic. Also device the equations for  $V_{OL}$ ,  $V_{OH}$ ,  $V_{IL}$  and  $V_{IH}$ . (08 Marks)
  - Calculate the critical voltage  $V_{OL}$ ,  $V_{OH}$ ,  $V_{IL}$  and  $V_{IH}$  and find the noise margins of the depletion load inverter circuit with the following parameter :

$$V_{DD} = 5V, V_{TO(\text{driver})} = 1.0V, V_{TO(\text{load})} = -3.0V, \left(\frac{W}{L}\right)_{\text{Driver}} = 2, \left(\frac{W}{L}\right)_{\text{Load}} = \frac{1}{3},$$

$$K_{n(\text{driver})} = k_{n(\text{load})} = 25\mu A/V^2, \gamma = 0.4V^{1/2}, \phi_F = -0.3V. \quad (08 \text{ Marks})$$

#### Module-2

- Draw the circuit of a CMOS inverter and derive the switching threshold ( $V_{th}$ ) equation for the same. (06 Marks)
  - Define propagation delay time and obtain the equations for  $\tau_{PHL}$  and  $\tau_{PLH}$  for CMOS inverter. (10 Marks)

OR

- Derive an equation for switching power dissipation of CMOS inverter with necessary circuit diagram and waveforms. (06 Marks)
  - How to measure the propagation delay of an inverter using ring oscillator? Explain with necessary diagrams and equations. (06 Marks)
  - With suitable circuit diagrams and equations, explain RC delay model to calculate the interconnect delay. (04 Marks)

#### Module-3

- With necessary circuit diagrams, explain the following dynamic RAM cells. 4T DRAM, 3T DRAM, 2T DRAM and 1T DRAM. (10 Marks)
  - Explain 4bit  $\times$  4bit NAND based ROM array with necessary diagrams. (06 Marks)

CMRIT LIBRARY  
BANGALORE - 560 037

CMRIT LIBRARY  
BANGALORE - 560 037

OR

- 6 a. Briefly explain memory structure of SRAM with read and write circuitry with the help of read and write timing diagrams. (10 Marks)
- b. Draw the schematic of flash memory cell and explain. (06 Marks)

**Module-4**

- 7 a. With necessary circuit diagram explain enhancement load based rationed, 3bit dynamic shift register. (08 Marks)
- b. Discuss the working principle of NORA CMOS logic and zipper CMOS logic with necessary diagrams. (08 Marks)

OR

- 8 a. What is BiCOMS logic? With neat circuit diagram explain the working of BiCMOS inverter? Also mention the advantages and disadvantages of BiCMOS. (10 Marks)
- b. Draw the BiCMOS circuit for the function  $Y = \overline{A(B+C)}$ . (04 Marks)
- c. Calculate the value of  $V_{out}$  in the circuit shown in Fig. Q8(c), if threshold voltage of pass transistor is 0.7V. (02 Marks)

 


Fig. Q8 (c)

**Module-5**

- 9 a. With relevant circuit diagram and symbolic representation, explain two types of input circuits. (08 Marks)
- b. Explain on-chip clock generation and clock distribution with necessary diagrams. (08 Marks)

OR

- 10 a. What is latch up in CMOS? Explain with necessary diagrams and equations? Also discuss guidelines for avoiding latch up. (10 Marks)
- b. Describe performance modeling procedure with a model. (06 Marks)