

USN

--	--	--	--	--	--	--	--	--	--

CMRIT LIBRARY
BANGALORE - 560 087

16/17EVE14

First Semester M.Tech. Degree Examination, Dec.2017/Jan.2018

Low Power VLSI Design

Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Explain the needs of low power VLSI design. (05 Marks)
- b. Derive the expression for power dissipation in CMOS circuit due to charging and discharging of capacitance. (07 Marks)
- c. Explain the basic principles of low power design. (04 Marks)

OR

- 2 a. Discuss the terms capacitive power dissipation, internal switching energy and static state power with respect to gate level logic simulation. (08 Marks)
- b. Discuss Monte Carlo power simulation. (08 Marks)

Module-2

- 3 a. Define static probability. Derive the equation that relates the static probability P of memoryless random logic signal to its expected frequency 'f'. (08 Marks)
- b. What is entropy? Discuss the power estimation of combinational logic using entropy. (08 Marks)

OR

- 4 a. Derive the relationship between the power dissipation and the stage ratio for an inverter chain. (08 Marks)
- b. Write a note on low power digital cell library. (08 Marks)

Module-3

- 5 a. Explain local restructuring rules of transformation with relevant illustrations. (08 Marks)
- b. With the help of an example, explain the precomputation logic optimization method to trade area for power in a synchronous digital circuit. (08 Marks)

OR

- 6 a. Explain the clock driving schemes for clock distribution. Also discuss the techniques used for delay reduction. (08 Marks)
- b. What is tolerable skew? With neat waveforms, explain the terms double clocking and zero clocking. Write the expressions to avoid them. (08 Marks)

Module-4

- 7 a. Briefly explain the principle of guarded evaluation and bus multiplexing for switching activity reduction. (08 Marks)
- b. Draw the control data flow graph for the equation $Y_n = a_n b_n + 3a_{n-1}$. Also write the corresponding hardware architecture to reduce area. (08 Marks)

OR

- 8 a. Discuss 16-bit carry skip adder with constant block width and variable block width. (08 Marks)
b. Explain 8-bit Wallace Tree multiplier. (08 Marks)

Module-5

- 9 a. Explain the sources of power dissipation in DRAM and SRAM. (08 Marks)
b. For low power CAD framework, explain the design flow with supporting tools. (08 Marks)

OR

- 10 a. Explain capacitance models for hardware modules and activity models for data and control signals, with respect to architectural estimation. (08 Marks)
b. Write a note on adiabatic computation. (08 Marks)