

USN

|  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|

**Internal Assessment Test 1 –Mar 2018**

**Sub:** Digital System Design using Verilog

**Date:** 14/03/2018    **Duration:** 90mins    **Max Marks:** 50    **Sem:** Ist

**Code:** 10ECE663


**Branch:** BE ECE  
NON CBCS

**Note: - Answer all questions**


|   |  |     |
|---|--|-----|
| 1 | Explain the systematic process of digital system from design to Embedded system design.  | 10M |
| 2 | Develop verilog code for priority encoder of 8:3   | 10M |
| 3 | Construct a multiplier for two 16-bit operands containing just one adder that adds successive partial products over successive clock cycles. | 10M |
| 4 | Construct a datapath to perform a complex multiplication. All inputs are 4 pre binary and 12 post binary points.                             | 10M |
| 5 | Explain flip-flops, counters and shift registers. Explain with syntax and proper example   | 10M |

1) Explain the systematic process of digital system from design to embedded system design.  
Design methodology :-


A simple Design methodology

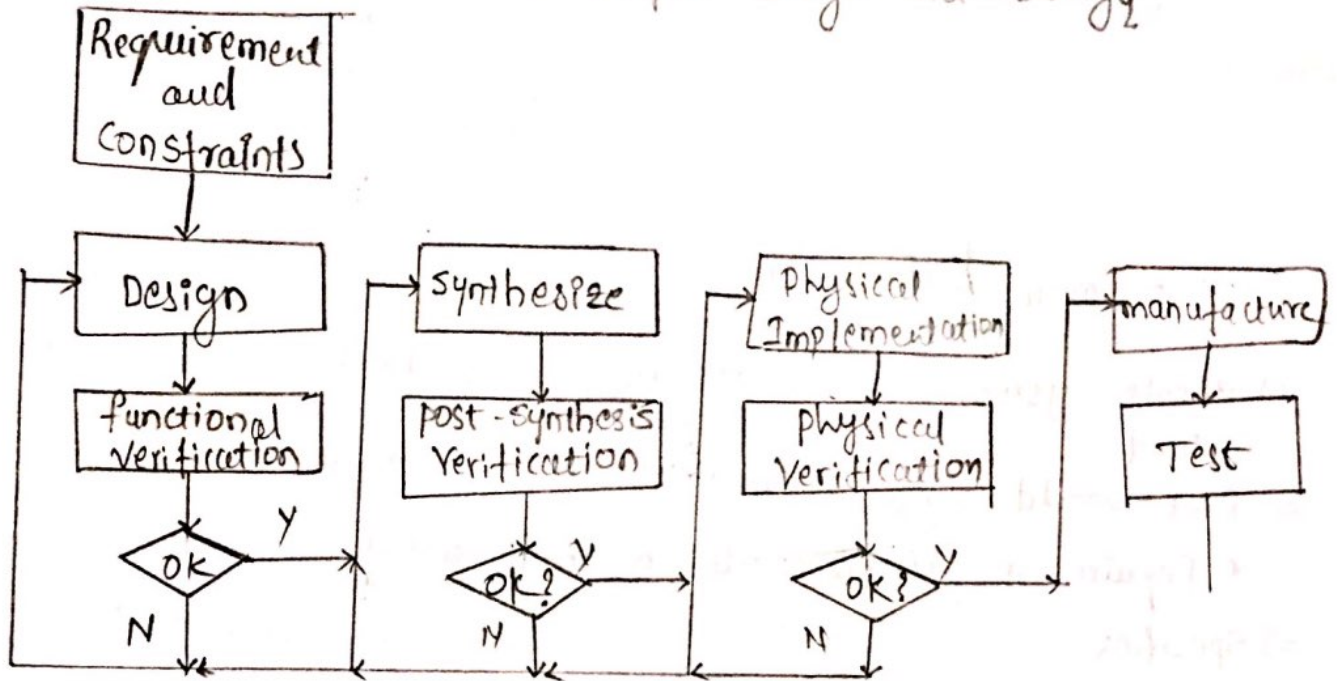

code Design methodology

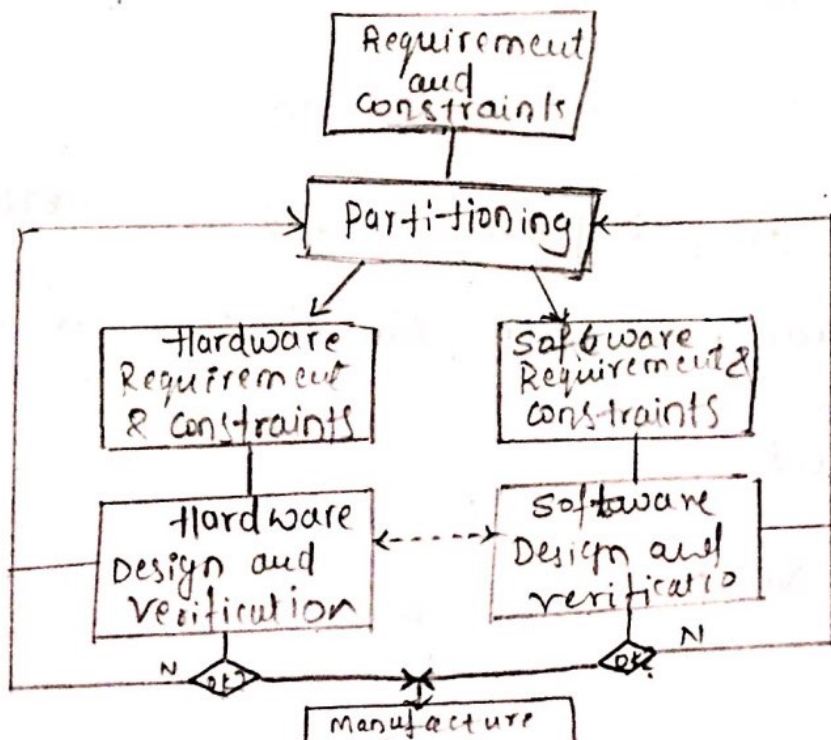


## Hierarchical Design :-

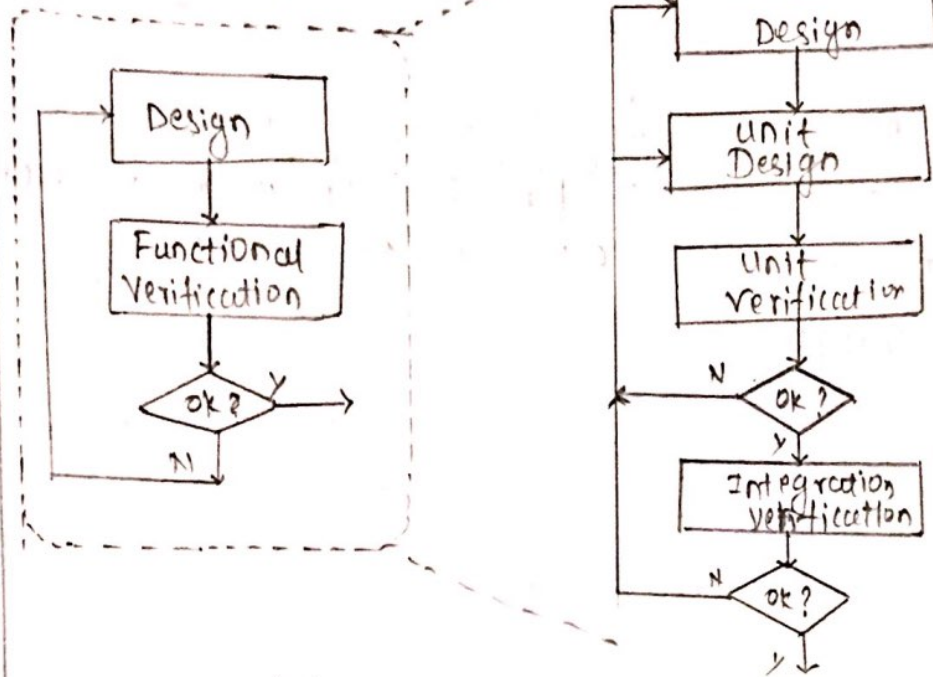

## Design methodology

- ⇒ Simple systems can be design by one person using ad hoc method
- ⇒ Real-world systems are design by teams
  - \* Require a systematic design methodology
- ⇒ Specifies
  - \* Tasks to be undertaken
  - \* Information needed and produced
  - \* Relationships b/w tasks
  - \* EDA tools used
- ⇒ Synthesis
  - \* we usually design using register-transfer level (RTL) verilog
  - \* synthesis tool translates to a circuit of gates that perform the same function
  - \* Specify to the tool.
  - \* post synthesis verifical

2) 8:3 Encoder :-

 

| $z_7$ | $z_6$ | $z_5$ | $z_4$ | $z_3$ | $z_2$ | $z_1$ | $z_0$ | a | b | c | valid |
|-------|-------|-------|-------|-------|-------|-------|-------|---|---|---|-------|
| 1     | x     | x     | x     | x     | x     | x     | x     | 0 | 0 | 0 | 1     |
| 0     | 1     | x     | x     | x     | x     | x     | x     | 0 | 0 | 1 | 1     |
| 0     | 0     | 1     | x     | x     | x     | x     | x     | 0 | 1 | 0 | 1     |
| 0     | 0     | 0     | 1     | x     | x     | x     | x     | 0 | 1 | 1 | 1     |
| 0     | 0     | 0     | 0     | 1     | x     | x     | x     | 1 | 0 | 0 | 1     |
| 0     | 0     | 0     | 0     | 0     | 1     | x     | x     | 1 | 0 | 1 | 1     |
| 0     | 0     | 0     | 0     | 0     | 0     | 1     | x     | 1 | 1 | 0 | 1     |
| 0     | 0     | 0     | 0     | 0     | 0     | 0     | 1     | 1 | 1 | 1 | 1     |

```

module 8-to-3-encod ( output a, b, c,
                    output valid,
                    input [0:7] z);
begin

```

```

    assign c = z[6] | z[4] | z[2] | z[0];

```

```

    assign b = z[5] | z[4] | z[1] | z[0];

```

```

    assign a = z[3] | z[2] | z[1] | z[0];

```

```

    assign valid = z[7] | z[6] | z[5] | z[4] | z[3] | z[2] | z[1] | z[0];


```

```

endmodule

```

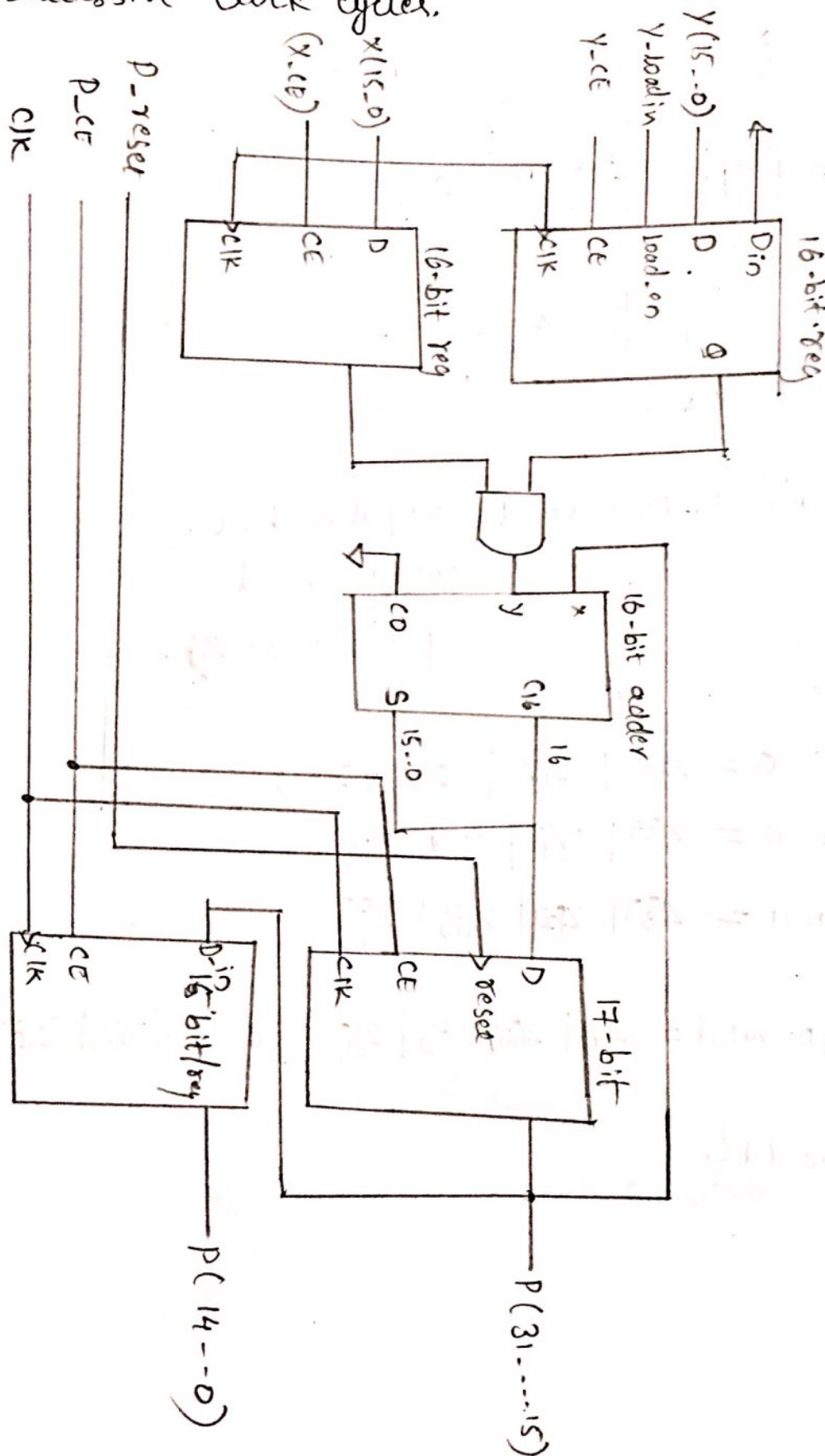
3) Construct a multiplier for two 16-bit operands containing just one adder that adds successive partial products over successive clock cycles.



Explain flip-flop, counters and shift register, explain with syntax & proper example,

Flipflop or latch is a circuit that has two stable states and can be used to store state information

 
Eg: D-Flipflop  
T-Flipflop  
JK-Flipflop



Syntax :-

```
module DFF (Output q, q1,
            input d, c);
    reg q, q1;
    initial
    begin
        q = 1'b0; q1 = 1'b1;
    end
    always @ (posedge c)
    begin
        q = d;
        q1 = ~d;
    end
end module
```

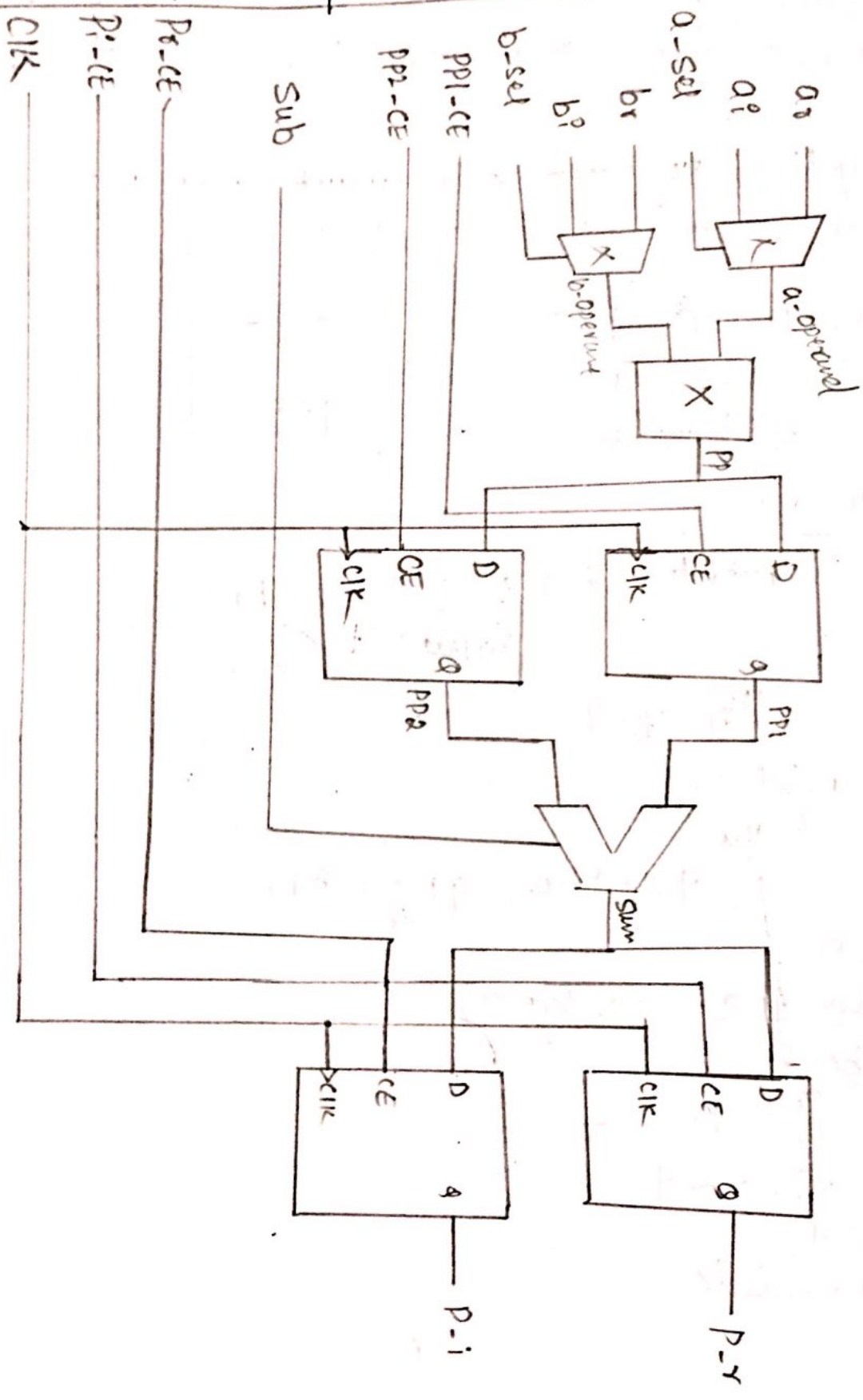4) Construct a datapath to perform a complex multiplication. inputs are 4 pre binary & 12 post binary point.



counters :- A simple form of counter is composed of an edge-triggered register & an incrementer. The value stored in the register is interpreted as an unsigned binary integer. The incrementer can be implemented using the circuit we described for an unsigned incrementer.

ex: up-down counter, Asynch, synch.

### syntax

```
module decoded_counter (output ctrl,  
                        input clk);
```

```
    reg [3:0] count_value;
```

```
    always @ (posedge clk)
```

```
        count_value <= count_value + 1;
```

```
    assign ctrl = count_value == 4'b0111 |
```


```
        count_value == 4'b0111;
```

```
endmodule
```


 
## shift register

A register, as we have seen, stores data and makes it available at the output unchanged. A shift register, on the other hand, can perform a shift operation on the stored data.



syntax .

always @ (LE or D)

if (LE) Q <= D;