

Ans 2:- Op-amp stands for operational amplifier which is a transistorised differential amplifier used for the amplification of difference between the two input voltages.

The five properties of op-amp are as followed:-

\* Open loop gain:- Ideally the gain of the op-amp must be infinite as  $V_o = A_d V_d$  where  $A_d$  is differential or open loop gain &  $V_d$  is the difference voltage as gain will be infinite then it means  $V_1 = V_2$  so that  $V_d \rightarrow 0$

But practically it is not infinite.

Offset voltage:- The presence of small output voltage even if both the inputs  $V_1$  &  $V_2$  are zero is called offset voltage.

Ideally the offset voltage must be zero.

But f

\* CMRR:- It is the ability of the op-amp to reject the common mode signal as it creates noise & disturbances. It is defined as the ratio of differential gain to common mode gain

$$\text{CMRR} = \left| \frac{A_d}{A_{cm}} \right|$$

The CMRR of ideal op-amp must be infinite as  $A_d$  is infinite which tends the  $A_{cm}$  to be zero so that common mode gain will

\* Slew rate:- Slew rate is defined as ratio of change in output voltage w.r.t time. It is actually the parameter which tells that the output changes simultaneously with inputs.

$$S = \frac{\Delta V_o}{\Delta t} \quad \text{or} \quad S = 2\pi f V_m$$

Ideally the slew rate should be infinite but practically it is not  $\infty$ .

\* PSRR:- It is the ratio of change in output offset voltage w.r.t change in one of the supply voltages keeping one supply constant.

$$PSRR = \left. \frac{\Delta V_{ios}}{\Delta V_{CC}} \right|_{V_{EE} = \text{constant}}$$

$$PSRR = \left. \frac{\Delta V_{ios}}{\Delta V_{EE}} \right|_{V_{CC} = \text{constant}}$$

Ideally it should be zero.

\* Infinite bandwidth:- Bandwidth is the range of frequency over which the gain remains constant & ideally it should be infinite.

\* Input impedance:- It is the impedance which is present at any one of the input terminals & ideally input impedance should be infinite.

Q.30. Given it is voltage follower

$$\text{So, } \beta = 1$$

$$A_{OL \text{ min}} = 50,000$$

$$A_{OL \text{ max}} = 2,00,000$$

$$Z_i = 2M\Omega$$

$$Z_o = 75\Omega$$

So, Minimum input impedance with feedback

$$\begin{aligned} Z_{i \text{ min}} &= Z_{im} (1 + A_{OL \text{ min}} \beta) \\ &= 2M\Omega (1 + 50,000 \times 1) \\ &= 1.000 \times 10^{11} \Omega \end{aligned}$$

5

$$\begin{aligned} Z_{i \text{ min max}} &= Z_{im} (1 + A_{OL \text{ max}} \beta) \\ &= 2M\Omega (1 + 2,00,000) \\ &= 4.000 \times 10^{11} \Omega \end{aligned}$$


Output impedance with feedback is given by

$$\begin{aligned} Z_{o \text{ min}} &= \frac{Z_o}{(1 + A_{OL \text{ max}})} \\ &= \frac{75\Omega}{(1 + 2,00,000)} \\ &= \frac{3.749 \times 10^{-4} \Omega \cdot 10^{-2}}{10^{-2}} = 0.3749 \text{ m}\Omega \end{aligned}$$

$$Z_{o \text{ max}} = \frac{Z_o}{(1 + A_{OL \text{ min}})} = \frac{75\Omega}{(1 + 50,000)} = 1.499 \text{ m}\Omega$$



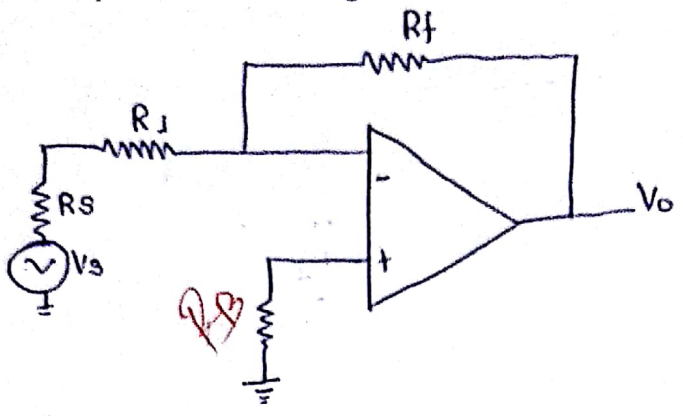Sol:3(b). Direct Coupled Inverting amplifier:-



Given output voltage = 2.5V  
& gain =  $A_v = 50$

So,  $\angle$  gain =  $\frac{V_o}{V_i}$

$$V_{im} = \frac{2.5V}{50} = 0.05V$$

&  $i_p = 100 \times 500nA = 50\mu A$

So,  $R_1 = \frac{V_{im}}{i_p}$   
 $= \frac{0.05V}{50\mu A}$   
 $= 1000\Omega$   
 $= 1k\Omega$

5

&  $A_v = \frac{R_f}{R_1}$


$$R_f = R_1 \times A_v$$

$$= 1k\Omega \times 50$$

$$= 50k\Omega$$

&  $R_{Bias} = R_1 \parallel R_f = 1k\Omega \parallel 50k\Omega = \frac{1k\Omega \times 50k\Omega}{1 + 50k\Omega} = 0.980k\Omega = 980\Omega$
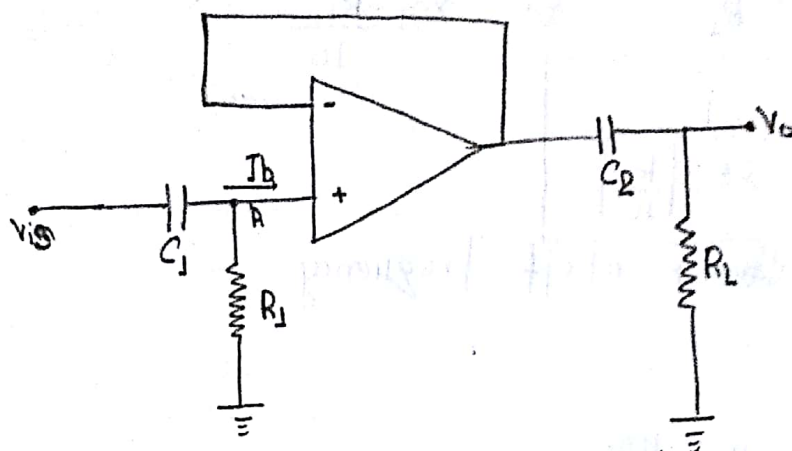
## Sol. 4. Capacitor Coupled Voltage follower:-



For converting into ~~dc~~ <sup>ac</sup> -amplifier we use capacitor coupled voltage follower. Here in input side we place a capacitor but it can block the dc base voltage required for operation of transistor so a resistance  $R_1$  is placed but there is in order of matching the impedance we use  $C_2$  at the output so there is no use of resistance in another terminal:-

Design:-


(i) For calculating  $R_1$  we need

$$R_1 = \frac{0.1 V_{BE}}{I_{B_{min}}} \quad \text{which} \quad \frac{0.07V}{500\mu A} = 140K\Omega$$

(ii) Now to find voltage across A we need voltage divider circuit:-

$$V_A = \frac{V_s \times R_1}{R_1 - jX_{C_1}}$$

$$|V_A| = \frac{V_s \times R_1}{\sqrt{R_1^2 + X_{C_1}^2}}$$

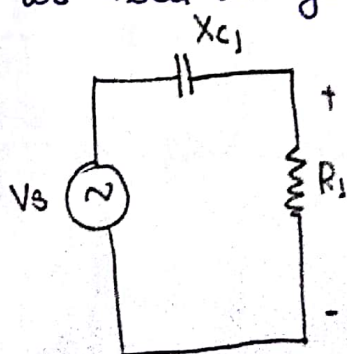

But here  $R_1$  is very high

So,  $\sqrt{R_1^2 + X_{C1}^2} = R_1$       So,  $X_{C1} = \frac{R_1}{10}$

$$C_1 = \frac{1}{2\pi f \left(\frac{R_1}{10}\right)}$$

where  $f$  is lower cutoff frequency

Now, across  $R_L$  we have:

$$\frac{V_o \times R_L}{R_L - jX_{C2}} = V_B$$

$$|NBI| = \frac{V_o \times R_L}{\sqrt{R_L^2 + X_{C2}^2}}$$

when  $R_L = X_{C2}$


$$\frac{V_o}{\sqrt{2}}$$

which means it is -3dB frequency which is cut-off frequency so.

$$R_L = X_{C2}$$

$$C_2 = \frac{1}{2\pi f R_L}$$

\* High impedance Voltage follower:-

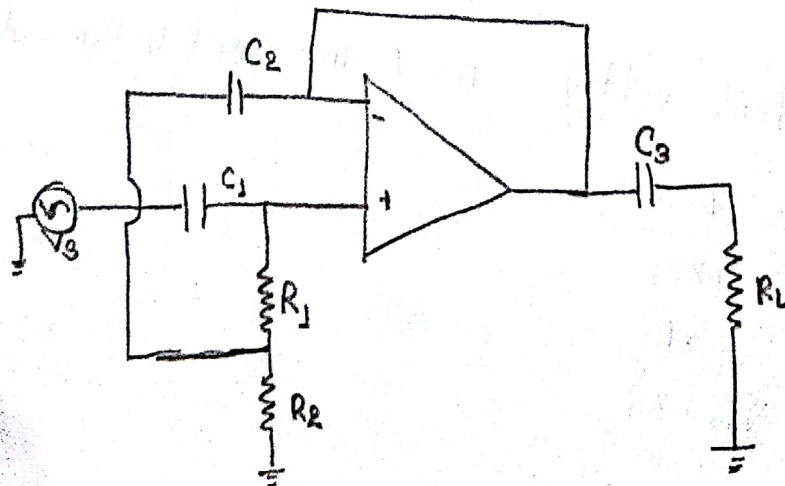



In the previous case the input impedance  $R_1$  was not so high so, we are using this configuration to make it a perfect buffer amplifier:-

We know,  $V_s = V_1 + V_o$

$$V_s = V_1 + \frac{V_{im}}{A_{OL}}$$

$$V_1 = \frac{V_s}{(1 + A_{OL})}$$

$$Z_{im} = \frac{V_s}{\frac{V_s}{R_1(1 + A_{OL})}} = R_1(1 + A_{OL})$$

Design:-

\*  $R_{max} = \frac{0.1 V_{BE}}{I_{B_{max}}} = 140 K\Omega$

$$R_1 + R_2 = R_{max}$$

$$R_1 = R_2 = \frac{R_{max}}{2} = 70 K\Omega \approx 68 K\Omega$$

Now as discussed previously.

$$X_{C_1} = \frac{R_1}{10}$$

$$C_1 = \frac{1}{2\pi f \left(\frac{R_1}{10}\right)}$$

$$C_2 = \frac{1}{2\pi f_L \left(\frac{R_2}{10}\right)}$$

&  $C_3 = \frac{1}{2\pi f_L R_L}$

as  $X_{C_3} = R_L$

good

10

Sol<sup>n</sup>. Given  $R_L = 22K\Omega$

$$V_S = 1.5V$$

$$R_S = 56K\Omega$$

$$Z_o = 75\Omega, Z_{im} = 2M\Omega, A_{OL} = 2 \times 10^5$$

(i) Load is directly connected.

$$\begin{aligned} \text{So, } V_L &= \frac{V_S \times R_L}{(R_S + R_L)} \\ &= \frac{1.5 \times 22K\Omega}{(22K\Omega + 56K\Omega)} \\ &= \frac{1.5 \times 0.22K\Omega}{0.78K\Omega} \\ &= 0.423V \end{aligned}$$


(ii) Load is connected through voltage follower:-

$$Z_{imf} = Z_{im} (1 + A_{OL}\beta) \quad \text{where } \beta = 1.$$

$$\begin{aligned} &(2 \times 10^6) (1 + 2 \times 10^5) \\ &= 4 \times 10^{11} \Omega \end{aligned}$$

$$\begin{aligned} \text{So, } V_{im} &= \frac{V_S \times Z_{imf}}{Z_{imf} + R_S} \\ &= 1.4999V \end{aligned}$$
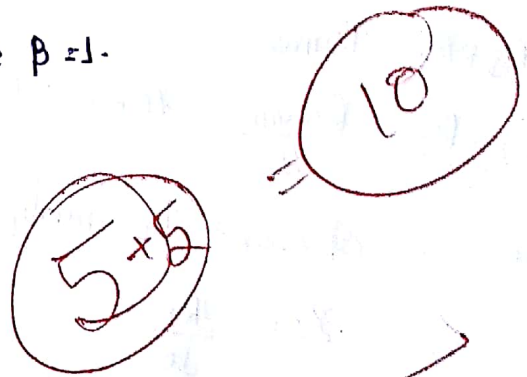
$$\begin{aligned} \text{So, now } V_o &= V_{im} \left[ 1 - \frac{1}{A_{OL}} \right] \\ &= 1.5 \left[ 1 - \frac{1}{2 \times 10^5} \right] \\ &= 1.49999V \end{aligned}$$





$$\begin{aligned}
 \text{So } V_L &= \frac{V_o \times R_L}{R_L + Z_{of}} \\
 &= 1.4999 \times \frac{22 \times 10^3}{(22 \times 10^3) + (3.749 \times 10^{-4})}
 \end{aligned}$$

$$\boxed{V_L = 1.49998 \text{ V}}$$

$$\begin{aligned}
 Z_{of} &= \frac{Z_o}{1 + A_{oL}} \\
 &= \frac{75 \Omega}{(1 + (2 \times 10^5))} \\
 &= 3.7499 \times 10^{-4} \Omega
 \end{aligned}$$

60Hz Given lower cutoff frequency = 50Hz -


$$\begin{aligned}
 I_{Bias} &= 500 \mu\text{A} \\
 R_L &= 8.3 \text{ K}\Omega \\
 A_{oL} &= 10^5
 \end{aligned}$$

$$\begin{aligned}
 \text{Now, we know } R_{max} &= \frac{0.1 V_{BE}}{500 \mu\text{A}} \\
 &= \frac{0.07}{500 \mu\text{A}} \\
 &= 140 \text{ K}\Omega
 \end{aligned}$$

$$\text{So, } R_1 = R_2 = \frac{R_{max}}{2} = 70 \text{ K}\Omega \approx 68 \text{ K}\Omega$$

$$\begin{aligned}
 \text{Now, } X_{C_1} &= \frac{R_1}{10} \\
 \frac{1}{2\pi f C_1} &= 6.8 \text{ K}\Omega
 \end{aligned}$$
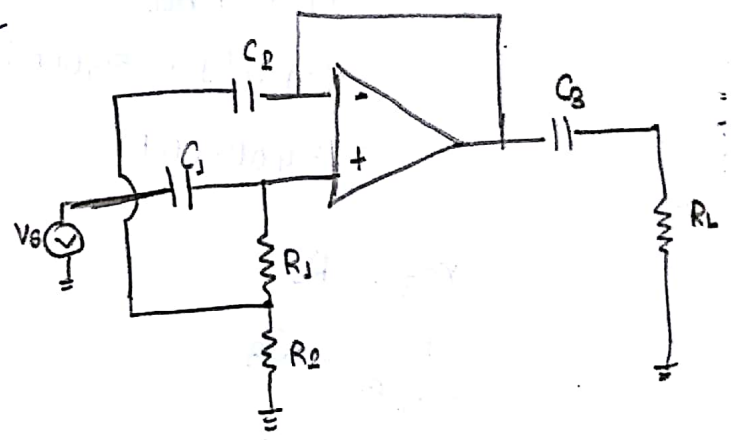
$$\begin{aligned}
 C_1 &= \frac{1}{2\pi f (6.8 \times 10^3)} \\
 &= \frac{1}{2\pi \times 50 (6.8 \times 10^3)} = \frac{1}{10} = 4.681 \times 10^{-7} \text{ F} \\
 &= 0.468 \mu\text{F}
 \end{aligned}$$



$$C_1 = C_2 = 0.4684 \mu\text{f}$$

$$\begin{aligned} Z_{im} &= R_1 (1 + A_{OL}) \\ &= 68\text{k}\Omega (1 + 10^5) \\ &= 6.8 \times 10^9 \Omega \end{aligned}$$

But ideally it will be

$$\begin{aligned} &R_1 (1 + A_{OL}) \\ &= 68\text{k}\Omega (1 + 50,000) \\ &= 3400.06 \text{ M}\Omega \end{aligned}$$

$$X_{C_3} = R_L$$


$$\frac{1}{2\pi f_L R_L} = C_3$$

$$\begin{aligned} C_3 &= \frac{1}{2\pi \times 50 \times (3.3 \times 10^9)} \\ &= 9.645 \times 10^{-7} \text{ F} \end{aligned}$$

$$C_3 = 0.9645 \mu\text{f}$$

10

50. Difference Amplifier:-

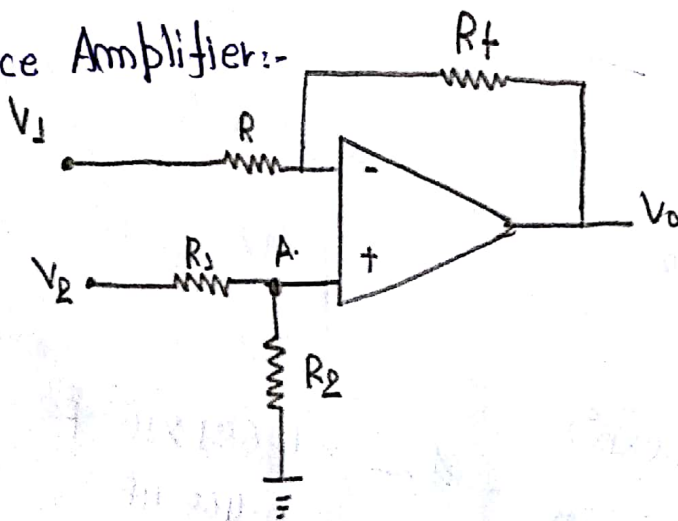

Difference amplifier is also called subtractor which is used to amplify the difference between the two voltages  $V_1$  &  $V_2$ .

In order to calculate it we have to make one active and another ground

Case I) Suppose  $V_1$  is active &  $V_2$  is grounded then it will be inverting amplifier so, the output voltage will be

$$V_0 = -\frac{R_f}{R_1} (V_1)$$

Case II. Now, Suppose here  $V_2$  is active &  $V_1$  is grounded then it will become non-inverting amplifier with output voltage

$$V_0 = \left(1 + \frac{R_f}{R}\right) V_A$$

good

& by potential divider we have

$$V_A = V_2 \times \frac{R_2}{(R_1 + R_2)}$$

$$V_0 = \left(1 + \frac{R_f}{R}\right) \frac{V_2 R_2}{(R_1 + R_2)}$$

5

$$V_0 - \frac{R_f}{R} V_1 = \frac{V_2 R_2}{(R_1 + R_2)} + \frac{R_f}{R} \frac{V_2 R_2}{(R_1 + R_2)}$$

$$\text{So, } V_0 = \frac{R_f}{R} (V_1 - V_2) = \frac{R_2}{R_1} (V_1 - V_2)$$




And it's input resistance is.

$$Z_{in} = R + R_1 + R_2$$

$$Z_{om} = R \parallel (R_1 + R_2)$$

(b) Non-inverting summing amplifier:-

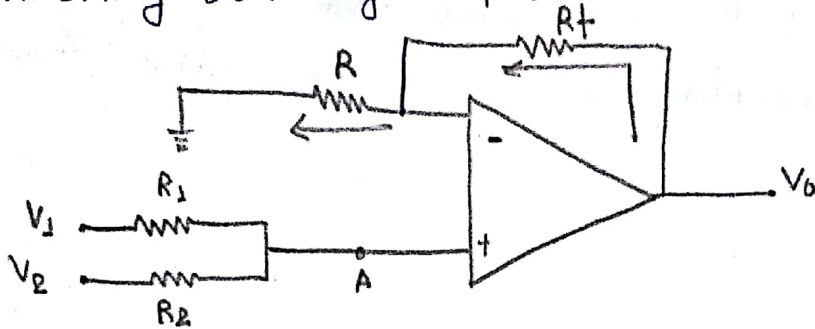

Here,  $I_1 = \frac{V_1 - V_A}{R_1}$

$$I_2 = \frac{V_2 - V_A}{R_2}$$

$$I_1 + I_2 = 0.$$

$$\frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2} = 0.$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = V_A \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\boxed{\frac{V_1 R_2 + V_2 R_1}{R_1 + R_2} = V_A}$$

Now by virtual ground we have

$$V_A = V_B.$$

5

Now,  $\frac{V_0 - V_B}{R_f} = \frac{V_B}{R}$

$$V_0 = \left(1 + \frac{R_f}{R}\right) V_B$$


So, here we have to substitute the value of  $V_B$

$$V_0 = \left(1 + \frac{R_f}{R}\right) \left(\frac{V_1 R_2 + V_2 R_1}{R_1 + R_2}\right)$$

As the two voltages  $V_1$  &  $V_2$  are applied to the non-inverting terminal so it is non-inverting summer.

Here it is collectively amplifying the voltage  $V_1$  &  $V_2$  to  $V_0$ .

Sol. 1. Basic op-amp circuit:-

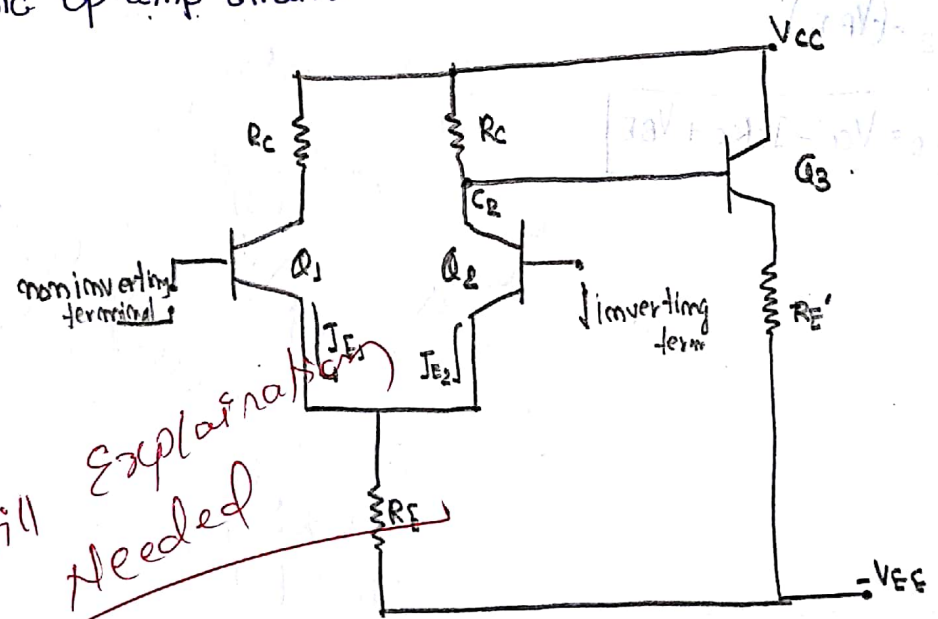

*Still explanation needed*

Here the base terminal of  $Q_1$  is non-inverting terminal where as base terminal of  $Q_2$  is inverting terminal.

Here in op-amp all the voltages  $V_{BE1}$  &  $V_{BE2}$  should be perfectly matched i.e  $V_{BE1} = V_{BE2} = V_{BE}$

& all the currents  $I_{E1}$  &  $I_{E2}$  should be same

$$\text{So, } I_{E1} = I_{E2} = I_E$$

$$V_{BE} + 2I_E R_E = V_{EE}$$

$$I_E = \frac{V_{EE} - V_{BE}}{2R_E}$$

Now at output side

$$I_C = I_E = I_{CQ}$$

$$\text{So, } V_{CE2} = V_{CC} - I_{CQ} R_C$$

where as

$$V_{CE2} = V_{C2} - (V_{BE})$$

$$V_{CE2} = V_{CC} - I_{CQ} R_C + V_{BE}$$

Taking some Resistor values  
finding  $V_{CE2}$  voltage when  
i/p is applied to inverting  
& non inverting.