



Internal Assessment Test – II

Sub:	LINEAR INTEGRATED CIRCUIT	Code:	15EC46
Date:	19/ 04 / 2018	Duration:	90 mins
		Max Marks:	50
		Sem:	IV
		Branch:	TCE
Answer Any FIVE FULL Questions			

OBE
Marks CO RBT

1 Explain the working of RC- phase shift oscillator using OPAMP and derive the frequency of oscillation. [10] CO4 L4

RC PHASE SHIFT OSCILLATOR:

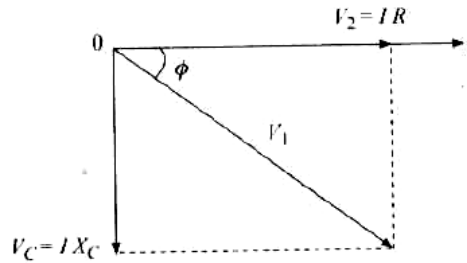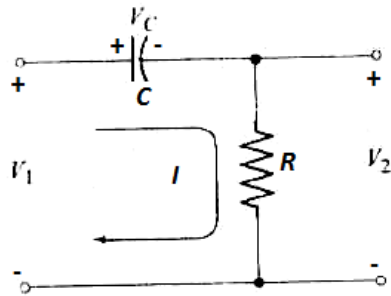


Explanation(5
marks)+Frequency
Derivation(5 marks)

$$A = \frac{V_o}{V_i} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC} \text{ hence } \theta = \tan^{-1}\left(\frac{\omega RC}{0}\right) - \tan^{-1}\left(\frac{\omega RC}{1}\right)$$

$$\Rightarrow \theta = \tan^{-1}(\infty) - \tan^{-1}\left(\frac{\omega RC}{1}\right) \Rightarrow \theta = 90^\circ - \tan^{-1}(\omega RC)$$

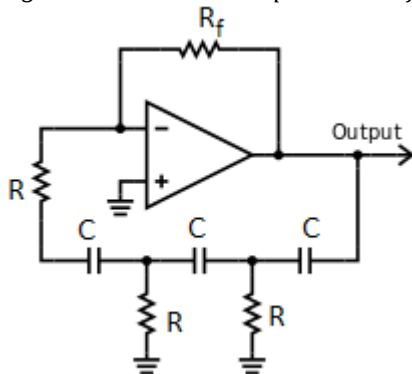hence when $\omega = 0$ then only we can get $\theta = 90^\circ$
angle θ will never be equal to 90° for a single RC network



The RC network connected between the amplifier output and input terminal consists of three resistors and capacitors. Resistor R_1 functions as the last resistors in the phase shift network and as the amplifier input resistance. The phase shift network is a phase lead network.


The frequency of the oscillator output depends upon the capacitor and resistor values of the phase shift network.

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

The phase shift network attenuates the amplifier output by a factor 29 i.e.

$$|\beta| = \left|\frac{1}{29}\right|$$

Hence the amplifier must have the voltage gain greater than or equal to 29. If the amplifier gain is less than 29, the circuit will not oscillate. When the gain is substantially greater than 29, the oscillator output waveform is likely to be distorted. A gain just slightly greater than 29 gives a reasonably undistorted sinusoidal waveform.

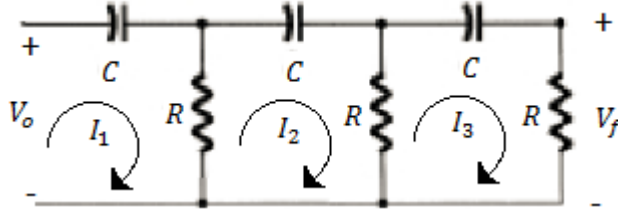

LOOP1:

$$V_o = I_1 \times \frac{1}{j\omega C} + (I_1 - I_2)R \quad \Rightarrow V_o = I_1 \times \left(\frac{1}{j\omega C} + R \right) - I_2 R \quad \text{--- (1)}$$

LOOP2:

$$0 = I_2 \times \frac{1}{j\omega C} + (I_2 - I_3)R + (I_2 - I_1)R \quad \Rightarrow 0 = -I_1 R + I_2 \left(\frac{1}{j\omega C} + 2R \right) - I_3 R \quad \text{--- (2)}$$

LOOP3:

$$0 = I_3 \times \frac{1}{j\omega C} + I_3 R + (I_3 - I_2)R \quad \Rightarrow 0 = -I_2 R + I_3 \left(\frac{1}{j\omega C} + 2R \right) \quad \text{--- (3)}$$

$$\begin{bmatrix} V_o \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} \left(\frac{1}{j\omega C} + R \right) & -R & 0 \\ -R & \left(\frac{1}{j\omega C} + 2R \right) & -R \\ 0 & -R & \left(\frac{1}{j\omega C} + 2R \right) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

By Cramer's Rule:

$$I_3 = \frac{\Delta_3}{\Delta}$$

$$\Delta_3 = \begin{vmatrix} \left(\frac{1}{j\omega C} + R \right) & -R & V_o \\ -R & \left(\frac{1}{j\omega C} + 2R \right) & 0 \\ 0 & -R & 0 \end{vmatrix} = V_o \times R^2$$

$$\Delta = \left(\frac{1}{j\omega C} + R \right) \left\{ \left(\frac{1}{j\omega C} + 2R \right)^2 - R^2 \right\} + R \left\{ -R \times \left(\frac{1}{j\omega C} + 2R \right) \right\}$$

$$\Delta = \left(\frac{1}{j\omega C} + R \right) \left\{ \frac{1}{j^2 \omega^2 C^2} + 4R^2 + \frac{4R}{j\omega C} - R^2 \right\} + R \left(\frac{-R}{j\omega C} - 2R^2 \right)$$

$$\Delta = \left(\frac{1}{j\omega C} + R \right) \left\{ \frac{1}{j^2 \omega^2 C^2} + 3R^2 + \frac{4R}{j\omega C} \right\} + \left(\frac{-R^2}{j\omega C} - 2R^3 \right)$$

$$\Delta = \frac{1}{j^3 \omega^3 C^3} + \frac{3R^2}{j\omega C} + \frac{4R}{j^2 \omega^2 C^2} + \frac{R}{j^2 \omega^2 C^2} + 3R^3 + \frac{4R^2}{j\omega C} - \frac{R^2}{j\omega C} - 2R^3$$

$$\Delta = \frac{1}{j^3 \omega^3 C^3} + \frac{6R^2}{j\omega C} + \frac{5R}{j^2 \omega^2 C^2} + R^3$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{V_o \times R^2}{\frac{1}{j^3 \omega^3 C^3} + \frac{6R^2}{j\omega C} + \frac{5R}{j^2 \omega^2 C^2} + R^3}$$

$$V_f = I_3 R = \frac{V_o \times R^3}{\frac{1}{j^3 \omega^3 C^3} + \frac{6R^2}{j\omega C} + \frac{5R}{j^2 \omega^2 C^2} + R^3} \Rightarrow V_f = \frac{V_o}{\frac{1}{j^3 \omega^3 R^3 C^3} + \frac{6R^2}{j\omega R^3 C} + \frac{5R}{j^2 \omega^2 R^3 C^2} + \frac{R^3}{R^3}}$$

$$\Rightarrow V_f = \frac{V_o}{\frac{1}{j^3 \omega^3 R^3 C^3} + \frac{6}{j\omega R C} + \frac{5}{j^2 \omega^2 R^2 C^2} + 1} = \frac{j}{\omega^3 R^3 C^3 - \frac{j6}{\omega R C} + \frac{-5}{\omega^2 R^2 C^2} + 1}$$

$$\Rightarrow V_f = \frac{V_o}{\left(1 - \frac{5}{\omega^2 R^2 C^2}\right) + j\left(\frac{1}{\omega^3 R^3 C^3} - \frac{6}{\omega RC}\right)}$$

Let $\frac{1}{\omega RC} = \alpha$ hence $V_f = \frac{V_o}{(1 - 5\alpha^2) + j(\alpha^3 - 6\alpha)}$

$$\text{Loop Gain} = \beta = \frac{V_f}{V_o} = \frac{1}{(1 - 5\alpha^2) + j(\alpha^3 - 6\alpha)}$$

Loop gain is real hence imaginary part has to be zero. $\alpha^3 - 6\alpha = 0 \Rightarrow \alpha^3 = 6\alpha \Rightarrow \alpha = \sqrt{6}$

$$\text{As } \alpha = \frac{1}{\omega RC} \Rightarrow \sqrt{6} = \frac{1}{\omega RC} \Rightarrow \omega = \frac{1}{RC\sqrt{6}} \Rightarrow 2\pi f = \frac{1}{RC\sqrt{6}} \Rightarrow f = \frac{1}{2\pi RC\sqrt{6}}$$

$$\beta = \frac{1}{(1 - 5\alpha^2)} = \frac{1}{(1 - 5 \times 6)} = -\frac{1}{29}$$

negative sign indicates that the phase shift is 180°

$$|\beta| = \left|\frac{1}{29}\right|$$

Hence for loop gain to be greater than unity, the gain of the amplifier must be $A > 29$

As the amplifier is the inverting amplifier the gain is

$$A_v = \frac{-R_f}{R_1} \geq 29 \Rightarrow R_f \geq 29R_1$$

- 2 **Design a Non-inverting amplifier to be capacitor coupled at input and output. The load resistor is $2.2\text{K}\Omega$, lower cut-off frequency is 120Hz . Make necessary modifications to give highest input impedance and determine capacitor values for $V_i = 15\text{mV}$ and $A_v = 66$.** [10] CO2 L3

$$I_2 = 100I_{B(\text{max})} = 100 \times 500\text{nA} = 50\mu\text{A}$$

$$R_3 = \frac{V_{R3}}{I_2} = \frac{V_i}{I_2} = \frac{15\text{mV}}{50\mu\text{A}} = 300\Omega \approx 270\Omega \text{ (standard register)}$$

$$V_o = A_v V_i = 66 \times 15\text{mV} = 990\text{mV}$$

$$R_2 + R_3 = \frac{V_o}{I_2} \Rightarrow R_2 + R_3 = \frac{990\text{mV}}{50\mu\text{A}} = 19.8\text{K}\Omega \Rightarrow R_2 + R_3 = 19.8\text{K}\Omega \Rightarrow R_2 = 19.8\text{K}\Omega - R_3$$


$$\Rightarrow R_2 = 19.8\text{K}\Omega - 270\Omega \Rightarrow R_2 = 19.53\text{K}\Omega \approx 18\text{K}\Omega \text{ (standard value)}$$

$$R_{\text{max}} = \frac{0.1V_{BE}}{I_{B(\text{max})}} = \frac{0.1 \times 0.7}{500\text{nA}} = 140\text{K}\Omega \approx 120\text{K}\Omega \text{ (Standard Value)}$$

$$C_1 = \frac{1}{2\pi f \left(\frac{R_1}{10}\right)} \Rightarrow C_1 = \frac{1}{2\pi \times 120 \times \left(\frac{120\text{K}\Omega}{10}\right)} = 0.11\mu\text{F} \approx 0.1\mu\text{F} \text{ (Standard Value)}$$

$$C_2 = \frac{1}{2\pi f R_L} = 0.6\mu\text{F} \approx 0.68\mu\text{F} \text{ (Standard Value)}$$

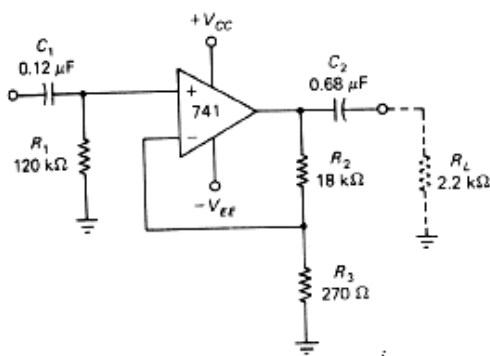General Design (5 marks)+ High impedance circuit Design (5 marks)



For High Input Impedance:

$$R_1 + R_3 = R_{(\text{max})} = \frac{0.1V_{BE}}{I_{B(\text{max})}} = \frac{0.1 \times 0.7}{500\text{nA}} = 140\text{K}\Omega \approx 120\text{K}\Omega \text{ (Standard Value)}$$

As $R_2 \approx 18K\Omega$ and $R_3 \approx 270\Omega$

hence $R_1 = R_{(max)} - R_3 \Rightarrow R_1 = 120K\Omega - 270\Omega = 119.73K\Omega$

As Z_{in} is very high hence C_1 has to be very small but its capacitance value should be greater than stray capacitance.


$$C_1 = 1000pF$$

$$X_{C_3} = \frac{R_L}{10}$$

$$C_3 = \frac{1}{2\pi f \left(\frac{R_L}{10}\right)} \Rightarrow C_3 = \frac{1}{2\pi \times 120 \times \left(\frac{2.2K\Omega}{10}\right)} \Rightarrow C_3 = 6.028\mu F$$

$$X_{C_2} = R_3$$
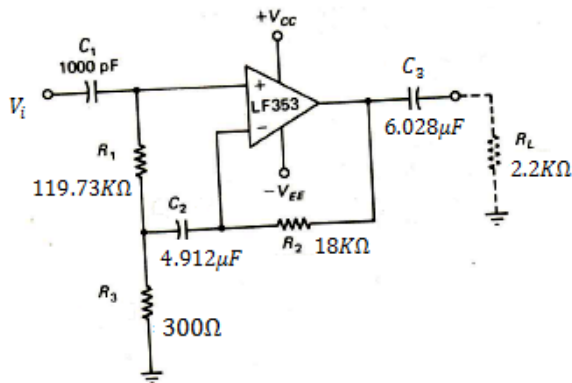
$$C_2 = \frac{1}{2\pi f R_3} = \frac{1}{2\pi \times 120 \times 270} = 4.912\mu F$$



- 3 The inverting amplifier designed with $V_o = 2.5V$ and $A_V = 50$, is to be capacitor coupled and to have a signal frequency range of 10Hz to 1KHz. If the load resistance is 250Ω. Calculate the required capacitor values [10] CO2 L2

R_1 and R_2 resistors can be calculated from the direct coupled inverting amplifier cir

$$I_1 = 100 \times I_{B(max)} = 100 \times 500nA = 50\mu A$$

$$V_i = \frac{V_o}{A_V} = \frac{2.5V}{50} = 0.05V$$

$$R_1 = \frac{V_i}{I_1} = \frac{0.05}{50\mu A} = 1K\Omega \text{ (Standard Value)}$$


$$R_2 = \frac{V_o}{I_1} = \frac{2.5}{50\mu A} = 50K\Omega \approx 47K\Omega \text{ (Standard Value)}$$

$$C_1 = \frac{1}{2\pi f_L \left(\frac{R_1}{10}\right)} \Rightarrow C_1 = \frac{1}{2\pi \times 10 \times \left(\frac{1K\Omega}{10}\right)} \Rightarrow C_1 = 0.159\mu F$$

$$C_2 = \frac{1}{2\pi f_L R_L} = \frac{1}{2\pi \times 10 \times 250\Omega} = 63.66\mu F$$

$$C_f = \frac{1}{2\pi f_H R_2} = \frac{1}{2\pi \times 1KHz \times 47K\Omega} = 3386.27pF$$

Calculation (5 marks)+ diagram (5 marks)

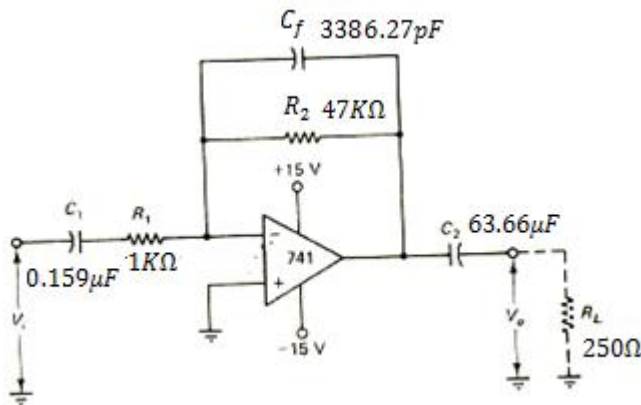

- 4 (a) What output voltage would be produced by a D/A converter whose output range is 0 to 10V and whose input binary number is [5] CO3 L1
- 10 (2-bit DAC)
 - 0110 (4-bit DAC)
 - 10111100(8-bit DAC)

ANSWER:

(5 marks)


- $V_0 = 10 \left(\frac{1}{2} \times 1 + \frac{1}{4} \times 0 \right) = 5V$
- $V_0 = 10 \left(\frac{1}{2} \times 0 + \frac{1}{4} \times 1 + \frac{1}{8} \times 1 + \frac{1}{16} \times 0 \right) = 3.75V$
- $V_0 = 10 \left(\frac{1}{2} \times 1 + \frac{1}{2^2} \times 0 + \frac{1}{2^3} \times 1 + \frac{1}{2^4} \times 1 + \frac{1}{2^5} \times 1 + \frac{1}{2^6} \times 1 + \frac{1}{2^7} \times 0 + \frac{1}{2^8} \times 0 \right) = 7.34V$

- (b) Explain the working of A to D converter using successive approximation method. [5] CO3 L4

SUCCESSIVE APPROXIMATION CONVERTER:


Diagram (3 marks)+
Explanation (2 marks)

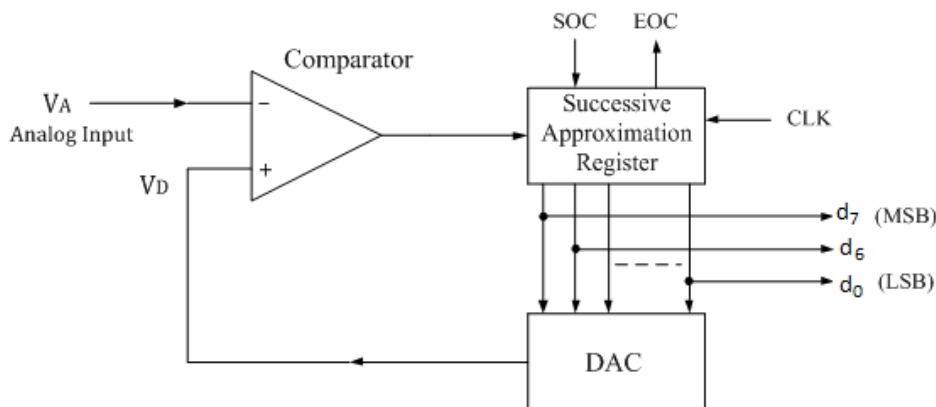- The successive approximation technique was a very efficient code search strategy to complete n-bit conversion in just n-clock period.
- E.g. an eight bit converter requires eight clock pulses to obtain a digital output.
- The circuit uses a successive approximation register (SAR) to find the required value of each bit by trial and error.




- With the arrival of START command, the SAR sets the MSB $d_7 = 1$ with all other bits to zero, so that the trial code is 10000000.
- The output V_d of the DAC is now compared with analog input V_a , if V_a is greater than V_d , then 10000000 is less than the correct digital representation. The MSB remains at '1' and the next lower significant bit is made '1' and further tested.
- However, if V_a is less than the DAC output, then 10000000 is greater than the current digital representation. So, reset the MSB to '0' and go on to the next lower significant bit.
- This procedure is repeated for all subsequent bits, one at a time, until all the bit position has been tested.
- When DAC output crosses V_a , the comparator changes state and this can be taken as the end of conversion (EOC) command.

Correct Digital Representation	Successive Approximation Register output V_d at different stages in the conversion	Comparator Output
11010100(212)	10000000(128)	1
	11000000(192)	1
	11100000(224)	0
	11010000(208)	1
	11011000(216)	0
	11010100(212)	1
	11010110(214)	0
	11010101(213)	0
	11010100(212)	

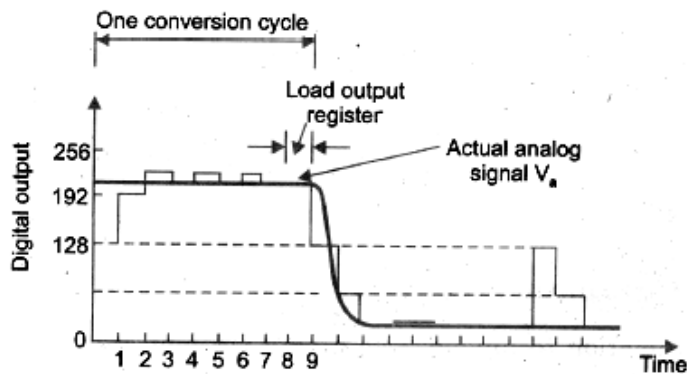

The D/A output voltage is seen to become successively closer to the actual analog input voltage

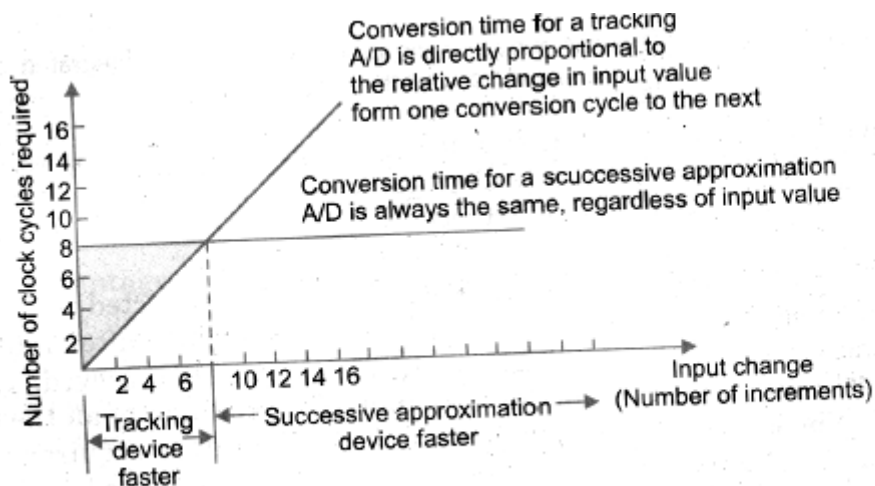9. It is seen that the DAC output voltage is closer to the actual input voltage. It requires 8 pulses to establish the accurate output regardless the value of the analog input. One additional clock pulse is required to load the output register and reinitialize the circuit.



Comparison of conversion times for tracking and successive approximation A/D

10. It is seen that successive approximation technique is more versatile. The tracking circuit is faster only for small changes in the input.

5 Explain the instrumentation amplifier with differential input/output which accepts a differential input voltage and amplifies it to produce a differential output using OPAMP


[10] CO2 L4

INSTRUMENTATION AMPLIFIER:

Instrumentation amplifier is the front end component of every measuring


Diagram (5 marks)+
Explanation (5 marks)

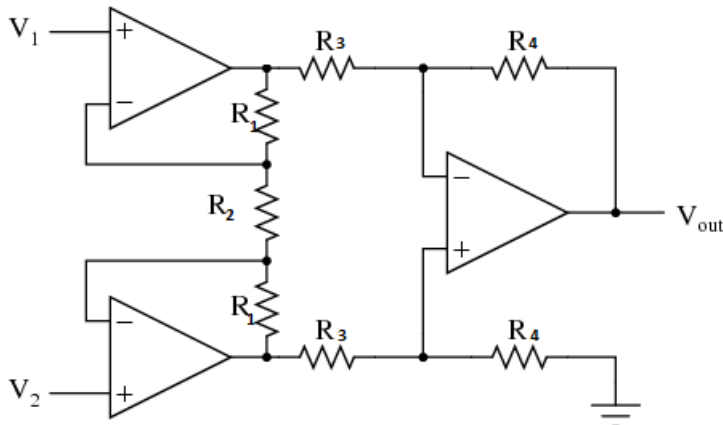instrument which receives the signal from the input electrical signal from the transducer. It uses the fact the noise is common to the both output terminals of a transducer across which the output is measured and sent to measuring instrument.



Differential input differential Output Amplifier:

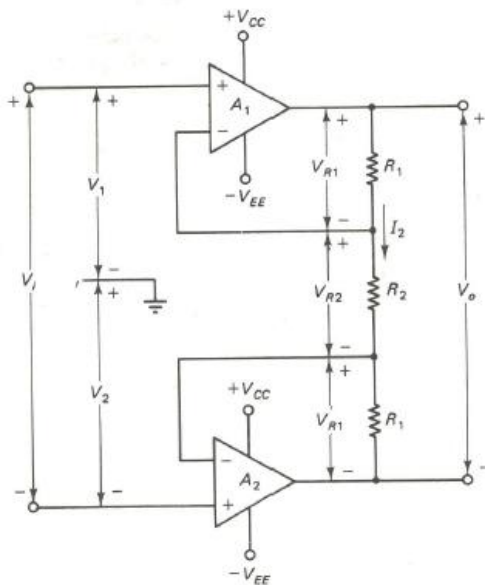This circuit accepts a differential input voltage and produces a differential output. The voltage at the junction of R_1 and R_2 is equal to the input voltage. Also, the voltage at the junction of R_2 and R_3 equals input voltage V_2 . The voltage across R_2 is



$$V_{R2} = V_1 - V_2 = V_i$$

The circuit current through R_2 as $I_2 = \frac{V_i}{R_2}$

The differential output voltage is

$$V_o = V_{R1} + V_{R2} + V_{R3} = I_2(R_1 + R_2 + R_3) = \frac{V_i}{R_2}(R_1 + R_2 + R_3)$$


The circuit differential voltage gain is

$$A_V = \frac{V_o}{V_i} = \frac{R_1 + R_2 + R_3}{R_2} \text{ normally } R_1 = R_3 \text{ hence } A_V = \frac{2R_1 + R_2}{R_2}$$

(Voltage gain can be altered by adjusting a single resistor R_2)

Suppose 2 inputs are connected together and a common mode noise voltage V_n is applied to the two. The junction of R_1 and R_2 will be at the same voltage as the non-inverting input terminal of A_1 and the junction of R_2 and R_3 will be at the same potential as the non-inverting input of A_2 . That is both resistor junctions will be at V_n . There will be no current flow through R_1, R_2 or R_3 and the output of the amplifier will be V_n . This means the common mode gain is

$$A_{V(cm)} = 1$$

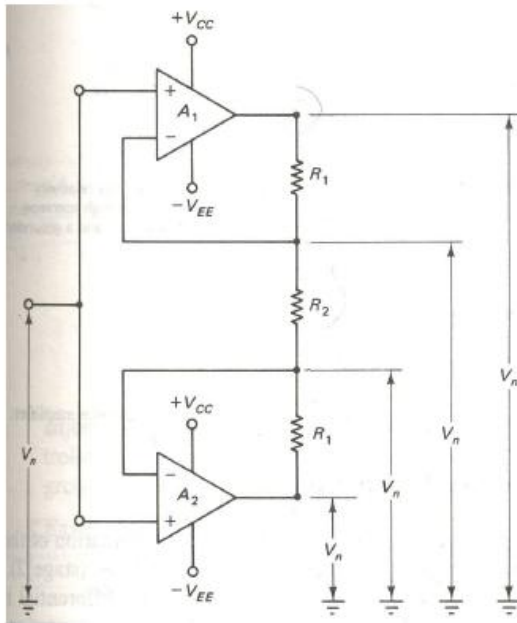


[A common mode voltage applied to a differential input and differential output amplifier]

So common mode signals will be passed through but not amplified by the differential input differential output amplifier.

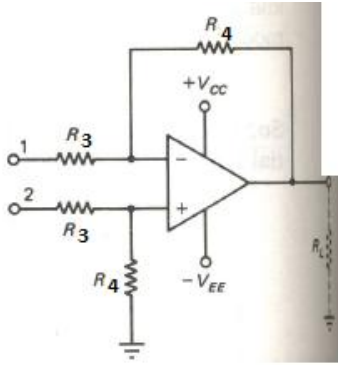1. The differential input and differential output amplifier is used in conjunction with the difference amplifier. The input impedance of differential input differential output amplifier is extremely high because of the non-inverting amplifier configuration. The input impedance of the differential amplifier is $R_i = R_1$ at the inverting terminal and $R_i = (R_3 + R_4)$ at the non-inverting terminal.
2. The voltage gain of the differential input and differential output stage can be changed by adjusting only one resistor R_2 . Changing the gain of the differential amplifier requires R_2 and R_4 to be adjusted together to maintain equal amplification of both inputs.
3. The common mode gain of the differential input/output amplifier is 1, compared to common mode gain of zero for the difference amplifier.
4. The differential input/output amplifier operates with a floating load, while the difference amplifier uses a grounded load.

Differential Amplifier:

The instrumentation amplifier is a combination of differential input/output amplifier (stage 1) and difference amplifier (stage 2). The voltage gain of the complete circuit is



$$A_V = A_{V1} \cdot A_{V2}$$

Where $A_{V1} = \left(1 + \frac{2R_1}{R_2}\right)$ and $A_{V2} = \frac{R_4}{R_3}$

$$A_V = \left(1 + \frac{2R_1}{R_2}\right) \left(\frac{R_4}{R_3}\right)$$

Instrumentation amplifier is a combination of the differential input/output amplifier (Stage 1) and difference amplifier (stage 2)

$$A_V = \left(1 + \frac{2R_1}{R_2}\right) \left(\frac{R_4}{R_3}\right) \quad \text{The overall gain can be controlled by adjustment of } R_2$$

6 **Draw the circuit of OPAMP Astable Multivibrator and explain its operation.**

[10] CO3 L2

ASTABLE MULTIVIBRATOR:

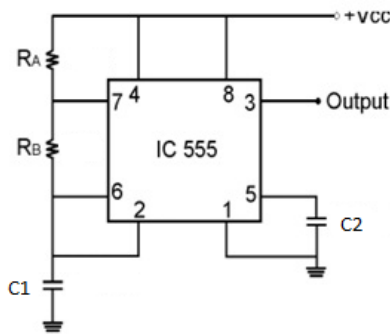


Diagram (5 marks)+
Explanation (5 marks)

Asymmetric

1. When the power supply V_{CC} is connected, the external timing capacitor C charges towards V_{CC} with a time constant $(R_A + R_B)C$. During this time the upper comparator produces the output as LOW and the lower comparator produces the output as HIGH. Hence the output of the S-R flip-flop is HIGH. i.e. $Q = 1$ (HIGH) and $\bar{Q} = 0$ (LOW). At the same time transistor Q_1 is OFF.
2. When the capacitor voltage is just greater than $\frac{2}{3}V_{CC}$, the upper comparator produces HIGH output and the lower comparator output is LOW. Hence the output of the S-R flip-flop is LOW. i.e. $Q = 0$ (LOW) and $\bar{Q} = 1$ (HIGH). So the transistor Q_1 is ON and the capacitor starts discharging towards ground through R_B .
3. During the discharge of the capacitor C , as it reaches just less than $\frac{1}{3}V_{CC}$, the lower comparator produces the output HIGH and the upper comparator produces the output as LOW. Hence the output of the S-R flip-flop is HIGH. i.e. $Q = 1$ (HIGH) and $\bar{Q} = 0$ (LOW). At the same time transistor Q_1 is OFF, so the capacitor starts charging.

4. The capacitor is thus periodically charged and discharged between $\frac{2}{3}V_{CC}$ and $\frac{1}{3}V_{CC}$ respectively.

Capacitor voltage at any instant of time can be calculated as

$$V_C(t) = V_{C(\text{final})} + [V_{C(\text{initial})} - V_{C(\text{final})}]e^{-\frac{t}{\tau}}$$

$$V_C(t) = V_{CC} + \left[\frac{1}{3}V_{CC} - V_{CC}\right]e^{-\frac{t}{(R_A+R_B)C}} \quad \text{as } \tau = (R_A + R_B)C$$


$$V_C(t) = V_{CC} + \left[-\frac{2}{3}V_{CC}\right]e^{-\frac{t}{(R_A+R_B)C}}$$

$$\text{at } t = T_{ON}, V_C(t) = \frac{2}{3}V_{CC}$$

$$\frac{2}{3}V_{CC} = V_{CC} - \frac{2}{3}V_{CC}e^{-\frac{T_{ON}}{(R_A+R_B)C}} \Rightarrow \frac{2}{3}V_{CC} - V_{CC} = -\frac{2}{3}V_{CC}e^{-\frac{T_{ON}}{(R_A+R_B)C}}$$

$$\Rightarrow -\frac{1}{3}V_{CC} = -\frac{2}{3}V_{CC}e^{-\frac{T_{ON}}{(R_A+R_B)C}} \Rightarrow 1 = 2e^{-\frac{T_{ON}}{(R_A+R_B)C}} \Rightarrow \frac{1}{2} = e^{-\frac{T_{ON}}{(R_A+R_B)C}}$$
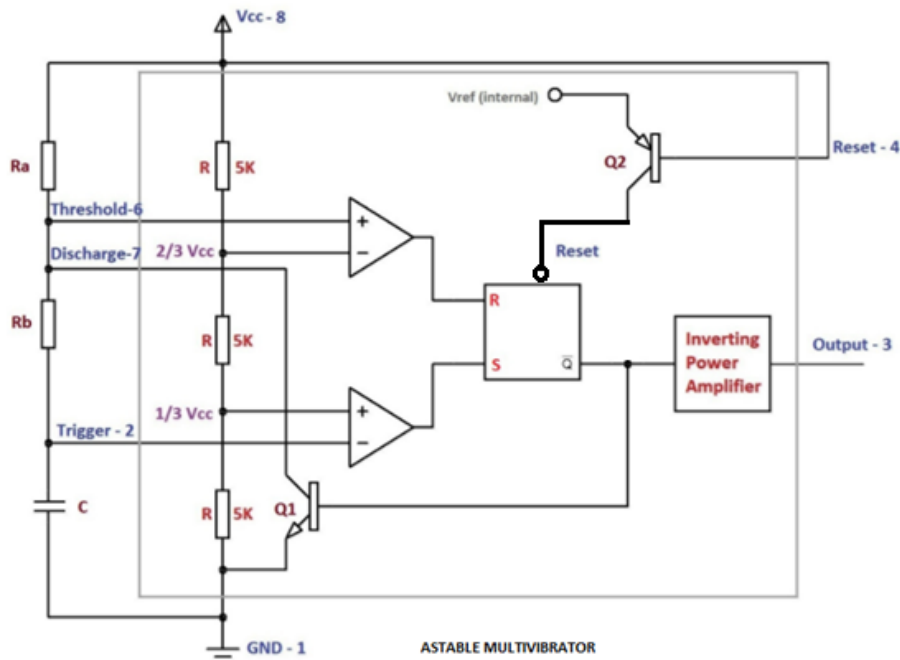
$$\Rightarrow \ln\left(\frac{1}{2}\right) = -\frac{T_{ON}}{(R_A + R_B)C} \Rightarrow -0.693 = -\frac{T_{ON}}{(R_A + R_B)C} \Rightarrow T_{ON} = 0.693(R_A + R_B)C$$




Similarly T_{OFF} can be derived as $T_{OFF} = 0.693R_B C$

$$\text{Duty Cycle, } D = \frac{T_{ON}}{T}$$

$$T = T_{ON} + T_{OFF}$$
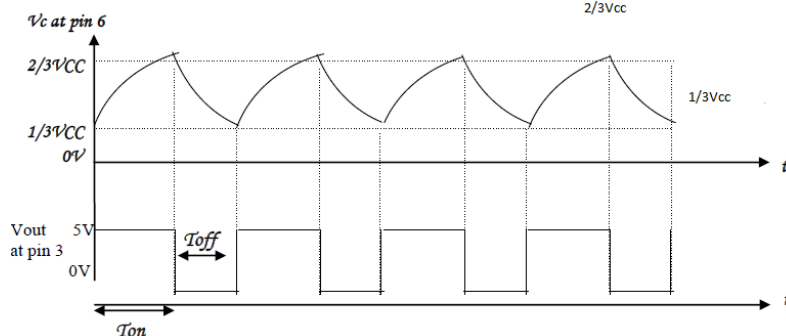
$$\text{Duty Cycle } D = \frac{T_{ON}}{T_{ON} + T_{OFF}} = \frac{0.693(R_A + R_B)C}{0.693(R_A + 2R_B)C} = \frac{R_A + R_B}{R_A + 2R_B}$$



- 7 (a) Design a precision voltage source to provide an output of 9V, the available supply is $\pm 12V$. Allow for approximately $\pm 10\%$ tolerance on the zener voltage.

[5] CO2 L3

$$V_z = \frac{V_o}{2} = \frac{9}{2} = 4.5V$$

The recommended current for best voltage stability current for zener diode is

$$I_z = 20mA$$

$$R_1 = \frac{V_o - V_z}{I_z} = \frac{9 - 4.5}{20mA} = 225\Omega \approx 220\Omega (\text{Standard Value})$$

For R_2, R_3 and R_4 $I_2 \gg I_{B(max)}$


$$I_2 = 100 \times I_{B(max)} = 100 \times 500nA = 50\mu A$$

$$R_3 + R_4 = \frac{V_z + 10\%}{I_2} = \frac{4.5 + 0.45}{50\mu A} = 99K\Omega$$

$$R_4 = 20\% \text{ of } (R_3 + R_4) = 20\% \text{ of } 99K\Omega = 19.8K\Omega \approx 20K\Omega (POT)$$

$$R_3 = 99K\Omega - 20K\Omega = 79K\Omega \approx 82K\Omega (\text{Standard Value})$$
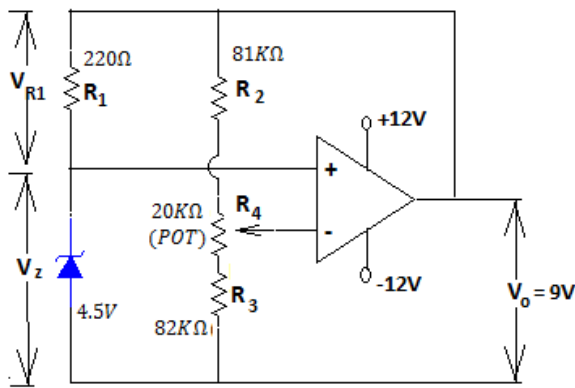
$$R_2 = \frac{V_o - (V_z + 10\%)}{I_2} = \frac{9 - (4.5 + 0.45)}{50\mu A} = 81K\Omega$$



Diagram(2 marks)+
Calculation (3 marks)

- (b) Explain the current amplifier circuit using operational amplifier and do necessary modification to the circuit to make it independent of load resistance.

[5] CO2 L4

Current Amplifier:


In this circuit R_2 has been added to the circuit. The current through R_2 is

$$I_2 = \frac{V_o}{R_2} = \frac{I_s R_1}{R_2}$$


Hence the output current is $\frac{R_1}{R_2}$ times of the input current and this circuit is a current amplifier if $R_1 > R_2$

But if $R_1 < R_2$ then, the circuit is a current attenuator.

Diagram(3 marks)+
Explanation (2
Marks)

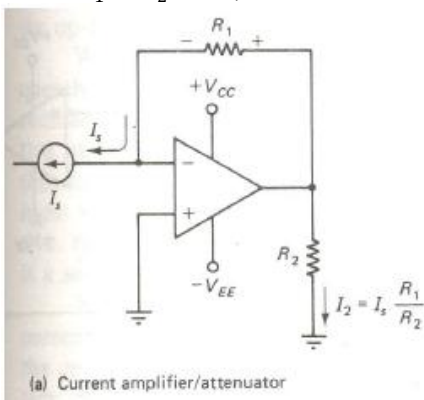

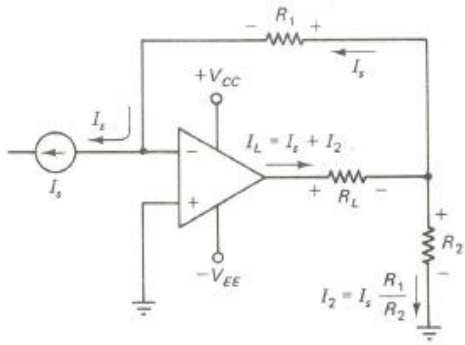The disadvantage of the circuit is that the current gain/attenuation is dependent on the resistance value of R_2 , which is the load resistance. If the load can be floating (ungrounded), then the circuit will become



(b) Current amplifier with gain independent of load

Here load current

$$I_L = I_S + I_2 = I_S + \frac{V_o}{R_2} = I_S + \frac{I_S R_1}{R_2} \Rightarrow I_L = I_S \left(1 + \frac{R_1}{R_2}\right)$$


Here the load current is independent of R_L . Hence the circuit operated as a current amplifier with a gain, which is independent of load resistance.


8 Draw the circuit of OPAMP Monostable Multivibrator and explain its operation. [10] CO3 L2

MONOSTABLE OPERATION:

Diagram (5 marks)+
Explanation (5 marks)

- Initially as the flip-flop output $Q = 0$ (LOW) and $\bar{Q} = 1$ (HIGH). This makes the output LOW and the external timing capacitor C is having zero potential because the transistor Q_1 is ON.
- When trigger is provided, the lower comparator produce the output as HIGH and at the same time the upper comparator produce the output as LOW, Hence the S-R flip-flop becomes SET. i.e. $Q = 1$ (HIGH) and $\bar{Q} = 0$ (LOW), this makes the output HIGH and the capacitor starts charging exponentially through R towards V_{CC} with a time constant RC .
- When the capacitor voltage is with in $V_C < \frac{2}{3}V_{CC}$

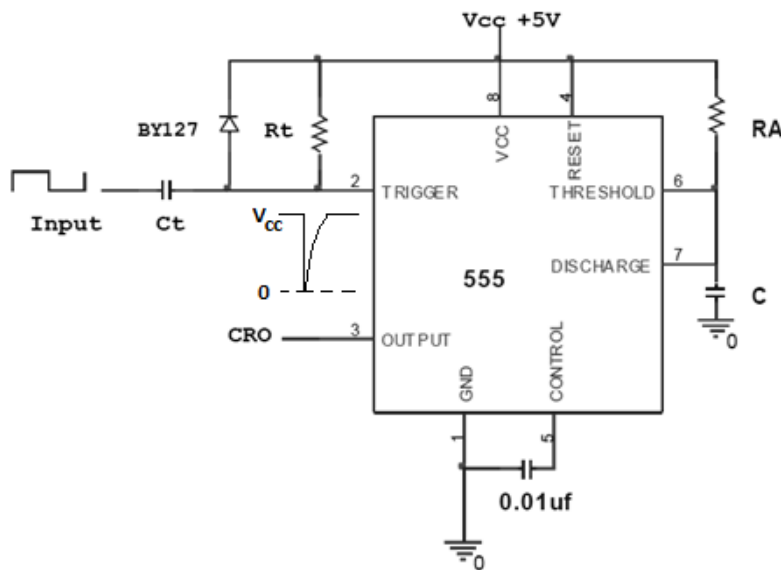

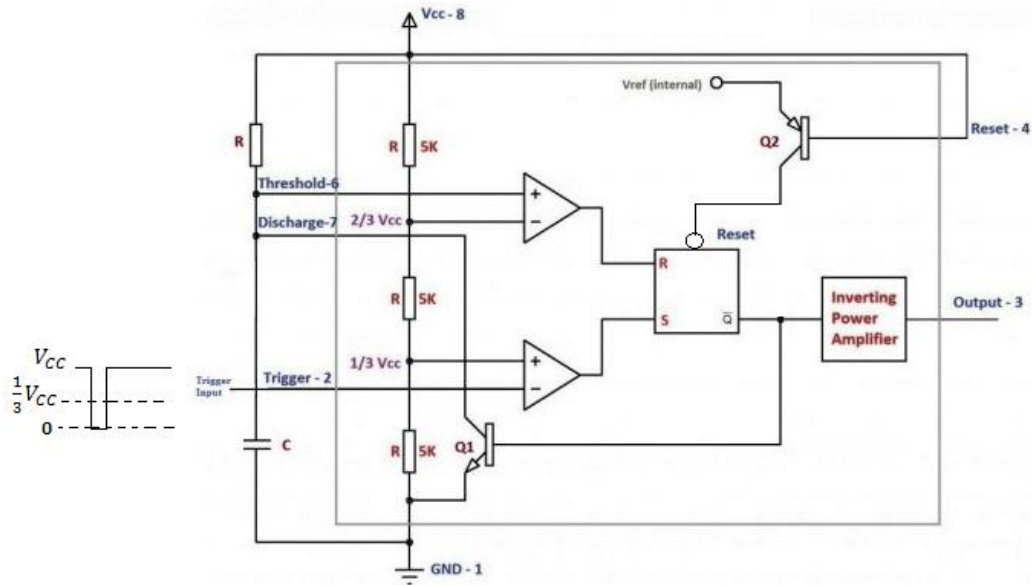

4. After the time period "T" the capacitor voltage is just greater than $\frac{2}{3}V_{CC}$. The lower comparator produces the output as LOW and the upper comparator produces the output as HIGH, hence the S-R flip-flop becomes RESET. i.e. $Q = 0$ (LOW) and $\bar{Q} = 1$ (HIGH), this makes the output LOW and the capacitor starts discharging the capacitor rapidly to ground potential. Capacitor voltage at any instant of time can be calculated as

$$V_C(t) = V_{CC} \left[1 - e^{-\frac{t}{RC}} \right]$$

$$\text{at } t = T_{ON}, V_C(t) = \frac{2}{3}V_{CC}$$

$$\frac{2}{3}V_{CC} = V_{CC} \left[1 - e^{-\frac{T_{ON}}{RC}} \right] \Rightarrow \frac{2}{3}V_{CC} = V_{CC} - V_{CC}e^{-\frac{T_{ON}}{RC}} \Rightarrow \frac{2}{3}V_{CC} - V_{CC} = -V_{CC}e^{-\frac{T_{ON}}{RC}}$$

$$\Rightarrow -\frac{1}{3}V_{CC} = -V_{CC}e^{-\frac{T_{ON}}{RC}} \Rightarrow \frac{1}{3} = e^{-\frac{T_{ON}}{RC}}$$

$$\Rightarrow \ln\left(\frac{1}{3}\right) = -\frac{T_{ON}}{RC} \Rightarrow -1.1 = -\frac{T_{ON}}{RC} \Rightarrow T_{ON} = 1.1RC$$

