


CMR INSTITUTE OF TECHNOLOGY		USN <input type="text"/>						 <small>CELEBRATING 25 YEARS</small> <small>CMR INSTITUTE OF TECHNOLOGY, BENGALURU</small> <small>ACCREDITED WITH A+ GRADE BY NAAC</small>	
Internal Assessment Test - II									
Sub:	MICROELECTRONICS CIRCUITS						Code:	15EC655	
Date:	22/ 05/2018	Duration:	90 mins	Max Marks:	50	Sem:	VI	Branch:	Professional Elective
Answer Any FIVE FULL Questions									

	Marks	OBE	
		CO	RBT
1. Consider a common-gate amplifier with active loads specified as follows: $W/L=7.2\mu\text{m}/0.36\mu\text{m}$, $\mu_n C_{ox}=387 \mu\text{A}/\text{V}^2$, $r_0=18 \text{ k}\Omega$, $I_D=100\mu\text{A}$, $g_m=1.25\text{mA}/\text{V}$, $\chi=0.2$, $R_S=10 \text{ k}\Omega$, $R_L=100 \text{ k}\Omega$, $C_{gs}=20\text{fF}$, $C_{gd}=5\text{fF}$ and $C_L=0$. Find A_{vo} , R_{in} , R_{out} , G_v , G_{is} , G_i and f_H . [10]		CO1	L1
2.(a) Explain the working of MOS differential pair with proper diagram. [05]		CO2	L1
(b) Derive the expression of differential gain of MOS differential pair. Also explain the effect of r_0 . [05]		CO2	L3
3. Explain CMOS implementation of CS amplifier with circuit diagram and voltage transfer characteristics. [10]		CO1	L1

CMR
INSTITUTE OF
TECHNOLOGY

USN



Internal Assessment Test - II

Sub:	MICROELECTRONICS CIRCUITS						Code:	15EC655	
Date:	22/ 05/2018	Duration:	90 mins	Max Marks:	50	Sem:	VI	Branch:	Professional Elective
Answer Any FIVE FULL Questions									

	Marks	OBE	
		CO	RBT
1. Consider a common-gate amplifier with active loads specified as follows: $W/L=7.2\mu\text{m}/0.36\mu\text{m}$, $\mu_n C_{ox}=387 \mu\text{A}/\text{V}^2$, $r_0=18 \text{ k}\Omega$, $I_D=100\mu\text{A}$, $g_m=1.25\text{mA}/\text{V}$, $\chi=0.2$, $R_S=10 \text{ k}\Omega$, $R_L=100 \text{ k}\Omega$, $C_{gs}=20\text{fF}$, $C_{gd}=5\text{fF}$ and $C_L=0$. Find A_{vo} , R_{in} , R_{out} , G_v , G_{is} , G_i and f_H . [10]		CO1	L1
2.(a) Explain the working of MOS differential pair with proper diagram. [05]		CO2	L1
(b) Derive the expression of differential gain of MOS differential pair. Also explain the effect of r_0 . [05]		CO2	L3
3. Explain CMOS implementation of CS amplifier with circuit diagram and voltage transfer characteristics. [10]		CO1	L1

4.	Explain the working of MOS differential pair with common-mode input and differential input.	[10]	CO1	L2
5.	For a MOS differential pair with common-mode voltage V_{cm} applied, when $V_{DD}=V_{SS}=1.5v$, $kn'(W/L)=4mA/V^2$, $V_t=0.5V$, $I=0.4mA$, $R_D=2.5K\Omega$, $\lambda=0$ calculate the following: a) V_{OV} , V_{GS} for each transistors b) V_S , I_{D1} , I_{D2} , V_{D1} , V_{D2} when $V_{CM}=0$ c) highest value of V_{CM} for which Q_1 & Q_2 remains in saturation.	[10]	CO1	L3
6.a)	A MOS differential pair is operated at a total bias current of $I=0.8mA$ using transistor with $W/L=100$, $\mu_n C_{OX}=0.2mA/V^2$, $V_A = 20V$. Calculate V_{OV} , gm , ro , A_d .	[05]	CO2	L2
b)	Derive the expression of R_{in} , R_{out} and A_{VO} of MOS Cascode amplifier with suitable diagram.	[05]	CO1	L1

4.	Explain the working of MOS differential pair with common-mode input and differential input.	[10]	CO1	L2
5.	For a MOS differential pair with common-mode voltage V_{cm} applied, when $V_{DD}=V_{SS}=1.5v$, $kn'(W/L)=4mA/V^2$, $V_t=0.5V$, $I=0.4mA$, $R_D=2.5K\Omega$, $\lambda=0$ calculate the following: a) V_{OV} , V_{GS} for each transistors b) V_S , I_{D1} , I_{D2} , V_{D1} , V_{D2} when $V_{CM}=0$ c) highest value of V_{CM} for which Q_1 & Q_2 remains in saturation.	[10]	CO1	L3
6a).	A MOS differential pair is operated at a total bias current of $I=0.8mA$ using transistor with $W/L=100$, $\mu_n C_{OX}=0.2mA/V^2$, $V_A = 20V$. Calculate V_{OV} , gm , ro , A_d .	[05]	CO2	L2
b).	Derive the expression of R_{in} , R_{out} and A_{VO} of MOS Cascode amplifier with suitable diagram.	[05]	CO1	L1

