

Q1. Derive an expression for drain current of a MOSFET in triode and saturation region.

Ans 1:

**DERIVATION OF  $I_D - V_{DS}$  RELATIONSHIP :-**

Let  $V_{GS} > V_t$  is applied b/w G & S to induce channel  
 also let  $V_{DS}$  is applied b/w D & S.  
 Considering operation is triode region for which channel is continuous  
 $V_{GS} > V_{GS,D}$  must be greater than  $V_t$  or  $V_{DS} < V_{GS} - V_t$  where channel will have tapered shape shown in diagram.  
 In MOSFET, G & channel forms a II plate capacitor with oxide layer as dielectric  
 If  $C_{ox}$  = capacitance / unit area  
 $t_{ox}$  = oxide layer thickness  
 $\therefore C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$ , where  $\epsilon_{ox}$  = permittivity of  $SiO_2$   
 $= 3.9 \epsilon_0 = 3.9 \times 8.854 \times 10^{-12}$   
 $= 3.45 \times 10^{-11} \text{ F/cm}$   
 for  $t_{ox} = 100 \text{ nm}$ ,  
 $C_{ox} = 3.45 \times 10^{-3} \text{ F/m}^2$  or  $3.45 \text{ fF}/\mu\text{m}^2$   
 Considering the infinitesimal strip of the gate at distance  $x$  from the S. Capacitance of this strip is  $C_{ox} w dx$ . To find the charge stored on this infinitesimal strip of the gate capacitance, the capacitance is multiplied by the effective V b/w G & channel at point  $x$ .  
 Effective V is the V that is responsible for inducing the channel at point  $x$ . It is thus  $(V_{GS} - V(x) - V_t)$ , where  $V(x)$  is the voltage in the channel at point  $x$ . The  $\bar{e}$  charge  $dq$  in the infinitesimal portion of the channel at point  $x$  is  $dq = -C_{ox} (w dx) [V_{GS} - V(x) - V_t]$  (3)  $C = \frac{dq}{dV}$

-ve sign indicates  $dq$  is -ve charge. The  $V_{DS}$  produces an EF along the channel in the -ve  $x$  direction. At point  $x$  this field can be expressed as

$$E(x) = -\frac{dV(x)}{dx} \quad \text{--- (4)}$$

EF  $E(x)$  causes the  $\bar{e}$  charge  $dq$  to drift toward the drain with a velocity  $dx/dt$ .

$$\therefore \frac{dx}{dt} = -\mu_n E(x) = \mu_n \frac{dV(x)}{dx} \quad \text{--- (5)}$$

where  $\mu_n = \bar{e}$  mobility in the channel (called surface mobility, whose value depends on fabrication process technology).

The resulting drift  $I(i)$  can be obtained as

$$i = dq = dq \times dx$$

substituting for charge/unit length  $(dq/dx)$  from equa. (3) & for  $\bar{e}$  drift velocity  $(dx/dt)$  from equa. (5)

$$i = -Cox W \cdot [V_{GS} - V(x) - V_T] \times \mu_n \frac{dV(x)}{dx}$$

$$\Rightarrow i = -\mu_n Cox W [V_{GS} - V(x) - V_T] \frac{dV(x)}{dx}$$

Although evaluated at a particular point  $x$ ,  $i$  is constant at all points along the channel.

$i = i_D$  in magnitude

$$i_D = -i = \mu_n Cox W [V_{GS} - V(x) - V_T] \frac{dV(x)}{dx} \quad \text{--- (6)}$$

Integrating equa. (6) on both sides from  $x=0$  to  $x=L$  &  $V(0)=0$  to  $V(L)=V_{DS}$ .

$$\int_0^L i_D dx = \int_0^{V_{DS}} \mu_n Cox W [V_{GS} - V(x) - V_T] dV(x)$$

$$\Rightarrow i_D = \mu_n Cox W \left( [V_{GS} - V_T] V_{DS} - \frac{1}{2} V_{DS}^2 \right) \quad \text{--- (7)}$$

Equa. (7) is the expression for triode region of the  $i_D - V_{DS}$  characteristic.

Equa. of  $I$  at the beginning of saturation region is found by substituting  $V_{DS} = V_{GS} - V_t$ .

$$\therefore i_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 \quad \text{--- (8)}$$

Equa. (8) is the expression for  $i_D - V_{DS}$  characteristic in saturation region; it gives the saturation value of  $i_D$  corresponding to the given  $V_{GS}$ . Saturation current  $i_D$  remains constant for a given  $V_{GS}$  as  $V_{DS}$  is varied.

$\mu_n C_{ox}$  = constant determined by the process technology. = known as process transconductance parameter  $\rightarrow k_n' \text{ (A/V}^2\text{)}$

$$\therefore k_n' = \mu_n C_{ox} \quad \text{--- (9)}$$

$$\therefore \text{For Triode region } i_D = k_n' \left(\frac{W}{L}\right) \left[ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$\text{For saturation region } i_D = \frac{k_n' \left(\frac{W}{L}\right)}{2} (V_{GS} - V_t)^2$$

Q2a. Derive an expression for drain to source current  $i_{DS}$  and finite output resistance  $r_o$  in saturation, if channel length modulation is considered.

Ans 2a.

→ But practically when  $V_{DS} > V_{DSsat}$ , channel will be affected. As  $V_{DS}$  is increased, the channel pinch-off point is moved slightly away from the D towards S. Voltage across the channel remains constant at  $V_{DS} - V_{DSsat} = V_{DS} - V_{GS} - V_{th}$  & the additional  $V$  applied to the D appears as a  $V$  drop across the narrow depletion region b/w the end of the channel & D region. This  $v$  accelerates the  $e^-$  that reach the D end of the channel & sweeps them across the depletion region into D. when depletion region widens, the channel length is in effect reduced, from  $L$  to  $L - \Delta L$ , a phenomenon called as CHANNEL-LENGTH MODULATION.

Now since  $i_D$  is inversely  $\propto$  to channel length,  $i_D \propto V_{DS}$  from eqn. (10),  $i_D = \frac{k_n \mu_n}{L} V_{DS}^2$ ,  $i_D$  increases as  $V_{DS}$  increases in saturation region.

$V_{DS}$  increases To account for the dependence of  $i_D$  on  $V_{DS}$  in saturation,  $L$  is replaced by  $L - \Delta L$  in eqn. (13)

$$i_D = \frac{k_n \mu_n}{2} \left( \frac{W}{L - \Delta L} \right) (V_{GS} - V_{th})^2$$

$$\Rightarrow i_D = \frac{k_n \mu_n}{2} \left( \frac{W}{L} \right) \frac{1}{\left( 1 - \frac{\Delta L}{L} \right)} (V_{GS} - V_{th})^2$$

} multiply both Numerator & Denominator by  $L + \Delta L$

$$\Rightarrow i_D = \frac{k_n \mu_n}{2} \left( \frac{W}{L} \right) \left( 1 + \frac{\Delta L}{L} \right) (V_{GS} - V_{th})^2 \quad \text{--- (1)}$$

assuming  $\left( \frac{\Delta L}{L} \right) \ll 1$  & assuming  $\Delta L \propto V_{DS}$ .


$$\Rightarrow \Delta L = \lambda' V_{DS} \quad \text{where } \lambda' = \text{process technology parameter} = \text{dimension (cm/V)}$$

$$\therefore i_D = \frac{k_n \mu_n}{2} \left( \frac{W}{L} \right) \left( 1 + \frac{\lambda' V_{DS}}{L} \right) (V_{GS} - V_{th})^2 \quad \text{--- (2)}$$

$$\left[ \frac{\lambda'}{L} = \lambda \right] \therefore i_D = \frac{k_n \mu_n}{2} \left( \frac{W}{L} \right) (1 + \lambda V_{DS}) (V_{GS} - V_{th})^2 \quad \text{--- (3)}$$

where  $\lambda = \lambda' / L$  = process technology parameter ( $V^{-1}$ )

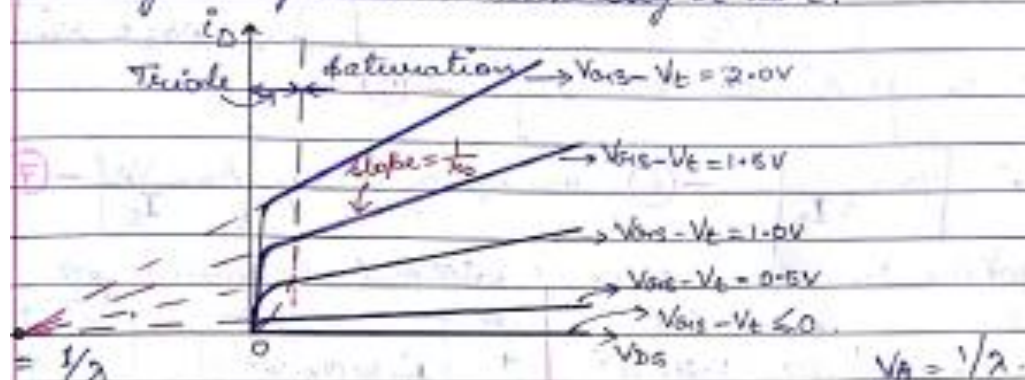For a given process  $\lambda$  inversely  $\propto$  to  $L$ .



Effect of  $V_{DS}$  on  $i_D$  in the saturation region, MOSFET parameter  $V_A$  depends on the process technology  $\lambda$  for a given process is  $\propto$  to channel length.

Equa. (3) shows the linear dependence of  $i_D$  on  $V_{DS}$  in saturation region, when the straight-line  $i_D - V_{DS}$  characteristics are extrapolated they intercept the  $V_{DS}$  axis at the point  $V_{DS} = -V_A$ , where  $V_A = +ve$  voltage. Equa. (3) indicates that  $i_D = 0$  at  $V_{DS} = -1/\lambda$ ,  $\therefore V_A = -V_{DS} = 1/\lambda$ .

$\therefore V_A$  = process technology parameter with dimension (V)  
For a given process  $V_A \propto$  channel length ( $L$ ).

$\therefore V_A \propto L \Rightarrow V_A = V_A' L$ .

where  $V_A'$  = process technology parameter with dimension ( $V/\mu m$ ) = typical value = (6-50)  $V/\mu m$ .

$\propto$  also called Early Voltage.

Equa. (3) indicates that when channel-length modulation is considered, the saturation values of  $i_D$  depends on  $V_{DS}$ . Thus for a given  $V_{GS}$ , a change  $\Delta V_{DS}$  yields a corresponding change  $\Delta i_D$  in  $i_D$  so the o/p resistance of circuit containing representing  $i_D$  in saturation is no longer infinite.

$$\therefore r_o = \left[ \frac{i_D}{V_{DS}} \right]^{-1} \quad \text{--- (4)} \quad \left. \begin{array}{l} V_{GS} = \text{constant} \\ r_o = \frac{V_{DS}}{i_D} \end{array} \right\}$$

$$r_{o0} = \frac{k_n' (\frac{W}{L})}{2} \frac{V_{DS}}{(V_{GS} - V_t)^2 (1 + \lambda V_{DS})} = \frac{k_n' (\frac{W}{L})}{2} \frac{V_{DS}}{(V_{GS} - V_t)^2} \cdot \frac{1}{1 + \lambda V_{DS}}$$

$$= \left[ \lambda \frac{k_n' (\frac{W}{L})}{2} (V_{GS} - V_t)^2 \right]^{-1}$$

∴ using eqn. (3) & (4),  $A_{v0} = \left[ \frac{k_n' \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})}{2} \right]^{-1}$

$$\Rightarrow A_{v0} = \left[ \frac{k_n' \frac{W}{L} (V_{GS} - V_t)^2 \lambda (r_{o0}^{-1})}{2} \right]^{-1}$$

∴  $A_{v0} = \left[ \lambda \frac{k_n' \frac{W}{L} (V_{GS} - V_t)^2}{2} \right]^{-1}$  — (5)

∴  $A_{v0} = \frac{1}{\lambda I_D}$  — (6) or equivalently  $A_{v0} = \frac{V_A}{I_D}$  — (7)

where  $I_D$  = drain current without channel-length modulation


$$I_D = \frac{k_n' \frac{W}{L}}{2} (V_{GS} - V_t)^2$$

∴  $A_{v0} \propto \frac{1}{I_D}$



Large-signal equivalent circuit model of NMOS in saturation with  $r_{o0}$  showing linear dependency of  $I_D$  on  $V_{DS}$ .

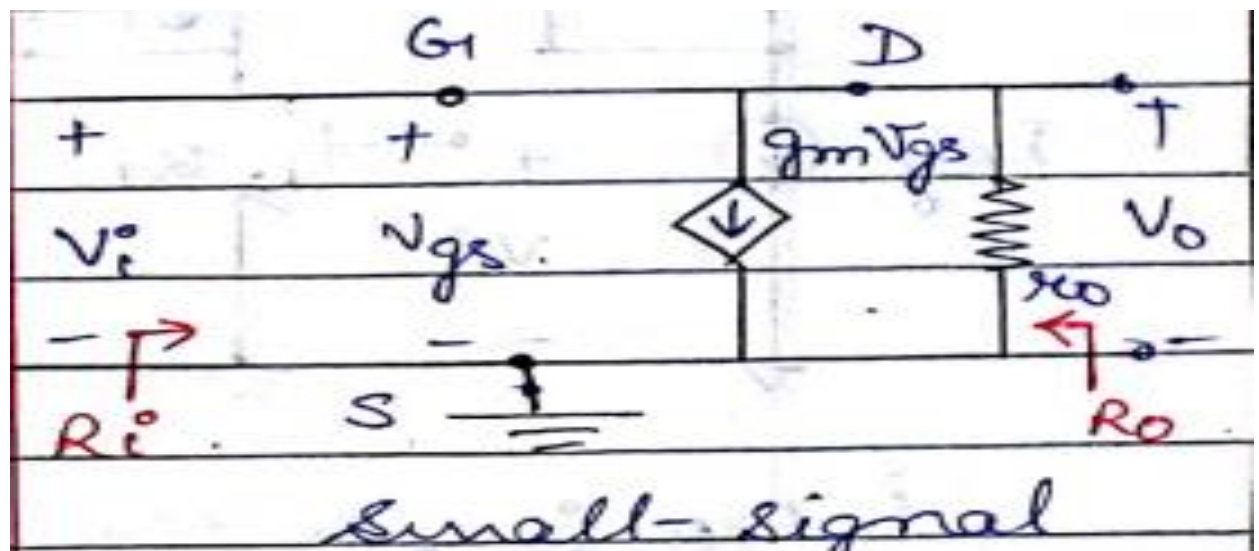
2b. Draw the small signal equivalent model of NMOS by considering  $r_o$  and explain.



3a. What is body effect and how it affects threshold voltage?

Ans 3a.

**THE BODY EFFECT - ROLE OF SUBSTRATE**

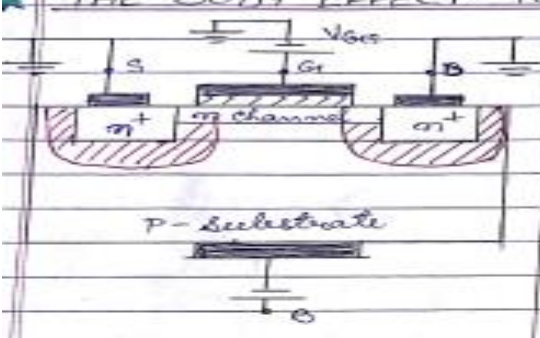

For many applications the S terminal is connected to substrate (Body terminal), which results in the p-n junction b/w the substrate & the induced channel having a constant zero bias. In such case the substrate does not play any role in ckt operation & its existence can be ignored.

In IC, the substrate is usually common to many MOS Ts. To maintain the cutoff condition for all the substrate-to-channel junction, the substrate is usually connected to the most -ve power supply in an NMOS ckt. The resulting RB voltage b/w S & body will have an effect on device operation. Consider an nMOS T, whose substrate is made -ve relative to S, which will widen the depletion region & reduce the channel depth, so to return the channel to its former state  $V_{GS}$  is increased. If reverse substrate bias  $V_{BS}$  is increased, then threshold  $V (V_t)$  also increases according to the relationship:

$$V_t = V_{t0} + \gamma \left[ \sqrt{2\phi_f + V_{BS}} - \sqrt{2\phi_f} \right] \quad \text{--- (1)}$$

where  $V_{t0}$  = threshold voltage for  $V_{BS} = 0$ .

$\phi_f$  = physical parameter;  $2\phi_f = 0.6V$  typically

$\gamma$  = fabrication-process parameter.

$$\gamma = \frac{\sqrt{2qNAE_s}}{C_{ox}} \quad \text{--- (2)} = \text{body-effect parameter.}$$

where  $q = e$  charge =  $1.6 \times 10^{-19} C$ .

$NA$  = doping concentration of p-type substrate

$E_s =$  permittivity of Si =  $11.7\epsilon_0 = 11.7 \times 8.854 \times 10^{-12} \times 1.06 \times 10^{-12} \text{ F/cm}$

$\gamma =$  dimension  $\sqrt{V}$  = typically  $0.4 V^{1/2}$ .

equa (1) is applicable for a p-channel device as well by taking  $|V_{BS}|$  &  $\gamma = -ve$ .

&  $\gamma = \frac{\sqrt{2qND_e s}}{C_{ox}}$ ;  $ND =$  doping conc. of n-type substrate

$2\phi_f = 0.75V$  &  $\gamma = -0.5V^{1/2}$   
 equa. (1) indicates; incremental change in  $V_{GS}$  gives rise to an incremental change in  $V_t$ , which in turn results in an incremental change in  $i_D$ , even though  $V_{GS}$  might have been kept constant. The body voltage controls  $i_D$  thus the body acts as another gate for the MOSFET, this phenomenon is known as body effect. The body-effect can cause considerable degradation in ckt performance

Q4. Design the circuit with  $R_D$  and  $R_S$  where n-MOS transistor operates at  $V_{DD}=+2.5V$ ,  $V_{SS}=-2.5V$ ,  $I_D=0.4mA$  and  $V_D=+0.5V$ . The transistor has  $V_t=0.7V$ ,  $\mu_n C_{ox}=100\mu A/V^2$ ,  $L=1\mu m$ ,  $W=32\mu m$  and gate is at ground. Neglect the channel length modulation effect.

Ans

$\therefore V_D = +0.5V > V_{GS}$ , means nMOS  $T_0$  is operating in saturation region. So, saturation-region expression of  $i_D$  is used to determine value of  $V_{GS}$ .  

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$\therefore I_D = 0.4mA = 400\mu A$ ,  $\mu_n C_{ox} = 100\mu A/V^2$ ,  
 $\frac{W}{L} = \frac{32\mu m}{1\mu m} = 32$ ,  $\therefore V_{GS} - V_t = V_{OV}$

$\therefore 400 \times 10^{-6} = \frac{100 \times 10^{-6}}{2} \times 32 \times V_{OV}^2$

$\Rightarrow V_{OV}^2 = \frac{4}{32} \Rightarrow V_{OV} = \frac{1}{2} = 0.5V$

$\therefore V_{GS} - V_t = V_{OV} \Rightarrow V_{GS} = V_{OV} + V_t = 0.5 + 0.7 \Rightarrow V_{GS} = 1.2V$

Figure shows  $G_t$  is at ground potential,  $\therefore S$  must be at  $-1.2V$ . & the required value of  $R_S$  is determined as  

$$R_S = \frac{V_S - V_{SS}}{I_D} = \frac{-1.2 - (-2.5)}{0.4 \times 10^{-3}} = 3.25k\Omega$$


To design the ckt, to establish a dc voltage of  $+0.5V$  at



the D, we must select  $R_D$  as follows:  
 $R_D = \frac{V_{DD} - V_D}{I_D} = \frac{2.5 - 0.5}{0.4} = 5\text{ k}\Omega$

5a. Draw the development of the T-equivalent circuit model for the MOSFET.

Ans.

 

5b. Briefly explain two types of biasing methods in MOS amplifier circuits

Ans

#### 4.5.1 Biasing by Fixing $V_{GS}$

The most straightforward approach to biasing a MOSFET is to fix its gate-to-source voltage  $V_{GS}$  to the value required to provide the desired  $I_D$ . This voltage value can be derived from the power supply voltage  $V_{DD}$  through the use of an appropriate voltage divider. Alternatively, it can be derived from another suitable reference voltage that might be available in the system. Independent of how the voltage  $V_{GS}$  may be generated, this is not a good approach to biasing a MOSFET. To understand the reason for this statement, recall that

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

and note that the values of the threshold voltage  $V_t$ , the oxide-capacitance  $C_{ox}$ , and (to a lesser extent) the transistor aspect ratio  $W/L$  vary widely among devices of supposedly the same size and type. This is certainly the case for discrete devices, in which large spreads in the values of these parameters occur among devices of the same manufacturer's part number. The spread is also large in integrated circuits, especially among devices fabricated on different wafers and certainly between different batches of wafers. Furthermore, both  $V_t$  and  $\mu_n$  depend on temperature, with the result that if we fix the value of  $V_{GS}$ , the drain current  $I_D$  becomes very much temperature dependent.

#### 4.5.2 Biasing by Fixing $V_G$ and Connecting a Resistance in the Source

An excellent biasing technique for discrete MOSFET circuits consists of fixing the dc voltage at the gate,  $V_G$ , and connecting a resistance in the source lead, as shown in Fig. 4.30(a). For this circuit we can write

$$V_G = V_{GS} + R_S I_D \quad (4.46)$$

Now, if  $V_G$  is much greater than  $V_{GS}$ ,  $I_D$  will be mostly determined by the values of  $V_G$  and  $R_S$ . However, even if  $V_G$  is not much larger than  $V_{GS}$ , resistor  $R_S$  provides *negative feedback*, which acts to stabilize the value of the bias current  $I_D$ . To see how this comes about consider the case when  $I_D$  increases for whatever reason. Equation (4.46) indicates that since  $V_G$  is constant,  $V_{GS}$  will have to decrease. This in turn results in a decrease in  $I_D$ , a change that is opposite to that initially assumed. Thus the action of  $R_S$  works to keep  $I_D$  as constant as possible. This negative feedback action of  $R_S$  gives it the name **degeneration resistance**, a name that we will appreciate much better at a later point in this text.

Figure 4.30(b) provides a graphical illustration of the effectiveness of this biasing scheme. Here we show the  $i_D$ - $v_{GS}$  characteristics for two devices that represent the extremes of a batch of MOSFETs. Superimposed on the device characteristics is a straight line that represents the constraint imposed by the bias circuit—namely, Eq. (4.46). The intersection of this straight line with the  $i_D$ - $v_{GS}$  characteristic curve provides the coordinates ( $I_D$  and  $V_{GS}$ ) of the bias point. Observe that compared to the case of fixed  $V_{GS}$ , here the variability obtained in  $I_D$  is much smaller. Also, note that the variability decreases as  $V_G$  and  $R_S$  are made larger (providing a bias line that is less steep).

6. Derive the expression for transconductance  $g_m$  and voltage gain  $A_v$  for a common source amplifier with small input signal.

Ans.

Next, consider the situation with the input signal  $v_{gs}$  applied. The total instantaneous gate-to-source voltage will be

$$v_{GS} = V_{GS} + v_{gs} \quad (4.56)$$

resulting in a total instantaneous drain current  $i_D$

$$\begin{aligned} i_D &= \frac{1}{2} k_n' \frac{W}{L} (V_{GS} + v_{gs} - V_t)^2 \\ &= \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 + k_n' \frac{W}{L} (V_{GS} - V_t) v_{gs} + \frac{1}{2} k_n' \frac{W}{L} v_{gs}^2 \end{aligned} \quad (4.57)$$

The first term on the right-hand side of Eq. (4.57) can be recognized as the dc bias current  $I_D$  (Eq. 4.54). The second term represents a current component that is directly proportional to the input signal  $v_{gs}$ . The third term is a current component that is proportional to the square of the input signal. This last component is undesirable because it represents *nonlinear distortion*. To reduce the nonlinear distortion introduced by the MOSFET, the input signal should be kept small so that

$$\frac{1}{2} k_n' \frac{W}{L} v_{gs}^2 \ll k_n' \frac{W}{L} (V_{GS} - V_t) v_{gs}$$

resulting in

$$v_{gs} \ll 2(V_{GS} - V_t) \quad (4.58)$$

or, equivalently,

$$v_{gs} \ll 2V_{OV} \quad (4.59)$$

where  $V_{OV}$  is the overdrive voltage at which the transistor is operating.

If this **small-signal condition** is satisfied, we may neglect the last term in Eq. (4.57) and express  $i_D$  as

$$i_D = I_D + i_d \quad (4.60)$$

where

$$i_d = k_n' \frac{W}{L} (V_{GS} - V_t) v_{gs}$$

The parameter that relates  $i_d$  and  $v_{gs}$  is the MOSFET **transconductance**  $g_m$ .

$$g_m = \frac{i_d}{v_{gs}} = k_n' \frac{W}{L} (V_{GS} - V_t) \quad (4.61)$$

or in terms of the overdrive voltage  $V_{OV}$ ,

$$g_m = k_n' \frac{W}{L} V_{OV} \quad (4.62)$$

Figure 4.35 presents a graphical interpretation of the small-signal operation of the enhancement MOSFET amplifier. Note that  $g_m$  is equal to the slope of the  $i_D$ - $v_{GS}$  characteristic at the bias point,

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS} = V_{GS}} \quad (4.63)$$

This is the formal definition of  $g_m$ , which can be shown to yield the expressions given in Eqs. (4.61) and (4.62).

### 4.6.3 The Voltage Gain

Returning to the circuit of Fig. 4.34, we can express the total instantaneous drain voltage  $v_D$  as follows:

$$v_D = V_{DD} - R_D i_D$$

Under the small-signal condition, we have

$$v_D = V_{DD} - R_D(I_D + i_d)$$

which can be rewritten as

$$v_D = V_D - R_D i_d$$

Thus the signal component of the drain voltage is

$$v_d = -i_d R_D = -g_m v_{gs} R_D \quad (4.64)$$

which indicates that the voltage gain is given by

$$A_v = \frac{v_d}{v_{gs}} = -g_m R_D \quad (4.65)$$

7a. Explain the operation of MOSFET as a switch

Ans

★ MOSFET AS A SWITCH :-


When MOSFET is used as a switch it operates at the extreme points of the transfer characteristics; device

- 1) Device = OFF, when  $V_i < V_t$ , operation within XA with  $V_o = V_{DD}$ .
- 2) Device = ON, when  $V_i \approx V_{DD}$ , operation close to point C  $V_o = V_{oc}$  with very small  $V_o$  (at C  $V_o = V_{oc}$ ).

∴ Common-source MOS ckt behaves as a inverter ckt. low V level  $\approx 0$  & high V level  $\approx V_{DD}$ .

7b. Design the circuit with  $R_D$  and  $R_S$  where n-MOS transistor operates at  $V_{DD}=+2.5V$ ,  $V_{SS}=-2.5V$ ,  $I_D=0.3mA$  and  $V_D=+0.4V$ . The transistor has  $V_t=1V$ ,  $\mu_n C_{ox}=60\mu A/V^2$ ,  $W/L=120\mu m/3\mu m$  and gate is at ground. Neglect the channel length modulation effect.

Ans.



$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$\Rightarrow 0.3 \times 10^{-3} = \frac{60 \times 10^{-6} \times 120 \times 10^{-6}}{2} (V_{GS} - 1)^2$$

$$\Rightarrow 300 \times 10^{-6} = \frac{60 \times 10^{-6} \times 120}{2} V_{OV}^2$$

$$\Rightarrow 300 = 60 \times 40 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = \sqrt{\frac{300}{60 \times 40}} = \sqrt{\frac{1}{8}}$$

$$\Rightarrow V_{OV} = 0.3535$$

$$\Rightarrow V_{GS} - V_t = V_{OV} \Rightarrow V_{GS} = V_{OV} + V_t = 0.3535 + 1 = 1.3535V$$

∵  $G_1$  is at ground potential, ∴  $S$  must be at  $-1.3535V$ .

$$R_S = \frac{V_S - V_{SS}}{I_D} = \frac{-1.3535 - (-2.5)}{0.3 \times 10^{-3}} = \frac{-1.3535 + 2.5}{0.3 \times 10^{-3}}$$

$$\Rightarrow R_S = \frac{1.1465}{0.3 \times 10^{-3}} = 3.821 K\Omega$$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{2.5 - 0.4}{0.3 \times 10^{-3}} = 7 K\Omega$$