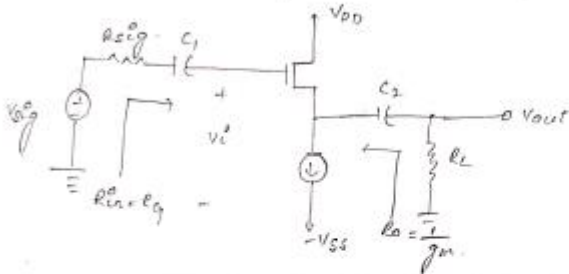



1. Determine the  $G_v$ ,  $A_v$ ,  $R_{out}$ ,  $R_{in}$ , and  $A_{v0}$  for a common Drain Amplifier.

In common drain amplifier circuit, the ~~gate~~ drain is provided signal ground and it acts as a common terminal b/w input and output ports. The input is provided ~~with~~ supplied to the gate terminal with a capacitor  $C_1$  coupled to it. The output is drawn from the source and a capacitor  $C_2$  is present.



As the drain is directly connected to ground signal, resistance  $R_D$  can be removed.

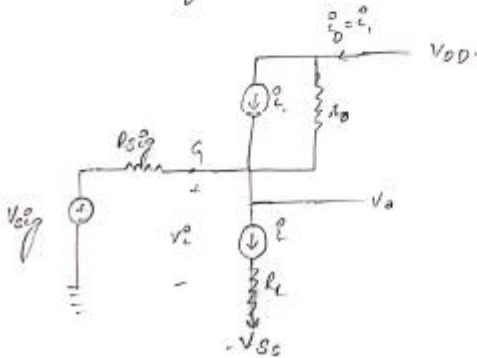The small signal equivalent circuit of the above circuit is as follows.



Looking at the small signal equivalent circuit, we can say that

$$R_{in} = R_G$$

$$v_o = \frac{v_{sig} R_{in}}{R_{in} + R_{sig}}$$

$$v_i = \frac{v_{sig} R_G}{R_G + R_{sig}}$$

The value of  $R_{sig} \gg R_{in}$ .

The output voltage

$$v_o = \frac{v_{in} (R_{L} \parallel R_L)}{(R_{L} \parallel R_L) + \frac{1}{g_m}}$$

From the above equation voltage gain  $A_v$  can be obtained

$$A_v = \frac{(r_o \parallel R_L)}{(r_o \parallel R_L) + \frac{1}{g_m}}$$

The overall voltage gain, denoted by  $A_{v_o}$  is given by

$$A_{v_o} = \frac{r_o}{r_o + \frac{1}{g_m}}$$

The total voltage gain  $G_v$  is given by

$$G_v = \frac{R_{in}}{R_{in} + R_{sig}} A_v$$

$$G_v = \frac{R_G}{R_G + R_{sig}} \left( \frac{r_o \parallel R_L}{(r_o \parallel R_L) + \frac{1}{g_m}} \right)$$

The output resistance  $r_o$  is given by

$$r_o = \frac{1}{g_m} \text{ without } r_o$$

$$R_o = \frac{1}{g_m} \parallel r_o \text{ with } r_o$$

2. For the CG Amplifier  $g_m = 1 \text{ mA/V}$  &  $R_D = 15 \text{ k}\Omega$ . Find  $R_{in}$ ,  $R_{out}$ ,  $A_v$ ,  $A_{v_o}$  and  $G_v$ , for  $R_L = 15 \text{ k}\Omega$  and  $R_{sig} = 50 \Omega$ . Calculate the overall voltage gain become for  $R_{sig} = 1 \text{ k}\Omega$ ?  $10 \text{ k}\Omega$ ?  $100 \text{ k}\Omega$ ?

$$\begin{aligned} R_{in} &= \frac{1}{g_m} \\ &= \frac{1}{10^{-3}} \\ &= 1 \text{ k}\Omega \end{aligned}$$

$$R_{in} = 1 \text{ k}\Omega$$

$$\begin{aligned} R_{out} &= (R_D \parallel R_D) \\ &= (15 \text{ k}\Omega \parallel 15 \text{ k}\Omega) \end{aligned}$$

$$R_{out} = 7.5 \text{ k}\Omega$$

$$A_v = g_m (R_D \parallel R_L)$$
$$A_v = 10^{-3} (7.5 \times 10^3)$$

$$A_v = +7.5 \text{ V/V}$$

$$A_{v_o} = g_m R_D$$
$$= 10^{-3} (15 \times 10^3)$$

$$A_{v_o} = +15 \text{ V/V}$$

$$G_v = \frac{A_v}{(1 + g_m R_{sig})}$$

ii when  $R_{sig} = 50 \Omega$

$$G_v = \frac{7.5}{(1 + (10^{-3} \times 50))}$$

$$G_v = +7.14 \text{ V/V}$$

iii when  $R_{sig} = 1 \text{ k}\Omega$

$$G_v = \frac{7.5}{1 + (10^{-3} \times 10^3)}$$

$$G_v = \frac{7.5}{(1+1)} = \frac{7.5}{2}$$

$$G_v = +3.75 \text{ V/V}$$

iv when  $R_{sig} = 10 \text{ k}\Omega$

$$G_v = \frac{7.5}{1 + (10^{-3} \times 10 \times 10^3)}$$

$$G_v = \frac{7.5}{(1+10)}$$

$$G_v = \frac{7.5}{11}$$

$$G_v = +0.68 \text{ V/V}$$

v when  $R_{sig} = 100 \text{ k}\Omega$

$$G_v = \frac{7.5}{1 + (10^{-3} \times 100 \times 10^3)}$$

$$G_v = \frac{7.5}{101}$$

$$G_v = +0.074 \text{ V/V}$$

3. Consider a source follower having  $g_m = 1 \text{ mA/V}$ ,  $r_o = 150 \text{ k}\Omega$ ,  $R_{sig} = 1 \text{ M}\Omega$ , and  $R_i = 15 \text{ k}\Omega$  calculate  $R_{in}$ ,  $R_{out}$  (with and without  $r_o$ ),  $A_{v0}$ ,  $A_v$  and overall small signal voltage gain  $G_v$ .

$$g_m = 1 \text{ mA/V}; r_o = 150 \text{ k}\Omega; R_{sig} = 1 \text{ M}\Omega; R_L = 15 \text{ k}\Omega.$$

$$R_{in} = R_g = 4.7 \text{ M}\Omega.$$

$$A_{v0} \text{ (without } r_o) = \frac{r_o}{r_o + 1/g_m} = \frac{150 \times 10^3}{150 \times 10^3 + 10^{-3}} = 0.993 \text{ V/V}$$

$$A_{v0} \text{ (without } r_o) = 1 \text{ V/V. as } r_o \gg 1/g_m.$$

$$A_v \text{ (with } r_o) = \frac{r_o \parallel R_L}{(r_o \parallel R_L) + 1/g_m} = \frac{(150 \times 10^3) \parallel (15 \times 10^3)}{(150 \times 10^3) \parallel (15 \times 10^3) + 10^{-3}}$$

$$= 0.9316 \text{ V/V.}$$

$A_v$  (without  $r_o$ )

$$A_v = \frac{R_L}{R_L + 1/g_m} = \frac{15 \times 10^3}{15 \times 10^3 + 10^{-3}}$$

$$= 0.9375 \text{ V/V.}$$

$R_{out}$  without  $r_o$ :-

$$R_{out} = 1/g_m = 1 \text{ k}\Omega.$$

$R_{out}$  with  $r_o$ :-

$$R_{out} = (1/g_m) \parallel r_o = (10^3) \parallel (150 \times 10^3)$$

$$R_{out} = 0.993 \text{ k}\Omega.$$

$$G_v = \frac{R_g}{R_g + R_{sig}} \cdot \left( \frac{(r_o \parallel R_L)}{(r_o \parallel R_L) + 1/g_m} \right)$$

$$G_v = 0.769 \text{ V/V}$$

4. A current mirror circuit has  $V_{DD}=3V$ ,  $I_{ref}=100\mu A$ ,  $I_O=100\mu A$ . calculate the value of R if  $Q_1$  and  $Q_2$  are matched and  $L=1\mu m$  and  $W=10\mu m$ ,  $V_t=0.7V$  and  $\mu_n C_{ox}=200\mu A/V^2$ . Also find the  $r_o$  of the source if  $V_A'=20V/\mu m$

$$I_{ref} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right) (V_{gs} - V_t)^2$$

$$100 \times 10^{-6} = \left(\frac{200 \times 10^{-6}}{2}\right) \left(\frac{10 \times 10^{-6}}{1 \times 10^{-6}}\right) (V_{gs} - 0.7)^2$$

$$V_{gs} = 1.016V$$

$$I_{ref} = \frac{V_{DD} - V_{gs}}{R}$$

$$R = \frac{V_{DD} - V_{gs}}{I_{ref}}$$

$$R = \frac{3V - 1.016}{100 \times 10^{-6}} = 20k\Omega$$

$$V_A \approx V_A' \times L$$

$$= 20 \times 10^6 \times 1 \times 10^{-6}$$

$$V_A = 20V$$

$$r_{o2} = \frac{20}{100 \times 10^{-6}} = 200k\Omega$$

5. For a Common Gate amplifier with active load, which has  $W/L=7.2\mu\text{m}/0.36\mu\text{m}$ ,  $\mu_n C_{ox}=387\mu\text{A}/\text{V}^2$ ,  $r_o=18\text{k}\Omega$ ,  $I_D=100\mu\text{A}$ ,  $g_m=1.25\text{mA}/\text{V}$ ,  $\chi=0.2$ ,  $R_s=10\text{k}\Omega$ ,  $R_L=100\text{k}\Omega$ ,  $C_{gs}=20\text{fF}$ ,  $C_{gd}=5\text{fF}$ ,  $C_L=0$ , determine  $A_{v0}$ ,  $R_{in}$ ,  $R_{out}$ ,  $G_v$  and  $f_H$

$$g_{m1} + g_{m1b} = 1.25 + 0.2 \times 1.25 = 1.5 \text{ mA/V}$$

$$A_{v0} = 1 + (g_{m1} + g_{m1b})r_o = 1 + 1.5 \times 18 = 28 \text{ V/V}$$

$$R_{in} = \frac{r_o + R_L}{A_{v0}} = \frac{18 + 100}{28} = 4.2 \text{ k}\Omega$$

$$R_{out} = r_o + A_{v0}R_s = 18 + 28 \times 10 = 298 \text{ k}\Omega$$

$$G_v = G_{v0} \frac{R_L}{R_L + R_{out}} = A_{v0} \frac{R_L}{R_L + R_{out}} = 28 \frac{100}{100 + 298} = 7 \text{ V/V}$$

$$G_{L1} = \frac{A_{v0}R_s}{R_{out}} = \frac{28 \times 10}{298} = 0.94 \text{ A/A}$$

$$G_i = G_{L1} \frac{R_{out}}{R_{out} + R_L} = 0.94 \frac{298}{298 + 100} = 0.7 \text{ A/A}$$

$$R_{si} = R_s \parallel R_{in} = 10 \parallel 4.2 = 3 \text{ k}\Omega$$

$$R_{sd} = R_L \parallel R_{out} = 100 \parallel 298 = 75 \text{ k}\Omega$$

$$\tau_H = C_{gs}R_{si} + C_{gd}R_{sd}$$

$$= 20 \times 3 + 5 \times 75$$

$$= 60 + 375 = 435 \text{ ps}$$

$$f_H \approx \frac{1}{2\pi\tau_H} = \frac{1}{2\pi \times 435 \times 10^{-12}} = 366 \text{ MHz}$$

6. Determine the small signal voltage gain for a common source amplifier with an active load having  $V_{dd}=3V$ ,  $V_{tn}=|V_{tp}|=0.6V$ ,  $\mu_n C_{ox}=200\mu A/V^2$ ,  $\mu_p C_{ox}=65\mu A/V^2$ . Length of all transistors are  $0.4\mu m$  and Width is  $4\mu m$  with  $V_{an}=20V$ ,  $|V_{ap}|=10V$  and  $I_{ref}=100\mu A$ .

$$I_D = I_{REF} = 100 \mu A = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) V_{OV}^2$$

$$100 = \frac{1}{2} \times 387 \times \left( \frac{7.2}{0.36} \right) V_{OV}^2$$

$$V_{OV} = 0.16 V$$

$$g_m = \frac{I_D}{V_{OV}/2} = \frac{100 \mu A}{(0.16/2) V} = 1.25 \text{ mA/V}$$

$$r_{o1} = \frac{V_{An}}{I_D} = \frac{5 \times 0.36}{0.1} = 18 \text{ k}\Omega$$

$$r_{o2} = \frac{|V_{Ap}|}{I_D} = \frac{6 \times 0.36}{0.1} = 21.6 \text{ k}\Omega$$

$$R'_L = r_{o1} \parallel r_{o2} = 18 \parallel 21.6 = 9.82 \text{ k}\Omega$$

$$A_M = -g_m R'_L = -1.25 \times 9.82 = -12.3 \text{ V/V}$$