

Internal Assessment Test – II/SCHEME AND SOLUTIONS


Sub:	DSDV	Code:	15EC663
Date:	/ 04 / 2019	Duration:	90 mins
		Max Marks:	50
		Sem:	VI
		Branch:	Open Elective
Answer all Questions			

1 Explain synchronous and asynchronous Static RAMs.

Marks	scheme	OBE	
		CO	RB T
[10]		CO3	L2
5M			
5M			

SOLN:- Asynchronous SRAM

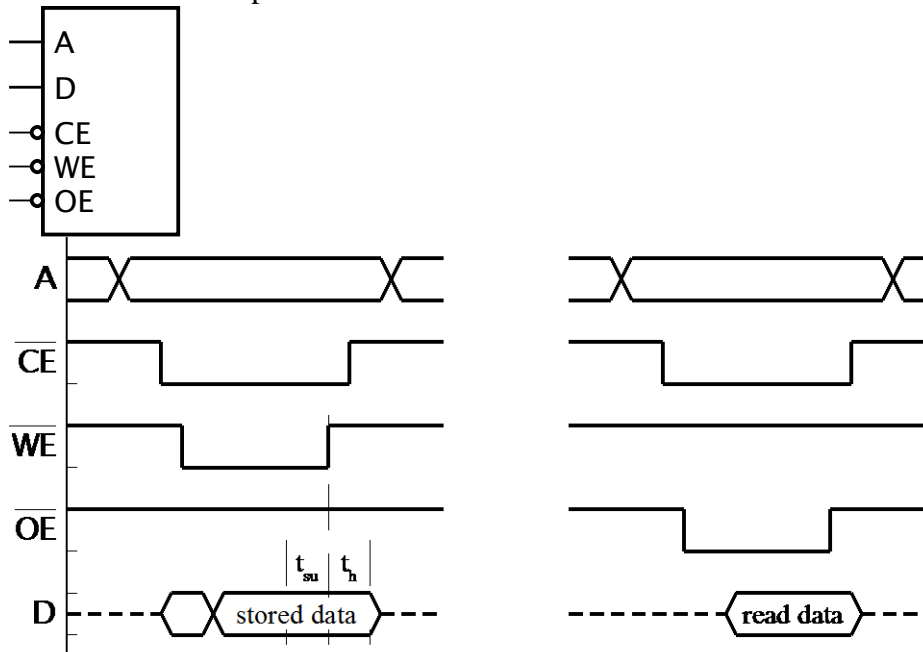- a. Data stored in 1-bit latch cells
- b. Address decoded to enable a given cell
- c. Usually use active-low control inputs
- d. Not available as components in ASICs or FPGAs




Synchronous SRAM

- a. Clocked storage registers for inputs
- b. address, data and control inputs
- c. stored on a clock edge
- d. held for read/write cycle

Flow-through SSRAM


- no register on data output

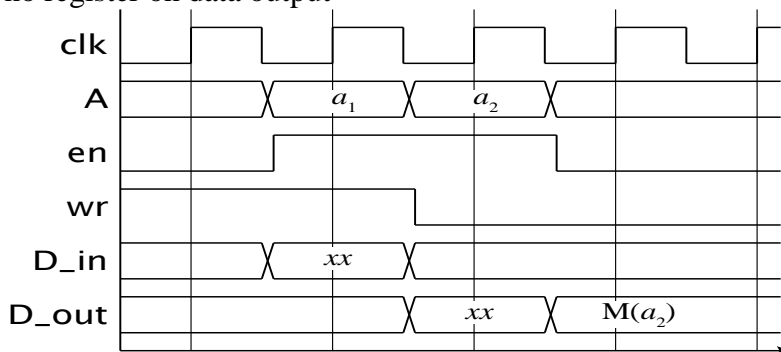

Pipelined SSRAM


- Data output also has a register
- More suitable for high-speed systems

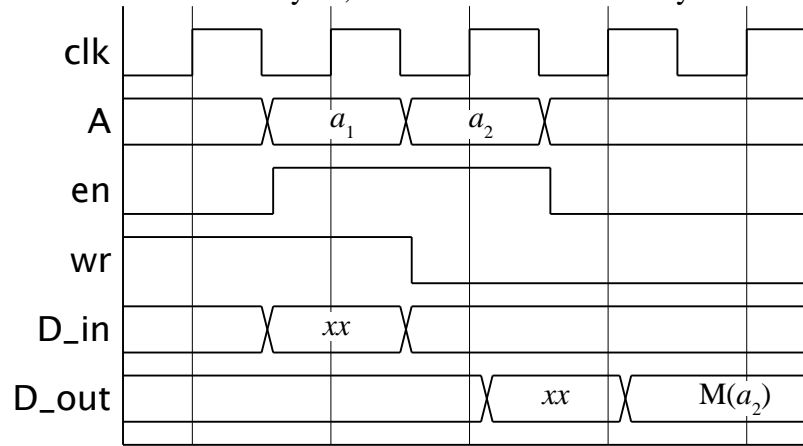- Access RAM in one cycle, use the data in the next cycle



3 Develop a verilog code for pipelined SSRAM.

Verilog code for pipelined SSRAM

 

```

reg    pipelined_en;
reg [15:0] pipelined_d_out;
...
Always @(posedge clk) begin
  if (pipelined_en) d_out <= pipelined_d_out;
  pipelined_en <= en;
  if (en)
    if (wr) begin
      data_RAM([a] <= d_in; pipelined_d_out <= d_in;
    end
    else
      pipelined_d_out <= data_RAM[a];
end


```

- 2 What is Error correction? Obtain ECC for data byte: - 01100001. Find, if received [10] ECC 000111000100 is having error, if so correct it.

Soln: Error-Correcting Codes (ECC)

- Allow identification of the flipped bit
- Hamming Codes
 - E.g., for single-bit-error correction of N -bit word, need $\log_2 N + 1$ extra bits
- Example: 8-bit word, $d_1 \dots d_8$
 - 12-bit ECC code, $e_1 \dots e_{12}$

 e_1, e_2, e_4, e_8 are check bits, the rest data



	CO3	L3
3M		

$$e_1 = e_3 \oplus e_5 \oplus e_7 \oplus e_9 \oplus e_{11}$$

$$e_2 = e_3 \oplus e_6 \oplus e_7 \oplus e_{10} \oplus e_{11}$$

$$e_4 = e_5 \oplus e_6 \oplus e_7 \oplus e_{12}$$

$$e_8 = e_9 \oplus e_{10} \oplus e_{11} \oplus e_{12}$$

ii) The check bits are

- Every data bit covered by two or more check bits
- On write: Compute check bits and store with data
- On read: Recompute check bits and XOR with read check bits
 - result called the *syndrome*
- 0000 => no error
- If data bit flipped
 - covering bits of syndrome are 1
 - = binary code of flipped ECC bit
- If stored check bit flipped
 - that bit of syndrome is 1
- On error, unflip bit and rewrite memory location

$$e_1 = e_3 \oplus e_5 \oplus e_7 \oplus e_9 \oplus e_{11} = d_1 \oplus d_2 \oplus d_4 \oplus d_5 \oplus d_7 = 1 \oplus 0 \oplus 0 \oplus 0 \oplus 1 = 0$$

$$e_2 = e_3 \oplus e_6 \oplus e_7 \oplus e_{10} \oplus e_{11} = d_1 \oplus d_3 \oplus d_4 \oplus d_6 \oplus d_7 = 1 \oplus 0 \oplus 0 \oplus 1 \oplus 1 = 1$$

$$e_4 = e_5 \oplus e_6 \oplus e_7 \oplus e_{12} = d_2 \oplus d_3 \oplus d_4 \oplus d_8 = 0 \oplus 0 \oplus 0 \oplus 0 = 0$$

$$e_8 = e_9 \oplus e_{10} \oplus e_{11} \oplus e_{12} = d_5 \oplus d_6 \oplus d_7 \oplus d_8 = 0 \oplus 1 \oplus 1 \oplus 0 = 0$$

Thus the ECC word is 011000000110.

iii) Determine whether there is an error in the ECC word

000111000100, and if so, correct it.

solution The check bits computed from the data bits of the ECC word

are

$$e_1 = e_3 \oplus e_5 \oplus e_7 \oplus e_9 \oplus e_{11} = 1 \oplus 0 \oplus 1 \oplus 1 \oplus 0 = 1$$

$$e_2 = e_3 \oplus e_6 \oplus e_7 \oplus e_{10} \oplus e_{11} = 1 \oplus 0 \oplus 1 \oplus 0 \oplus 0 = 0$$

$$e_4 = e_5 \oplus e_6 \oplus e_7 \oplus e_{12} = 0 \oplus 0 \oplus 1 \oplus 0 = 1$$

$$e_8 = e_9 \oplus e_{10} \oplus e_{11} \oplus e_{12} = 0 \oplus 0 \oplus 0 \oplus 1 = 1$$

The syndrome is 1101 \oplus 1000 _ 0101. Thus, there is an error in bit e5

of the

read ECC. That bit should be flipped back from 0 to 1, giving the

corrected

ECC word 000111010100.

3 Explain FPGA design with block diagram.

Soln:

FPGA


3M

4M


[10]

CO4


L2

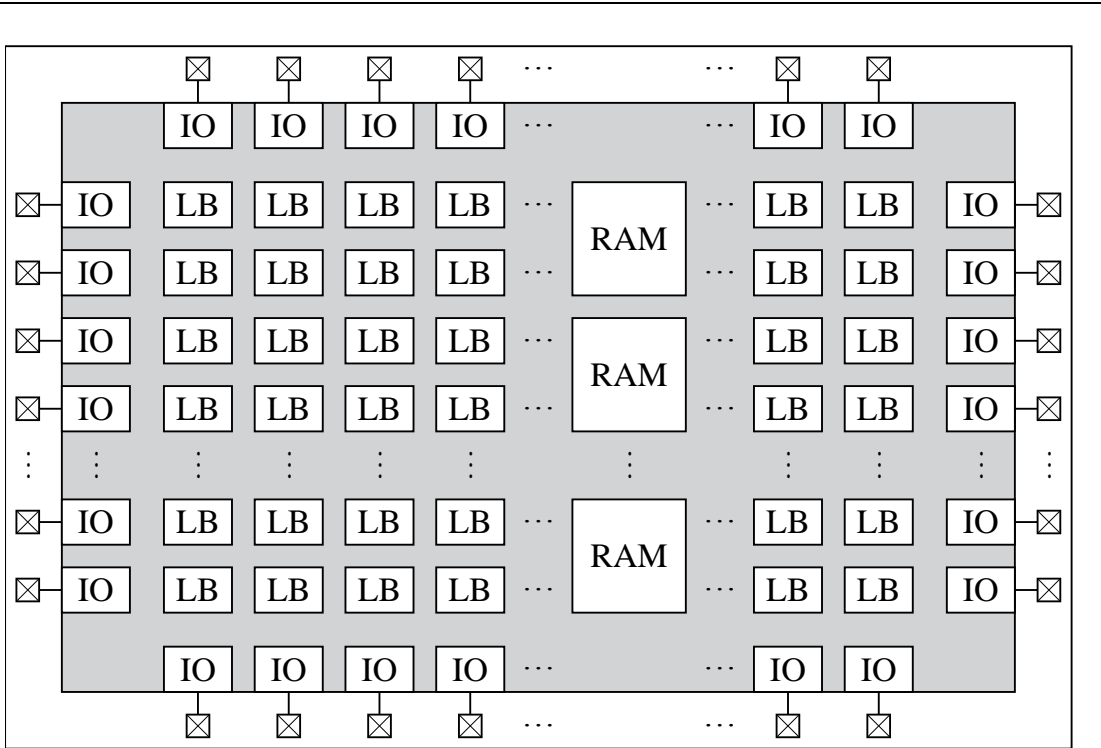


4M

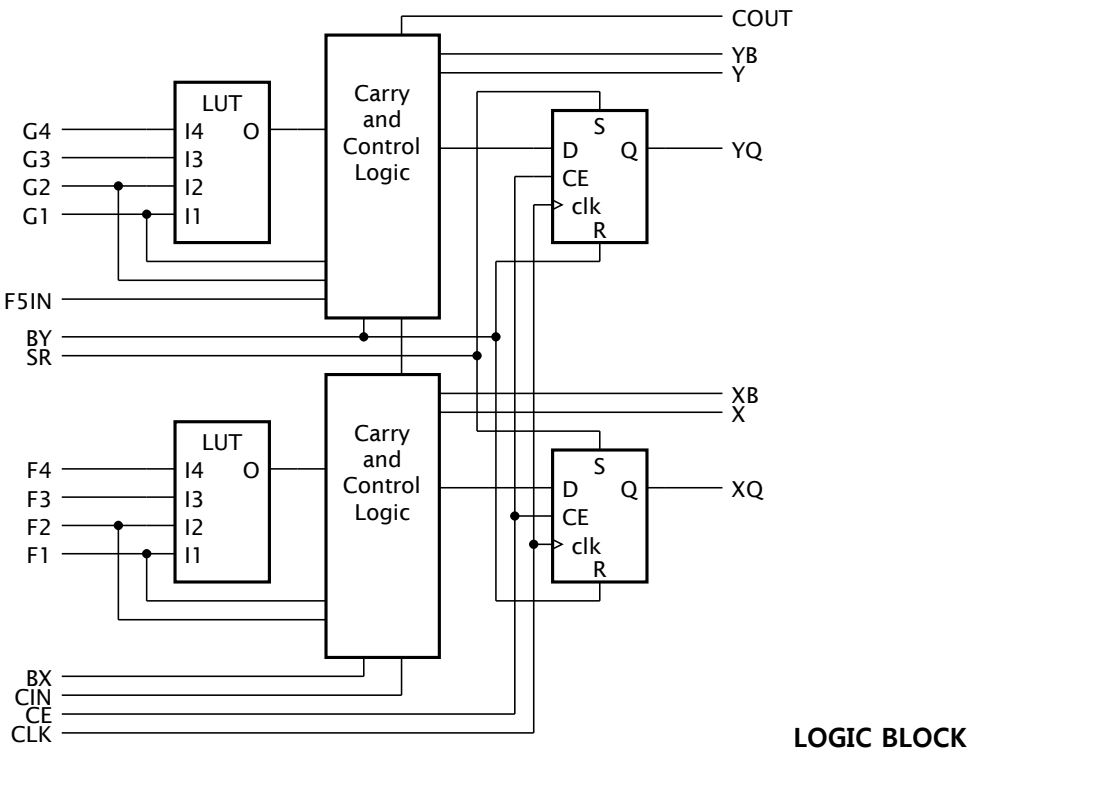

3M

 

 

The basic elements within logic blocks are small 1-bit-wide asynchronous RAMs called lookup tables (LUTs). The LUT address inputs are connected to the inputs of the logic block. The content of an LUT determines the values of a Boolean function of the inputs. By programming the LUT content differently, we can implement any Boolean function of the inputs. The logic blocks also contain one or more flipflops and various multiplexers and other logic for selecting data sources and for connecting data to adjacent logic blocks. The logic block contains two such slices, together with a small amount of additional logic. Each slice consists of two 4-input LUTs, each of which can be programmed to implement any function of the four inputs. The carry and control logic consists of circuitry to combine the LUT outputs, an XOR gate and an AND gate for implementing adders and multipliers, as well as multiplexers that can be used to implement a fast carry chain.

The I/O block of an FPGA is typically organized as shown. The select inputs of the multiplexers are programmed to control whether the output is registered or combinational. The top flip-flop and multiplexer control the high-impedance state of the tristate driver that drives the pin as an output, and the middle flip-flop and multiplexer drive the output value. The output driver is programmable, allowing selection of logic levels (regular 5V TTL, low voltage TTL, or others) and control of the slew rate, that is, rate of voltage change at the output.


	3M				

4 Explain the working of SAR Based ADC with example.


[10]

CO4 L3

 Explain the working of successive approximation ADC.



- * The above fig shows a successive approximation ADC, analog signals are indicated and the rest all are digital.
- * It uses a digital to analog converter internally to make successively closer approximations to the input signal over several clock periods
- * When start signal is activated, the successive approximation register (SAR) is initialized with input value
- * This value is provided to DAC, which produces the first approximation, just less than half of the full scale voltage.
- * Comparator then compares this approximation with input voltage. If ^{input} output is higher, the comparator output is 1. If input is lower, the comparator output is 0.
- * The comparator output is stored as the MSB in SAR, remaining bits are shifted down one place
- * This gives the input to next approximation

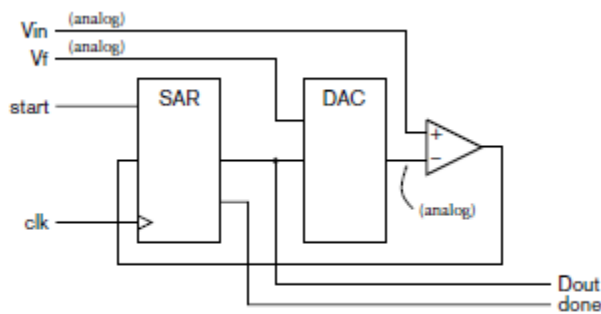

SAR based ADC

5 Explain the parallel bus concept. Briefly discuss the solutions to overcome the [10] disadvantages of parallel buses.

- Interconnect components in a system
 - Transfer bits of data in parallel
- Conceptual structure
 - All inputs and output connected


4M

6M

2M

CO4


L3

 


- Use multiplexer(s) to select among data sources
 - Can partition to aid placement on chip

Multiplexed buses

8.3 Parallel

 


Distributed multiplexed bus

 

- Use tristate drivers for data sources
 - Can “turn-off” (Hi-Z) when not supplying data
- Simplified bus wiring


Tristate buses

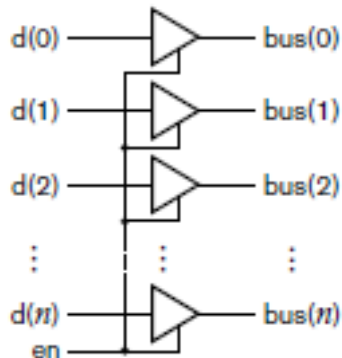


2M

2M

2M

 

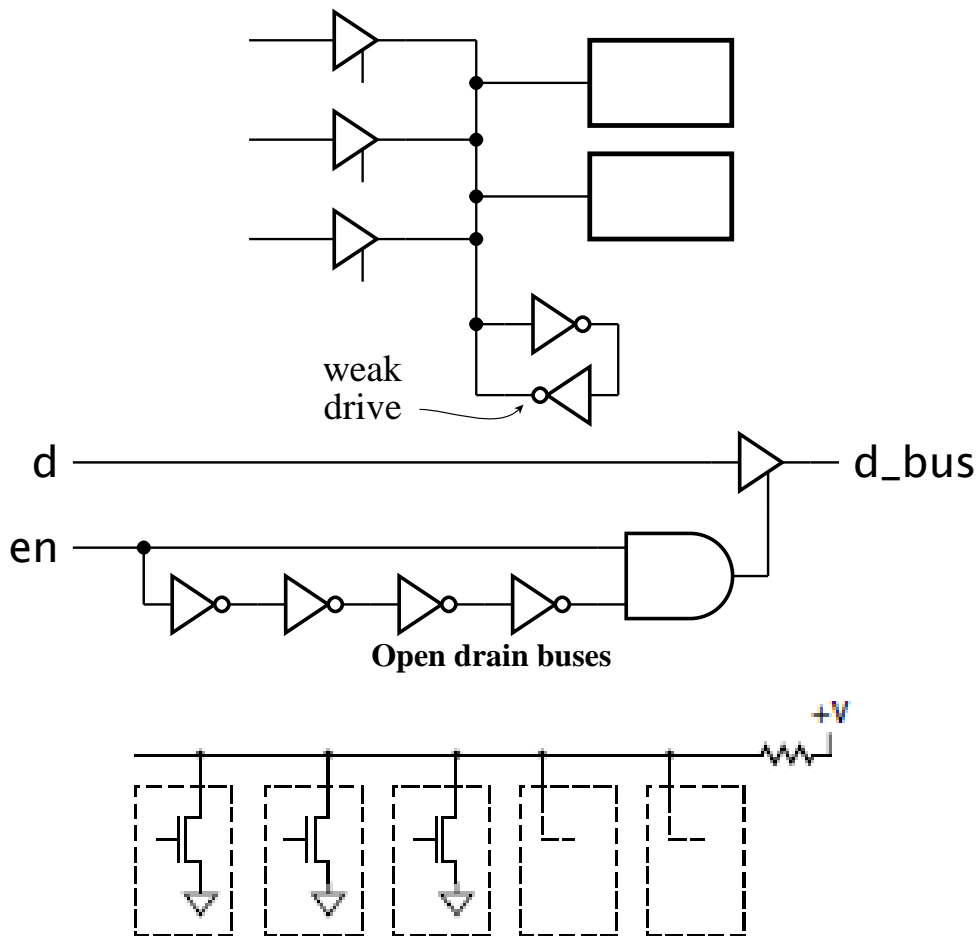- Floating bus can cause spurious switching
 - Use pull-up resistors or weak keepers
- Need to avoid driver contention
 - Dead cycle between turn-off and turn-on
 - Or delayed enable



- Bus is 0 if any driver pulls it low
- If all drivers are off, bus is pulled high
 - Wired-AND
- Can also use open-collector drivers

2M

