

Module-3

- 5 a. Draw the circuit of Darlington emitter follower. Derive the expression for current gain using its ac equivalent circuit. (08 Marks)
- b. What are the advantages of negative feedback in amplifiers? Explain briefly. (06 Marks)
- c. For the voltage series feedback amplifier, derive an expression for output impedance. (06 Marks)

OR

- 6 a. Explain the need of cascading amplifier. Draw and explain the block diagram of two stage cascade amplifier. (08 Marks)
- b. A given amplifier arrangement has the following voltage gains $A_{v_1} = 10$, $A_{v_2} = 20$ and $A_{v_3} = 40$. Calculate the overall voltage gain and determine the total voltage gain in dBs. (06 Marks)
- c. An amplifier with negative feedback has a voltage gain of 120. It is found that without feedback an input signal of 60mV is required to produce a particular output, whereas with feedback the input signal must be 0.5V to get the same output. Find voltage gain (A_v) and β of the amplifier. (06 Marks)

Module-4

- 7 a. Derive an expression for frequency of oscillations in Wien bridge' oscillator. (08 Marks)
- b. Explain the operation of class B push pull amplifier. Prove that the maximum efficiency of class B configuration is 78.5%. (08 Marks)
- c. A crystal has following parameters. $L = 0.3344\text{H}$, $C = 0.065\text{pF}$, $C_m = 1\text{pF}$ and $R = 5.5\text{k}\Omega$. Calculate: i) Series resonance frequency ii) Parallel resonance frequency. (04 Marks)

OR

- 8 a. Explain the operation of class A transformer coupled power amplifier and prove that the maximum efficiency is 50%. (08 Marks)
- b. A class B push pull amplifier operating with $V_{CC} = 25\text{V}$ provides a 22V peak signal to 8Ω load. Calculate circuit efficiency and power dissipated per transistor. (06 Marks)
- c. Explain the principle of operation of oscillator and the effect of loop gain ($A\beta$) on the output of oscillator. (06 Marks)

Module-5

- 9 a. With the help of neat diagram, explain the working and characteristics of N-channel JFET. (08 Marks)
- b. Determine Z_i , Z_o and A_v for JFET common source amplifier with fixed bias configuration using AC equivalent small signal model. (08 Marks)
- c. Write down the differences between BJT and JFET. (04 Marks)

OR

- 10 a. With the help of neat diagrams, explain the construction, working and characteristics of N-channel depletion type MOSFET. (10 Marks)
- b. Write down the differences between MOSFET and JFET. (04 Marks)
- c. For the circuit given in the Fig Q10(c), determine: i) Input impedance ii) Output impedance and iii) voltage gain. (06 Marks)

 


Fig Q10(c)

CBGS SCHEME

USN 1 C R 1 7 E E 0 4 2

17EE34

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019
Analog Electronic Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Draw a double ended clipper circuit and explain its working principle with transfer characteristics. (07 Marks)
- b. Draw and explain the working of clamper circuit which clamps the positive peak of a signal to zero. (07 Marks)
- c. With suitable graph, explain the significance of operating point. (06 Marks)

OR

- 2 a. Derive the expression for stability factor for fixed bias circuit, with respect to I_{co} , V_{BE} and β . (07 Marks)
- b. A voltage divider biased circuit has $R_1 = 39k\Omega$, $R_2 = 82k\Omega$, $R_c = 3.3k\Omega$, $R_E = 1k\Omega$ and $V_{CC} = 18V$. The Silicon transistor used has $\beta = 120$. Find Q-point and stability factor. (08 Marks)
- c. Calculate the Q point values (I_c and V_{CE}) for the circuit given in Fig Q2(c). (05 Marks)

 


Fig Q2(c)

Module-2

- 3 a. State and prove Millers theorem. (08 Marks)
- b. Starting from fundamentals define h-parameters and obtain an h-parameter equivalent circuit of common emitter configuration. (08 Marks)
- c. Compare the characteristics of CB, CE and CC configurations. (04 Marks)

OR

- 4 a. Derive an expression for input impedance, current gain and output impedance for an emitter follower circuit using h-parameters model for the transistor. (08 Marks)
- b. For the transistor connected in CE configuration, determine A_v , A_i , R_i and R_o using complete hybrid equivalent model. (08 Marks)
- c. A transistor in CE mode has h-parameters $R_L = 1k\Omega$, $h_{ie} = 1k\Omega$, $h_{re} = 2 \times 10^{-4}$, $h_{fe} = 100$ and $h_{oe} = 20\mu A/V$. A transistor in CE mode has h-parameters $h_{ie} = 1.1k\Omega$, $h_{re} = 2 \times 10^{-4}$, $h_{fe} = 100$ and $h_{oe} = 25\mu A/V$. Determine the equivalent CB parameters. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.