 


CBCS SCHEME

17EE34



USN

--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, Aug./Sept.2020 Analog Electronic Circuits


Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

 
- 1 a. For the clipper circuit shown in fig. Q1(a), the input is $V_i = 50 \sin \omega t$. Calculate and plot to scale the transfer characteristic, indicating slopes and intercept. (10 Marks)



 - b. An emitter bias circuit has $R_C = 2K \Omega$, $R_E = 680 \Omega$, $V_E = 2.1V$, $V_{CE} = 7.3V$, $I_B = 20\mu A$. Find V_{CC} , R_B & β . (05 Marks)
- c. What is meant by transistor biasing? Compare different biasing methods used for transistor biasing with respect to stability. (05 Marks)

OR

- 2 a. Design a suitable circuit represented by the box shown below. Which has input and output waveforms as indicated in fig. Q2(a). (08 Marks)



- b. Find the operating point for the voltage divider bias circuit with $\beta = 80$ and $V_{BE} = 0.6V$. Find the new operating point when β changes to 100 and V_{BE} changes to 0.25V. Given $V_{CC} = 15V$, $R_1 = 100K\Omega$, $R_2 = 18K\Omega$, $R_C = 4.7K\Omega$ and $R_E = 1K\Omega$. (08 Marks)
- c. Explain the circuit of a transistor switch being used as an inverter. (04 Marks)

Module-2

- 3 a. Draw the hybrid small signal model of a transistor. Mention the advantages of h-parameters. (04 Marks)
- b. Derive the expression for A_V , A_I , Z_i and Z_o for CE fixed bias configuration using complete hybrid equivalent model. (10 Marks)
- c. State and prove Miller's theorem. (06 Marks)


CMRIT LIBRARY
BANGALORE - 560 037

OR

- 4 a. Derive the expressions for Z_i , Z_o , A_V and A_I for CB - configuration of transistor using approximate hybrid equivalent model. (10 Marks)

- b. The circuit shown in fig.Q4(b) uses transistor with $h_{ie} = 1100\Omega$, $h_{fe} = 50$, $h_{oe} = 0.025 \times 10^{-3} \text{ S}$, $h_{re} = 2.5 \times 10^{-4}$. Calculate $R_i = \frac{V_1}{I_1}$, $R'_i = \frac{V_1}{I_b}$, $A_v = \frac{V_o}{V_1}$ and $A_{vs} = \frac{V_o}{V_s}$.

Fig.Q4(b)

 

(10 Marks)

Module-3

- 5 a. Explain with the help of circuit, what is cascade connection? What are the advantages of this connection? (06 Marks)
 b. What is negative feedback in amplifiers? Show that negative feedback increases the bandwidth of an amplifier. (08 Marks)
 c. An amplifier with negative feedback has a voltage gain of 100. It is found that without feedback, an input signal of 50mV is required to produce a given output. Where as with feedback the input signal must be 0.5V for the same output. Determine the value of A and β . (06 Marks)

OR

- 6 a. With appropriate h – parameters equivalent circuit, obtain the expression for Z_i , Z_o , A_v for a Darlington emitter follower. (10 Marks)
 b. Derive expression Z_{if} and Z_{of} for voltage series feedback amplifier. (10 Marks)

Module-4

- 7 a. Discuss the different types of power amplifiers. (04 Marks)
 b. Show that the maximum percentage efficiency for a series fed class A amplifier is 25%. (10 Marks)
 c. A Quartz crystal has $L = 0.12\text{H}$, $C = 0.04\text{PF}$, $C_M = 1\text{PF}$ and $R = 9.2\text{K}\Omega$. Find
 i) f_s and ii) f_p . (06 Marks)

OR

- 8 a. State and explain the Barkhenssen's criterion to obtain sustained oscillations. (06 Marks)
 b. With the help of circuit diagram, explain the working principle of R_c = phase shift oscillator, with relevant equations. (08 Marks)
 c. A class B amplifier provides a 20V peak signal to a 16Ω load and a power supply of $V_{CC} = 30\text{V}$. Determine the input power, output power and circuit efficiency. (06 Marks)

Module-5

- 9 a. Draw the JFET amplifier using fixed bias configuration. Derive Z_i , Z_o and A_v using small signal model. (08 Marks)
 b. Compare JFET and MOSFET. (04 Marks)